

Digital System

- ① - Boolean expressions, laws, k-maps, Hazards in digital system
- ② - Multiplexer, Decoder, Encoder
- ③ - Flip-flop, interconnection, counters, shift registers
- ④ - Number systems, representation, fixed point & floating point arithmetic.

① Combinational circuits

$$y = f(x)$$

In this current output depends on current input.
Its ckt. of sequential elements.

② Sequential circuits

$$y = f(x, s)$$


$s \rightarrow$ state (previous output)

In this current output depends on current input & previous output i.e. state. ex: $\rightarrow$ flip flop


formula for number of flip-flop required $\equiv \log_2 n$

③ Combinational function

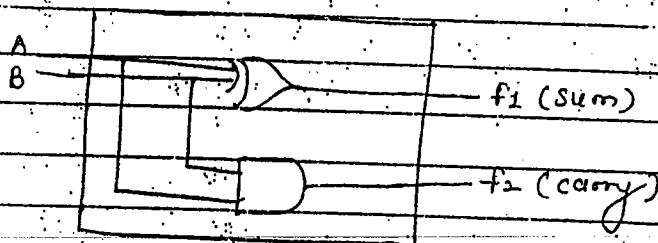- $\rightarrow$ Multi input & single o/p system ex: $\rightarrow$ XOR gate
- $\rightarrow$ Multi input & multi o/p system ex: $\rightarrow$ Half Adder




Half Adder

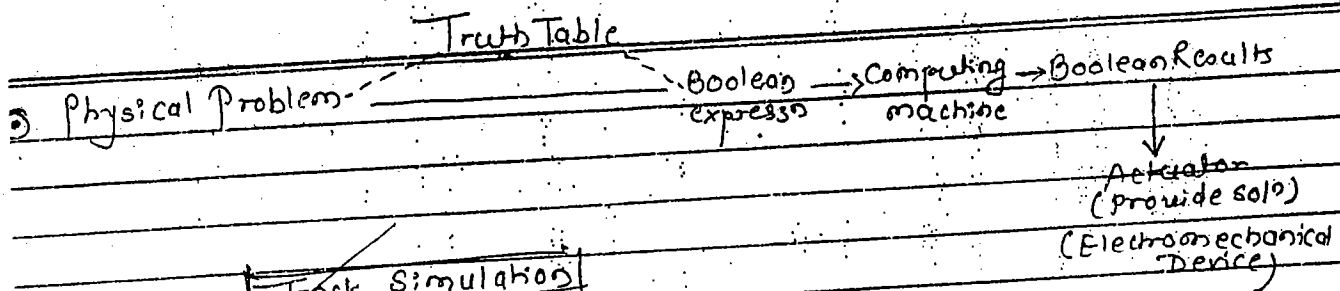

Track Simulation

ex: $\rightarrow$

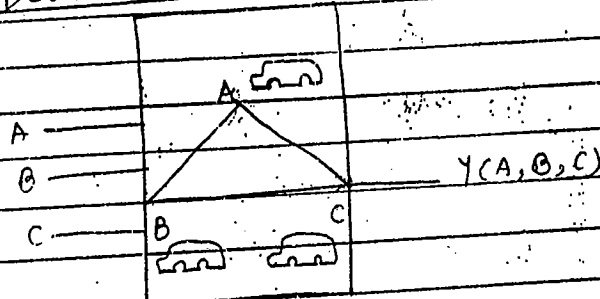


- Track laid in form of equilateral triangle.
- Three vehicles moving with same velocity are present at three vertices.
- System should generate output 1 as when any two vehicles meet together.

0 $\rightarrow$ clockwise movement

1 $\rightarrow$ anticlockwise movement

minterms: - product of i/p such that product is 1 i.e. $A'B'C$

	A	B	C	Y
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

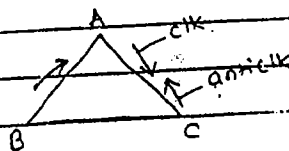

max terms

max terms $\rightarrow$ sum of i/p such that total value of sum is 0 $\rightarrow A+B+C$

$$0 + 0 + 0 \rightarrow 0$$

When all vehicle moving in same direction then they can not meet together.

* Sum of Products * (SOP)

* Product of sum * (POS)

Input combination for which output is '1' called min term.

Sum of Products (SOP) All the Min term

$$Y(A, B, C) = A'B'C + A'BC' + A'BC + AB'C' + AB'C + ABC'$$

$$= \sum (1, 2, 3, 4, 5, 6)$$

* Product of sum (POS) *

$$Y(A, B, C) = (A+B+C) \cdot (A'+B'+C') = \pi(0, 7)$$

for sum of products (SOP) $\Rightarrow$

6 ... (3 i/p) AND gate

1 ... (6 i/p) OR gate

3 ... NOT gate

for product of sum (POS) $\Rightarrow$

2 ... (3 i/p) OR gate } 3 - NOT gate

1 ... (2 i/p) AND

If more min term i.e. output is '1' then use POS because we have to reduce h/w required.

min


$$A+B$$

1
2

A	B	OR
0	0	0
0	1	1
1	0	1
1	1	1

POS $\Rightarrow f(A,B) = A+B$ ✓
 SOP $\Rightarrow f(A,B) = A'B + AB' + AB$

min term
go for
pos

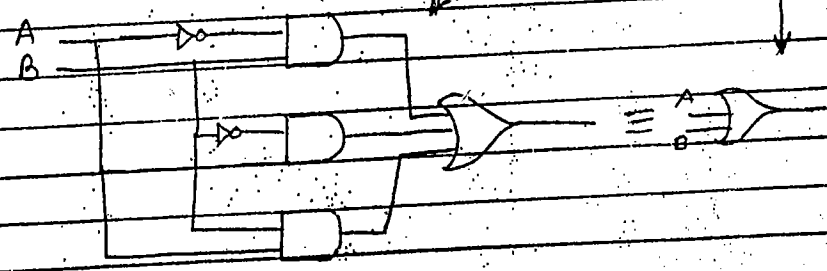

A	B	AND
0	0	0
0	1	0
1	0	0
1	1	1

max term
sop

POS $\Rightarrow (A+B) \cdot (A+B') \cdot (A'+B)$ //
 SOP $\Rightarrow (A+B')$ ✓

SOP

Identify the max terms for following expressions

$f(A,B,C) = A' + BC$

- (a) 3, 5, 6
- ✓ (b) 4, 5, 6
- (c) 3, 4, 5, 6
- (d) None

A	B	C	$A' + BC$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Max term

$\Rightarrow (A' + BC) = (A' + B) \cdot (A' + C)$ } POS form

A	B	C	A	B	C
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	0
1	1	1	1	1	1

{ 4, 5, 6 }

Remaining 0, 1, 2, 3, 7 are minterms

② Consider following 4 i/p and 4 o/p system.

I/p's are a b c d
o/p's are w x y z.

The system having the following behaviour

$$p_0 = (p_i + 3) \text{ Mod } 16$$

Where,

$p_0, p_i \rightarrow$ Are decimal Value of
Concerned binary i/p's and
o/p's resp.

A	B	C	D	
1	1	0	1	$\rightarrow p_i$
				13
Then				
$(13 + 3) \text{ Mod } 16 = 0 = p_0$				
$\downarrow$				
	w	x	y	z
	0	0	0	0
	$\rightarrow$ Max term			

See page No - ④ $\Rightarrow$

to be continue...

+ → OR 16/6/2011
 ... → AND

Note:
 See page No - 11 directly

* Boolean laws *

① Identity law ⇒ Identical operation on identical variable gives unique result.

ex → $A + A + A = A$
 $A \cdot A \cdot A = A$ } Identical Law

② AND, OR follows this law.

NAND ($\uparrow$) ⇒ $\neg((A \uparrow A) \uparrow A) \uparrow A \dots$
 $(\bar{A}) + \bar{A} = A + \bar{A} = 1, 0$

$\boxed{A\bar{B} = \bar{A} + B = A \uparrow B}$

③ NAND, NOR does not follow identity law.

④ XOR ⇒ $\neg((A \oplus A) \oplus A) \oplus A \dots = 0$, { alternates 0, A }
 $0 \oplus A = A$
 $A \oplus A = 0, \checkmark$

∴ XOR and XNOR does not follow identity law.

⑤ $\boxed{A \oplus B = A + B' = \oplus(A, B)}$ $\frac{00}{11} A+B$

$\neg((X \oplus X) \oplus X) \oplus X \dots = 1$
 $X \oplus X' = 1$

$\boxed{1 \oplus X' = 1}$

∴ $\oplus$ follows identity law.

Note: AND, OR and $\oplus$ follows Identity law.

only 21 (12)

Continue...

A	B	C	D	
1	1	0	1	$\Rightarrow P_i$
				13
Then $(13+3) \text{ Mod } 16 = 0 = P_0$				
				$\Downarrow$
				$w \times x \times y \times z$
				$\textcircled{0} \ 0 \ 0 \ 0$
				$\rightarrow \text{max term}$

which of the following gives eqn for

$w(A, B, C, D)$

- ~~X~~ $\textcircled{a} \sum (3, 4, 5, 6, 7, 8, 9, 10, 11, 12)$
- ~~X~~ $\textcircled{b} \sum (5, 6, 7, 8, 9, 10, 11, 12)$
- ~~X~~ $\textcircled{c} \sum (6, 7, 8, 9, 10, 11, 12, 13)$
- ~~X~~ $\textcircled{d} \sum (5, 6, 7, 8, 9, 10, 11, 12, 13)$

Σ min term
(1) only

Soln: 13 can not be min term - because $(13+3) \text{ Mod } 16 = 0$
so eliminate option $\textcircled{a}$ and $\textcircled{d}$

$P_i = 3$ $P_0 = (P_i + 3) \text{ Mod } 16$
 $= (3 + 3) \text{ Mod } 16$
 $P_0 = 6$

	A	B	C	D	P_i	w	x	y	z
$P_i = 3$	0	0	1	1	6	$\textcircled{0}$	1	1	0

for 3 binary is

3 cannot be Min term

eliminate option $\textcircled{a}$

$\therefore$ The correct option is $\textcircled{b}$ Ans.

Observation: If $P_0 = (P_i + n) \mod 16$ then

$n \rightarrow$ is any no. from 0 to ∞

$P_i \rightarrow$ is from 0 to 15 for 4-variable

then option (c) is always correct option

③ with resp. to Above problem identify the correct statement

① Except the function 'w' all the output function having equal no. of minterm and maxterm.

② Except for the f'n 'z' all output having equal no. of minterm and maxterm.

③ All the outputs having equal no. of Minterm and maxterm.

④ only f'n 'w' has 8 minterm and 8 maxterm.

Ex. f(A,B,C)

we get 8 input
by these are 3-variable

Ex.

8 input

P_i is from 0 to 15

This is for 3 variable

$P_0 = (P_i + k) \mod 16$
Where k is any no. from 0 to 15

$$P_0 = (P_i + 3) \mod 16$$

A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	1
1	0	1	1	1	1	1	0
1	1	0	0	1	1	1	1
1	1	0	1	0	0	0	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	1	0

That's these are equal no. of minterms and maxterms for all outputs

Characteristics of Boolean Expression

- Duality
- Complementation

① Duality :-

$$\begin{array}{c} \text{dual} \curvearrowright \\ F(x_1, x_2, x_3, \dots, x_n, +, \cdot, \uparrow, 0) \\ \text{Boolean variable} \quad \text{operator} \\ \searrow \\ F_d(x_1, x_2, x_3, \dots, x_n, \cdot, +, 0, \uparrow) \end{array}$$

$$AND \Rightarrow OR$$

$$0 \Rightarrow 1 \quad (0 \text{ changes to } 1 \text{ and vice versa})$$

→ providing function properties indirectly

- Inter-conversion realization across the Logic system.

$$\boxed{+ve \Rightarrow -ve}$$

Categories of Boolean exp. on basis of Behaviour:

- $f = f_d$ Orthogonal $\Rightarrow f_d \rightarrow f'$
- Self-dual $\Rightarrow f_d \rightarrow f$
- Non-orthogonal
- Non-self-dual $\Rightarrow f_d \neq f'$
 $f_d \neq f$

AND Replace with OR & vice-versa

$$f_1(A, B) = A \cdot B + A \cdot B' \quad (\text{EX-OR})$$

$$\begin{aligned} f_{1d}(A, B) &= (A' + B) \cdot (A + B') \quad \text{EX-NOR} \\ &= A'B' + AB \quad (\text{EX-NOR}) \end{aligned}$$

$$f_1' = f_{1d} = (A' + B) \cdot (A + B')$$

$$f_{1d} = f_1' \text{ orthogonal}$$

For Even no. of Variable, EX-OR,

EX-NOR follows Complementary relation.

For odd no. of Variable, EX-OR

EX-NOR follows Equality relation.

Example:- $A \oplus B \oplus C = A \odot B \odot C$

$$A \oplus B = (A \odot B)'$$

$$f_2(A, B, C) = AB + BC + CA$$

$$f_{2d}(A, B, C) = (A+B)(B+C)(C+A)$$

$$\Rightarrow (B+AC)(C+A)$$

$$AC + AC + AB = AB + BC + CA$$

$$f_{2d} = f_2$$

Check

$$a' + 1 = 1$$

$$1 \cdot 0 = 0$$

$$f_3(A, B) = A + B$$

$$f_{3d}(A, B) = A \cdot B$$

$$f_3' = A \cdot B, f_{3d} \neq f_3, f_{3d} \neq f_3'$$

$$f$$

$$f_d$$

property (p)


If f has property p, then f_d also follows property p.

5V $\rightarrow$ 1
 -5V $\rightarrow$ 0

+ve logic and -ve Logic

+ve logic : In +ve most voltage is '1'

-ve logic : In -ve most voltage is '0'

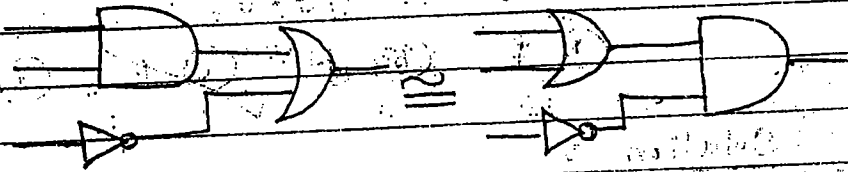

If it is +ve logic then it is -ve logic

Vice versa


If it is -ve logic then it is +ve logic

$$A' + B' + C' = A'(B + C)$$

+ve logic -ve logic system

+ve logic AND become OR in -ve logic

+ve logic NAND becomes NOR in -ve logic

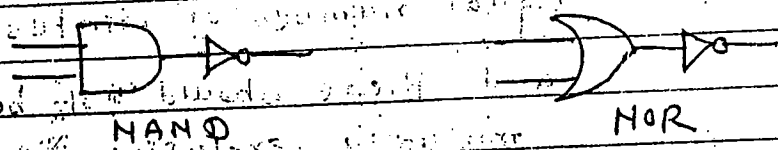

$$\boxed{f = f_d} \quad \swarrow \quad \boxed{f = f_1}$$

* Self Duality *

Que $\rightarrow f(A, B, C) = \sum (0, 1, 2, 3)$ } it is self dual f's
 the dual function of f is f_1

$$f' \cdot f_1' + f \cdot f_1$$

(a) f (b) f_1' (c) 1 (d) 0

Solution :

$$\begin{aligned} f' \cdot f_1' + f \cdot f_1 &= f' \cdot f_1' + f \cdot f \\ &= f' + f \\ &= 1 \quad \text{Ans} \end{aligned}$$

$$f(A, B, C) = (A'B'C) + A$$

$$f_d(A, B, C) = (A' + B' + C) \cdot A$$

Note: A boolean function becomes Self dual if and only if it contains

Equal number of minterm and maxterm
 and there should not be any
mutually exclusive term

The presentation of mutually exclusive term is given by condition.

(8)

$$\Sigma = \min = 1 \text{ SOP}$$

$$\Pi = \max = 0 \text{ POS}$$

$$f(x_1, x_2, x_3, \dots, x_n) = f(x'_1, x'_2, x'_3, \dots, x'_n)$$

$$f_1(A, B, C) = \Sigma(0, 1, 3) \quad \text{Not a self dual func}$$

$$f_2(A, B, C) = \Sigma(0, 1, 2, 6) \quad \text{Not self dual fn.}$$

Minterm $\rightarrow$ output 1

Maxterm $\rightarrow$ output 0

$$f_2(0) = 1 \quad f_2(0, 0, 0)$$

$$f_2(1) = 1 \quad f_2(0, 0, 1)$$

$$f_2(2) = 1 \quad f_2(0, 1, 0)$$

$$f_2(6) = 1 \quad f_2(1, 1, 0)$$

$$f_2(7) = 0 \quad f_2(1, 1, 1)$$

maxterm

The function f_2 is not self dual.

1 and 6 are mutually exclusive

Hence, it can not be self dual.

$$\text{If } (0, 7), (1, 6), (2, 5), (3, 4)$$

then they are Mutual Exclusive

If 0 is present then there is no 7 then it is called self dual.

$$f_3(A, B, C) = \Sigma(0, 1, 2, 3)$$

$\rightarrow$ self dual

$(0,7), (1,6), (2,5), (3,4)$

$2^3 = 8$ combinations

Q. What will be number of self dual function are possible with three boolean variables, (A, B, C)

$n=3$

- (a) 8 (b) 8 (c) 16 (d) 256

Soln: $\sum (0, 1, 2, 3)$
 $\sum (0, 1, 2, 4)$
 $\sum (0, 1, 5, 3)$

$n-1$
 $\text{no. of group} = 2$
 $\text{no. of self} = 2$
 $2^{n-1} = 2^{3-1} = 2^2 = 4$

4 group
 $2^4 = 16$
 $2^{\text{self dual}}$

$\sum (0, 1, 5, 4)$

2^{n-1}
 $2^{3-1} = 2^2 = 4$

$(0,7), (2,5), (1,6), (3,4) = 2^4 = 16 = 2^{(\text{no. of groups})}$

Q. How many self dual possible with n boolean variable

$\text{no. self dual} = 2$

- Ans: (a) 2^{n-1} (b) $2^n - 1$ (c) 2^{2^n} (d) $2^{2^{n-1}}$

Soln: n variable 2^n combinations are possible

$3 = 2^3 = 8$

$\frac{2^n}{2} = 2^{n-1}$ groups

$2^2 = 4$

$2^{(\text{group})} = (2^{2^{n-1}})$ Ans

$2^{2^{n-1}}$

$2^4 = 2^4 = 16$

Ans: 16

Complementation

The complementation obtain similar to that of dual with only exception is even variable also to be replace by their complements.

$$F = F(x_1, x_2, x_3, \dots, x_n, +, \cdot, 0, 1)$$

$$F' = F^D(x_1', x_2', x_3', \dots, x_n', \cdot, +, 1, 0)$$

(n) Variable $\longleftrightarrow$ complemented.

$$AND \longleftrightarrow OR$$

$$0 \longleftrightarrow 1$$

Complementation in term of Duality

$$F^D(x_1, x_2, x_3, \dots, x_n) = F_d(x_1', x_2', x_3', \dots, x_n')$$

Duality in term of Complementation.

$$F_d(x_1, x_2, x_3, \dots, x_n) = F'(x_1', x_2', x_3', \dots, x_n')$$

If the variable of Complementation function is complemented then it becomes dual.

$$F(A, B, C) = A + B \cdot C$$

$$F_d(A, B, C) = A \cdot (B + C)$$

$$F'(A, B, C) = A' \cdot (B' + C')$$

$$F'(A, B, C) = F_d(A', B', C')$$

$$= A' \cdot (B' + C')$$

only variable of F_d are complement

Vice-Versa

$$f_d(A, B, C) = f'_d(A', B', C')$$

$$= (A')' \cdot (B')' + (C')'$$

$$= A(B+C)$$

Gate Que

How many boolean functions possible with n boolean such that

$$f(x_1, x_2, x_3, \dots, x_n) = f'(x'_1, x'_2, \dots, x'_n)$$

It is nothing but both are same

$$f(x_1, x_2, \dots, x_n)$$

no. of Variable
Number of
of f

Q

If the following exp. solve then

$$A' + Bc = 0$$

$$AB + A'c = 1$$

$$B'D' + BD = 0$$

What will be the values of A, B, C, D

Soln :- $A' = 0$ $Bc = 0$ then

$$\therefore (A = 1)$$

$$A' + Bc = 0$$

$$AB + A'c = 1$$

$$B'D' + BD = 0$$

$$0 + 1 \cdot 0 = 0$$

$$1 \cdot B + 0 \cdot c = 1$$

$$\therefore B = 1$$

$$D = 0$$

$$A' + Bc = 0$$

$$A = 1$$

Mixed Logic

How many binary functions are possible with n boolean variables

$$2^{2^n}$$




(10)

$P \rightarrow$ no. of variable
 $m \rightarrow$ Nature of variable
 $n \rightarrow$ Nature of function

$n \rightarrow$ no. of variable
 $2 \rightarrow$ Nature of variable (binary)
 $2 \rightarrow$ Nature of function

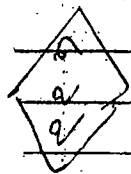Ans:- How many boolean function possible with n -boolean variable



Ternary $\left\{ \begin{matrix} 0 \\ 1 \\ 2 \end{matrix} \right.$

$\Rightarrow n \rightarrow$ Number of variable
 $2 \rightarrow$ Nature of variable
 $2 \rightarrow$ Nature of function


for 3 function

$$3^2 = 3^4 = 81$$

$P \rightarrow$ Number of variable
 $m \rightarrow$ Nature of variable
 $n \rightarrow$ Nature of function

① How many boolean function possible with 4 binary variable
 $2^{34} = 2^{34}$

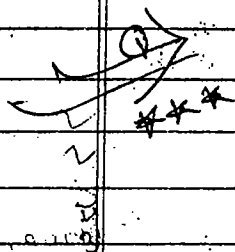$m^n P \rightarrow$ Number of $(m\text{-ary})$ function formed by P variable of n -valued Algebra.



① How many boolean function possible with 3 boolean variables such that the output contains Atmost 3 minterms



$$8C_0 + 8C_1 + 8C_2 + 8C_3 + \dots + \dots = 1 + 8 + 28 + 56 = 93$$

with 8 min term

$$8C_0 + 8C_1 + 8C_2 + 8C_3 + 8C_4 + 8C_5$$

$$+ 8C_6 + 8C_7 + 8C_8$$

$$2^8 = 256$$

no. of boolean exp. with 3 variable

such that it content

$$= 256 - (8C_0 + 8C_1 + 8C_2)$$

$$= 256 - 37$$

$$\text{Hence, the number of boolean exp.} = 219$$

Q. How many neutral function are possible with 3 variables.

$$2^n C_{2^n} = 2^3 C_{2^3} = 8C_4$$

$$= 35$$

Q. How many min term function with 3 variables

is there

How many min term function with 3 variables

- (a) $2^n C_{2^n}$ (b) $2^{2^n} C_{2^n}$ (c) $2^n C_n$ (d) None

$$2^3 + 2^3 + 2^3 + 2^3 + 2^3 + 2^3 + 2^3 + 2^3$$

$$= 8 + 8 + 8 + 8 + 8 + 8 + 8 + 8$$

Continue...

② Commutative Law $\Rightarrow$ Order of inputs does not change the result.

ex: $\rightarrow$ $AB = BA$ } Commutative
 $A+B = B+A$

③ All symmetric functions follow commutative law. NAND, NOR, XOR & XNOR are symmetric functions.

④ A symmetric function is not going to be changed by permuting the inputs.

$$f(A, B, C) = AB + BC + CA$$

****** $f(B, A, C) = f(C, A, B) = f(C, B, A)$ ******

above function follows commutative law.

BCA	—	
CAB	—	
ABC	—	

⑤ A boolean function is said to be symmetric if it contains all possible terms for each a-number (nC_2). (The a-number of a term is total number of 1's in its binary pattern.)

ex: $\rightarrow$ a-number of 8 (1000)₂ is '4'
 a-number of 7 (111)₂ is '3'.

$$\text{ex: } \rightarrow f(A, B, C) = \sum (3, 5, 6, 7) \equiv \sum_{a=2,3} (A, B, C)$$

$\downarrow \downarrow \downarrow \downarrow$
 a-number 2, 2, 2, 3 (1's in 3, 5, 6, 7)

Total possible terms with a-number '2' = ${}^3C_2 = 3$

Total possible terms with a-number '3' = ${}^3C_3 = 1$

$\therefore$ the given function satisfies req. for a-number 2 & a-number 3 & hence it is symmetric.

$S \rightarrow$ symmetric function

The given function is symmetric as it satisfied nC_2 requirement for each a-number & hence this function follows commutative law.

$$\text{ex} \rightarrow S_{0,3}(A, B, C) = f(A, B, C) = \sum (0, 7) \quad \left. \begin{array}{l} \sum C_0 = 1 \\ \sum C_2 = 1 \end{array} \right\}$$
$$= A'B'C' + ABC$$

Que) Check whether following function is symmetric or not and if its not symmetric what are the minimum no. of terms to be added to make the function as symmetric.

$$f(A, B, C, D) = \sum (1, 2, 3, 4, 6, 8, 10, 12, 15)$$

$n=4$ a-num $\downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow$
1, 1, 2, 1, 2, 1, 2, 2, 4

$$4C_1 + 4C_2 + 4C_4 \rightarrow \text{total term}$$

$$4 + 6 + 1 = 11$$

$4C_1$ satisfied i.e. 4 1's present & $4C_4$ also satisfied
But $4C_2$ not satisfy as $4C_2 = 6$ & terms are only 4
 $\therefore$ not symmetric

The function is symmetric if these terms 5 & 9 are added.

$$f(A, B, C, D) + \sum (5, 9) \quad \left. \begin{array}{l} \text{as minimum term to be} \\ \text{added} \therefore 5, 9 \end{array} \right\}$$

$$0 \oplus x = 0'x + 0x' = 1 \cdot x = x$$

$$1 \oplus x = 1'x + 1x' = 0 + x' = x'$$

③ Associative law $\Rightarrow$ Order of operation does not change the outcome or result.

ex: $\rightarrow A + (B + C) = (A + B) + C$
 $A \cdot (B \cdot C) = (A \cdot B) \cdot C$ } Associative law.

④ NAND $\Rightarrow$ Prove $A \uparrow (B \uparrow C) = (A \uparrow B) \uparrow C$

$$\downarrow \quad B' + C' \quad | \quad A' + B' + C' = AB + C'$$

$$A' + (B' + C') = A'(B + C)$$

$$A' + BC$$

$$A' + BC \neq AB + C'$$

Not follow Associative law.

$\therefore$ NAND, NOR does not follow associative law.
 XOR follow Associative property.

Which of the following operation is commutative associative, But not distributive.

- ① AND ② NAND ③ OR ④ XOR

④ XOR $\Rightarrow A \oplus (B \oplus C) = (A \oplus B) \oplus C$

fixed A variable on both sides. (any variable can fix)

	A=0	A=1	B⊙C	
LHS	B⊕C	(B⊕C)'	B⊕C	0⊕x=x
RHS	B⊕C	B'⊕C = (B')'C + B'C'		1⊕x=x'
		= BC + B'C'		
		= B⊙C		0⊙x=x'
				1⊙x=x

$\therefore$ LHS = RHS

XOR, XNOR follows commutative associative law.

$$A \oplus B = A' \odot B = A \odot B' = A' \oplus B'$$

$$A \odot B = A' \oplus B = A \oplus B' = A' \odot B'$$

$$\begin{aligned}
 A' \oplus B' &= (A')' \cdot B' + A' \cdot (B')' \\
 &= AB' + A'B \\
 &= A \oplus B
 \end{aligned}$$

$$A \oplus A = 0$$

1) Which of the following is not equivalent to 2 input ^{XNOR} ~~XOR~~ gate.

(a) $(A \oplus B)' = (A \oplus B)' = (A \oplus B)' = A' \oplus B = A \odot B$

(d)
$$\begin{aligned}
 &[(A' + B)(A + B')] \\
 &= (A' + B' + AB) \\
 &= A \oplus B
 \end{aligned}$$

2) Let p denotes $p = A \oplus B$, what's the value of the expression $p \oplus A \oplus p \oplus A \oplus p \oplus B \oplus A$

- (a) 0 (b) 1 (c) A (d) B

⇒ XOR is commutative & associative.

$$p \oplus p \oplus p \oplus A \oplus A \oplus A \oplus B$$


$$0 \oplus p \oplus 0 \oplus A \oplus B$$

$$0 \oplus A \oplus B \oplus 0 \oplus A \oplus B = 0 \oplus A \oplus A \oplus B \oplus B \oplus 0$$

$$0 \oplus 0 \oplus 0 \oplus 0$$

$$A \oplus A = 0$$

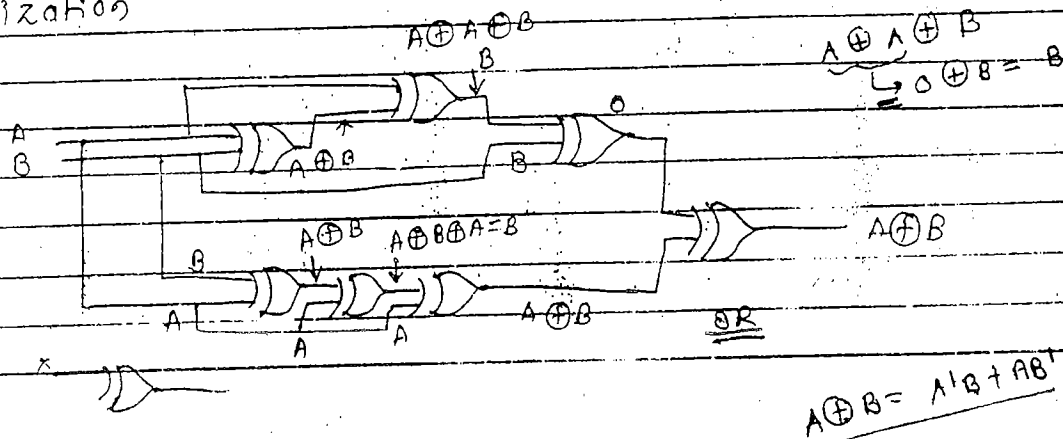3) What was the value given by the following realization



④ ~~Distributive law~~ $\Rightarrow$ This law is exclusively used in the minimisation.

$$A + BC = (A + B) \cdot (A + C)$$

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$$

The distributive law is available in two forms:-

i) Combining law

ii) Absorption law

④ combining law $\Rightarrow$ $AB + AB' = A$
 $(A + B) \cdot (A + B') = A$ ✓

④ Absorption law $\Rightarrow$ $A + AB = A$
 $A \cdot (A + B) = A$

ex: $\rightarrow$
$$\begin{array}{c} (xy + A'B + AB) \\ \underbrace{\quad\quad\quad}_P \quad \underbrace{\quad\quad}_Q \end{array} \quad (A'B + AB)' = A'B + AB'$$

$$\begin{array}{c} (xy + A'B + AB') \\ \underbrace{\quad\quad\quad}_P \quad \underbrace{\quad\quad}_{Q'} \end{array}$$

que.) The simplified SOP expression of the fcn $(P + \bar{Q} + \bar{R})(P + \bar{Q} + R)(P + Q + \bar{R})$

Ⓐ $\bar{P}Q + \bar{R}$ Ⓑ $P + \bar{Q}\bar{R}$ Ⓒ $\bar{P}Q + R$ Ⓓ $PQ + R$

$$\Rightarrow (P + \underbrace{\bar{Q}}_A + \underbrace{\bar{R}}_B) (P + \underbrace{\bar{Q}}_A + \underbrace{R}_C)$$

$$\begin{array}{c} \uparrow \quad \uparrow \quad \uparrow \\ (P + \bar{Q} + \bar{R})(\bar{Q} + R) \\ (P + \bar{Q}) \cdot (P + \bar{Q}R) = \begin{array}{c} \uparrow \quad \uparrow \quad \uparrow \\ (P + \bar{Q}) \quad (P + \bar{Q}R) \end{array} \end{array}$$

OR

$$P + (\bar{Q} + \bar{R}) (\bar{Q} + R) (\bar{Q} + \bar{R})$$

The behaviour of XOR on distributive property

① XOR is not distributive on any other operation including itself.

② No other operation is distributive on XOR except AND operation.

$$\textcircled{i} \quad A \oplus (B \oplus C) = (A \oplus B) \oplus (A \oplus C)$$

$$\textcircled{ii} \quad A + (B \oplus C) = (A + B) \oplus (A + C)$$

$$\textcircled{iii} \quad A \cdot (B \oplus C) = A \oplus AC$$

If in above case $A=1$

$$\star \star \quad \left\{ \begin{array}{l} \text{LHS } (B \oplus C)' = B \odot C \\ B' \oplus C' = B \oplus C \\ A=1 \end{array} \right.$$

$$\text{RHS} = 1$$

$$\text{RHS} = 1 \oplus 1 = 0$$

$$A=0$$

$$\text{LHS} = 0$$

$$\text{RHS} = 0 \oplus 0 = 0$$

$$A=1$$

$$\text{LHS} = B \oplus C$$

$$\text{RHS} = B \oplus C$$

SOP gives NAND-NAND & it represented by A

* De-Morgan's Law *


Special form of complementation

$$A + B = \overline{\overline{A} \cdot \overline{B}}$$

$$AB = \overline{\overline{A} + \overline{B}}$$


- ① NAND $\iff$ Bubbled OR
- ② Any AND-OR realization is repeated with NAND-NAND (SOP)
- ③ Basic realization $\iff$ Universal realization
- ④ Bubbled NAND $\iff$ OR gate

① NAND - NAND

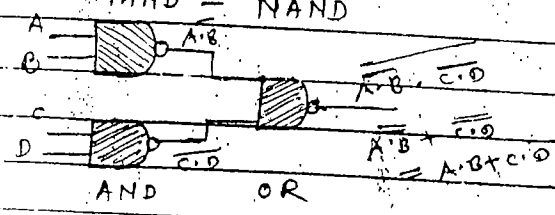


- ① $\overline{AB + CD} = \overline{AB} \cdot \overline{CD}$
- ② $AB + CD$
- ③ $(\overline{A} + \overline{B})(\overline{C} + \overline{D})$
- ④ $(\overline{A}\overline{B}) + (\overline{C}\overline{D})$

② Functions represented by

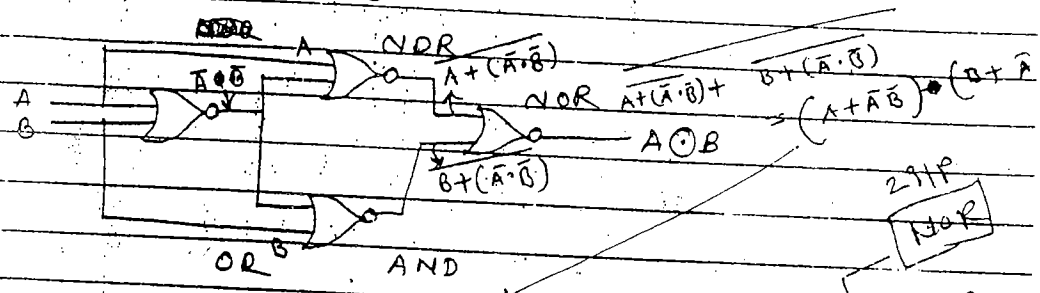
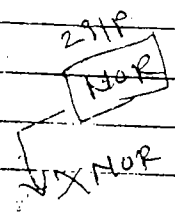
$$\begin{aligned}
 & (\overline{A \cdot B} + A) \cdot (\overline{A \cdot B} + B) \\
 & (A + \overline{A \cdot B}) \cdot (B + \overline{A \cdot B}) \\
 & 1 \cdot (A + B) \cdot 1 \cdot (\overline{A \cdot B}) \\
 & (A + B) \cdot (\overline{A \cdot B}) \\
 & (AB + \overline{A \cdot B})
 \end{aligned}$$




Note $\rightarrow$ Minimum number of 2 input gates required to realize XNOR = 4



$$A(A+B) \\ A+AB = A(1+B) \\ = A \cdot 1 = A$$

Minimum number of 2 input NAND gates required to realize XOR $\Rightarrow 4$


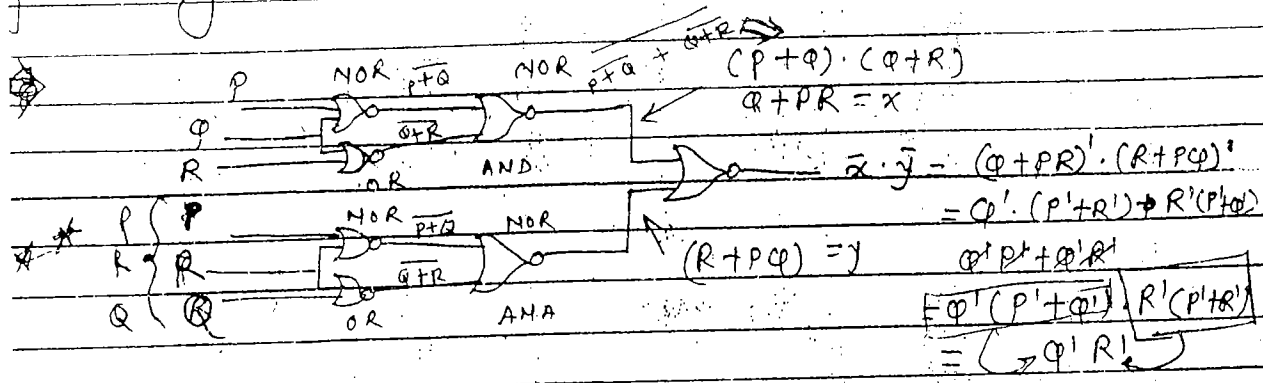
Q What will be the function represented by the following realization?



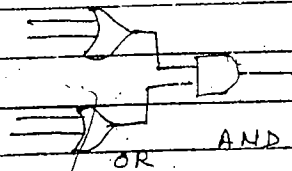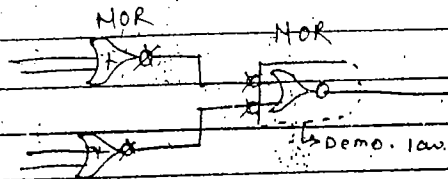How NOR-NOR replaced with OR-AND? $\therefore A(A+B) = A$





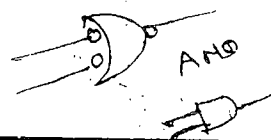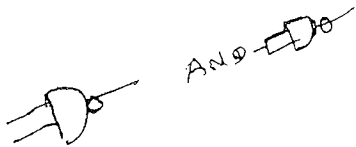Q What will be the minimum no. of two input NAND gates required to realise the following one




(AB)


AND-OR replaced with NAND

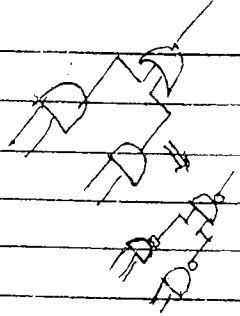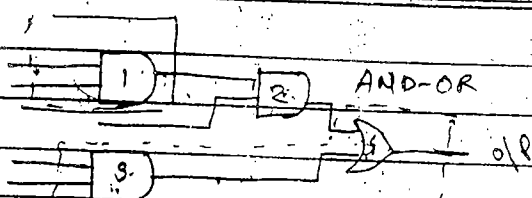


NAND

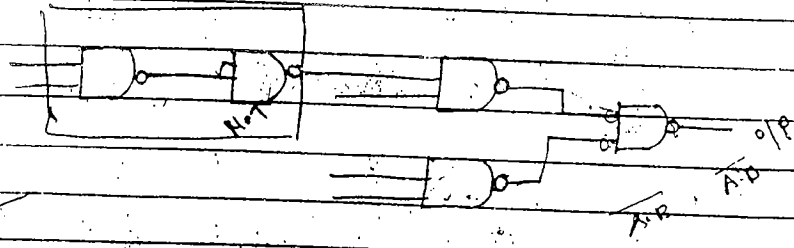

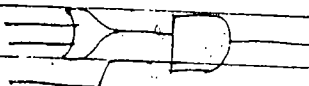
Minimum no. of NOR gates required to realise following



Additional OR gate is required

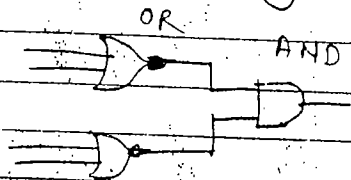



then convert to NOR NOR

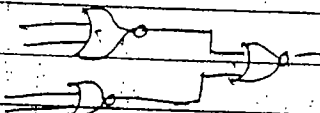


Q. Minimum of 2 i/p NOR gate req. to realise $f(A, B, C) = A + B + C$

$$= (A+B) + C$$

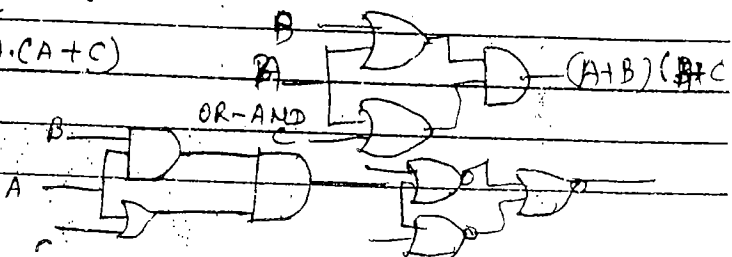

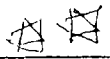


NOR - NOR

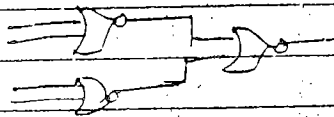

3 NOR gate required to realised it.

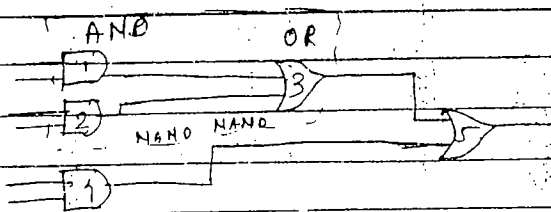Q/ What will be the minimum no. of two i/p
NAND gates required to realised the following
funcn



Ⓐ 4 Ⓑ 5 Ⓒ 6 Ⓓ 7


NAND = Bubble OR

So/ᳵ:

$$\overline{A} \overline{B} = A + B$$


$$\overline{A} \cdot \overline{B} = A + B$$

Bubbled NAND-OR

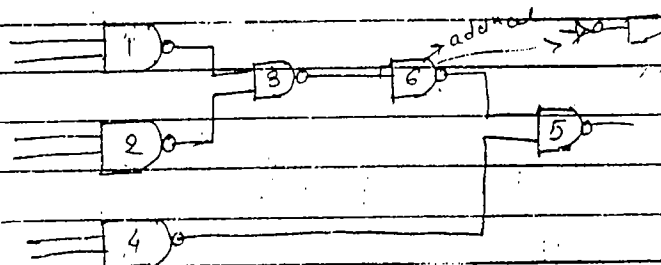

Q. > which of the following can't be used as an inv

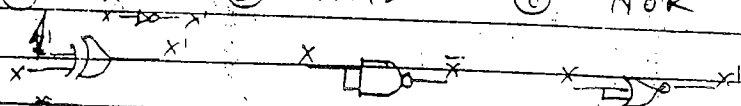- (a) XOR (b) NAND (c) NOR (d) none of above



* Compensation Theorem *

To identify redundant term & remove them.

$$AP_1 + A'P_2 + \underbrace{P_1P_2}_{\text{redundant}} = AP_1 + A'P_2$$

$$(A+P_1) \cdot (A'+P_2) \cdot \underbrace{(P_1+P_2)}_{\text{redundant}} = (A+P_1) \cdot (A'+P_2)$$

$$P_1 \cdot P_2 = 0$$

$$\text{LHS} = \text{RHS}$$

$$P_1 P_2 = 1 \Rightarrow P_1 = P_2 = 1$$

$$\text{LHS: } A + A' + 1 = 1$$

$$\text{RHS: } A + A' = 1$$

As LHS = RHS in both case hence it's redundant

Q. > $(A' + BC)(B' + CA)(C' + AB)$

$$\begin{aligned} &\Rightarrow (A' + B) \cdot (A' + C) \cdot (B' + C) \cdot (B' + A) \cdot (C' + A) \cdot (C' + B) \\ &= (A' + B') \cdot (A' + C) \cdot (B' + C) \cdot (A + C') \cdot (A' + B) \cdot (B + C') \quad \text{redundant} \\ &= (A' + B') \cdot (A' + C') \cdot (A' + C) \cdot (A' + B) \quad \text{from } \{ \text{from } \text{com} \} \\ &= (A' + B'C') \cdot (A' + BC) = \underline{AA' + ABC + A'B'C' + B'C'BA} \\ &= \underline{A'B'C' + ABC} \end{aligned}$$

* Limitations of Boolean Laws

1) The boolean laws ~~unable~~ are able to provide minimization but it is not possible to know which boolean law is to be applied when. If the laws are not substituted in proper order, the expression may end up in expansion form instead of minimization.

2) We are not sure that the final expression is in redundant form or irredundant form. These problems are resolved using k-maps.

* K-Maps *

K-maps provides systematic way of minimization. It denotes the truth table in pictorial form. A k-map of n -variables contains 2^n cells. Each of which is addressed by gray code.

1) The adjacent cells containing minterms or maxterms form prime implicants.

2) A prime implicant can't be subset of another. And it becomes essential if it exclusively covers at least one minterm.
 $\rightarrow$ not share by anybody

3) If a map contains all essential prime implicants then it will have only one minimal form.

4) If none of the prime implicants are essential

(cyclic implicants) the map will have more than one minimal expression.

① If the no. of variables are 6 or more construction of k-maps is difficult & hence minimization also difficult. As an alternative method tabulation method, variableEntered map are used

② The minimal expression also called as "Minimal Cover." It must be minimum & cover all minterms.

Minimal expression = Minimal cover = All Essential + Prime Implicant required to cover remaining minterms, if any.

① $F(A, B, C) = \sum (1, 2, 3, 4, 6)$

C \ AB	00	01	11	10
0	0	1	1	1
1	1	1	1	0

Diagram showing prime implicants: P (01, 11), Q (00, 01), R (01, 11), S (11, 10).

Basic terms

- ① How many prime implicants? $\Rightarrow 4$ i.e. P, Q, R, S (pairs)
- ② How many essential prime implicants? P, S
- ③ How many redundant prime implicant? Q, R
- ④ How many minimal expression?
- ⑤ How many literals?

② $\Rightarrow$ 2 are essential prime implicant P and S.
becoz it contains essential '1' not covered by other.

③ $\Rightarrow$ Q, R are redundant prime implicant. (1, 2, 3, 4, 5)

④ $\Rightarrow$ 2 minimal expressions $P+S+Q$ and $P+S+R$ to cover left.
prime implicant

~~⑤~~ $P+S+Q = A'C + A'C' + A'B$
 $P+S+R = A'C + A'C' + BC'$

⑤ $P+S+Q = \underbrace{A'C}_2 + \underbrace{A'C'}_2 + \underbrace{A'B}_2$, $P+S+R = \underbrace{A'C}_2 + \underbrace{A'C'}_2 + \underbrace{BC'}_2$

No. of literals in SOP is $2+2+2=6$.
though it simplify $A'(B+C) + AC'$ gives literal 5
but we have asked SOP so its 6.

* for above 1 maximization is $\Rightarrow$

$\bar{C}$	AB	00	01	11	10
0		0	2	6	4
1		1	3	7	5

$\nearrow$ p $\nwarrow$ q

① $\Rightarrow$ 2 prime implicants for POS. P & Q

② $\Rightarrow$ 2 prime imp. which is essential

③ $\Rightarrow$ No redundant.

④ $\Rightarrow$ POS have one min. exp.

yz \ wx	00	01	11	10
00		1	1	1
01		1		1
11		1	1	1
10		1		1

⑤ $\Rightarrow$ pos have 5 literals $(A+B+C) \cdot (A'+C')$
3 2

expansion of pos $\Rightarrow (A+B+C) \cdot (A'+C')$
 $= AC' + A'B + BC' + A'C$
compensate OR

$= AC' + A'B + A'C$
 $= AC' + A'B + BC' + A'C$
compensate

POS = $AC' + BC' + A'C = SOP$

① How many minimal expressions possible for following k-map?

yz \ wx	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

- (a) 3
- (b) 4
- (c) 6
- (d) 7

$f(w, x, y, z) = \sum (4, 5, 6, 7, 8, 9, 10, 11, 12, 15)$

prime implicants are 6
 essential prime implicants 2 (quads)
 redundant prime implicants 4 (pairs)

minimal expression $\Rightarrow$ All essential prime implicants + 12 + 15
↓ ↓
to cover to cover
12 A or B



All Essential prime Implicants $+A+B$

$+A+D$

$+B+C$

$+B+D$

$\therefore$ 4 minimal exp.

Literals are $\Rightarrow (2+2+3+3) = 10$

from quad element $\therefore 4-2=2$
 from other $\therefore 4-2=2$

$$w'x + w'x + xy'z' + xyz \quad \rightarrow A+C$$

$$w'x + w'x + xy'z' + wyz \quad \rightarrow A+B$$

$$w'x + w'x + wy'z' + xyz \quad \rightarrow B+C$$

$$w'x + w'x + wy'z' + wyz \quad \rightarrow B+D$$

$$f(w, x, y, z) = \sum (4, 5, 6, 7, 8, 9, 10, 11, 12, 15)$$

$$f(w, x, y, z) = \prod (0, 1, 2, 3, 13, 14)$$

wx \ yz	00	01	11	10
00	0*	4	12	3
01	0	5	13*	9
11	0	7	15	11
10	0	6	14*	10

Annotations: A circle groups the 0s in the first column (yz=00, 01, 11, 10). An arrow points from the top-right corner to the 14 in the bottom row, labeled wx'y.

1 $\Rightarrow$ prime implicants are 3.

2 $\Rightarrow$ essential prime implicants are also 3.

③ $\Rightarrow$ redundant are 0:

④ $\Rightarrow$ minimal expression ~~are~~ is 1

⑤ $\Rightarrow$ Literals are $2+4+4=10$

⑥ $\Rightarrow$ Identify which of the following is not prime implicant?

AB \ CD	00	01	11	10
00	0	4	12	8
01	1*	5	13	9
11	3	7	15	11
10	2	6	14	10

- (a) BD *
- (b) A'C'D
- (c) A'B'C *
- (d) ABD

$\Rightarrow$ prime implicant can't be subset of another & cover minterm.

As ABD is a subset of BD i.e. pair within the quad.

$\therefore$ ABD not prime implicant.

dual of

3) With respect to the number of literals of minimal SOP & POS identify the correct statement.

(a) The number of literals in minimal SOP is 1 more than POS.

(b) The number of literals in minimal SOP is 1 less than POS.

(c) The difference between minimum number of literals in SOP & POS is 2.

(d) The number of literals are equals in both SOP & POS.

→ from que. 2

SOP literals $4 \times 3 = 12$

Prime I. 5 → (4-P, 1-Q)

→ E.P.I. 4 → (4-P)

→ Redunt. $(10) \rightarrow 1 \Rightarrow P.I - E.P.I = 5 - 4 = 1$

→ Exp. literals 1

$$8 \times 3 + 3 \times 3 = 12$$

POS literals $3 \times 4 = 12$

SOP expression of que 2 → $A'C'D + A'BC + ABC' + ACD$
 $(A+C+D)(A+B+C)(A+B+C')(A+C+D)$

POS expression → $AC'D + A'BC + AB+C + ACD$

POS dual of SOP

Essential P.I. check whether term present in k-map

Essential P

Q1. Consider hypothetical map in which E.P.I. are covering all the minterms except 2. Each of the leftover minterm is covered by three different redundant prime implicants. What will be the number of minimal expressions denoted by this map?

- (a) 3 (b) 6 (c) 9 (d) 12

Ans. $\Rightarrow$ minimal cover = All E.P.I. + $\underbrace{P+Q+R}_{m_1} + \underbrace{S+T+U}_{m_2}$

$$P+S \quad Q+S \quad R+S$$

$$P+Q+T \quad Q+T \quad R+T$$

$$P+U \quad Q+U \quad R+U$$

Q2. Which of the following is not represented by k-map?

E.P.I.

	yz \ wx	00	01	1	10
00	0	1	1	1	1
01	1	1	1	1	1
11	3	1	1	1	1
10	2	1	1	1	1

Annotations: $W\bar{y}\bar{z}$ (covering 00, 01), P (covering 01, 1, 10), R (covering 1, 10, 11), Q (covering 1, 11, 10), $g+wx$ (covering 1, 10, 11, 10).

(a) $w'y'z' + xy'z + w'yz + \underline{wx'y}$ $\rightarrow$ E.P.I. 5 $\rightarrow g+wx$

(b) $w'y'z' + wx'y + w'xy' + \underline{wxz}$

(c) $w'x'y + xy'z + w'yz + \underline{wxz}$ $\rightarrow$ as essential prime implicant is missing

hence not 1

k-map

Q. What will be the no. of minimal exp. represented by above map?

- ☒ (a) 3
 ☐ (b) 4
 ☐ (c) 5
 ☐ (d) 6

$\Rightarrow$ $ESR + P + R$
 $ESR + Q + R$
 $ESR + Q + S$

} Minimality should be protected & not violated.

Q. A three variable function $f(A, B, C)$ is minimised as $f(A, B, C) = A + BC$. The minterms of f are 3, 5, 6.

Which of following don't cares (X) are used in the minimisation?

- ☐ (a) $\sum_{\phi} (2, 7)$
 ☒ (b) $\sum_{\phi} (4, 7)$
 ☐ (c) $\sum_{\phi} (2, 4, 7)$
 ☐ (d) $\sum_{\phi} (2, 4)$

$\Rightarrow$

	AB	00	01	11	10
C	0	0	2	1	6
1	1	3	ϕ	7	5

BC ← → A

Q. What will be the values of don't cares P, Q, R of the k-map is minimised?

$\Rightarrow$

	00	01	11	10
00	0	Q	P	0
01	0	1	1	1
11	1	1	1	1
10	R	0	0	0

P, Q, R
(a) 0 0 0
(b) 1 0 0
(c) 1 1 0
(d) 1 1 1

As octal is happens with POS all are 0.

Q. The funcⁿ represented by following k-map is for
from - (a) 1 variable, (b) 2 variables (c) 3 variables
(d) dependent on all

yz \ wx	00	01	11	10
00	0	1	1	0
01	1	0	0	1
11	1	0	0	1
10	0	1	1	0

$x'z$ $x'z + xz'$
 xz'

Application on k-maps

Let, $A \oplus B = A' + B$ what will be the expression denot
by $f_1 \oplus f_2$.

R \ PQ	00	01	11	10
0	0	1	0	0
1	1	0	1	0

f_1

R \ PQ	00	01	11	10
0	0	1	1	0
1	1	0	0	1

f_2


$$f_1(A, B, C) = \sum (0, 1, 7) + \sum_{\phi} (2, 4)$$

$$f_2(A, B, C) = \sum (1, 2, 3, 6) + \sum_{\phi} (0)$$

① $f_1 + f_2 = ?$

② $f_1 f_2 = ?$

~~Q2 = 40-10~~

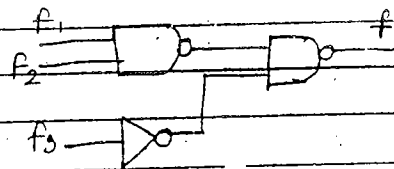

③ $f_1(x, y, z) = \Sigma(0, 1, 3, 5)$

$f_2(x, y, z) = \Sigma(1, 6, 7)$

$f(x, y, z) = \Sigma(1, 4, 5)$

$f_3 = ?$

Soln

$A \# B = A' + B$

$\Rightarrow A \# B = 0$

if $A' = 0$ & $B = 0$
($A = 1$)

where 1st var is 1 &
2nd var is 0 then
B obtain

else $A \# B = 1$

$A = 1, B = 0 \Rightarrow 0$

else 1

R	P	Q	00	01	10	11
0	0	0	1	1	1	1
0	0	1	1	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1

$\therefore f_1 \# f_2 = (A' + B' + R')$

A	B	f0	f1	f2	f6	f14	f15
0	0	0	0	0	0	1	1
0	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1
1	1	0	1	0	0	0	1
		↓	↓	↓		↑	↑
		NULL	AND	OR		NAND	Tautology

$$f_1 = \sum (0, 1, 7) + \sum_{\phi} (2, 4)$$

$$f_2 = \sum (1, 2, 3, 6) + \sum_{\phi} (0)$$

① $\Rightarrow \phi + 0 = \phi$ — (a)
 maxterm

The term must be in ϕ list of one function & max of another function for OR operation + it's in don't care list.

② $\phi \cdot \phi = \phi$ — (b)
 minterm

The term must be in ϕ list of one function & minterm of another function for AND.

$\therefore$ from case (a)

$$f_1 + f_2 = \sum (0, 1, 2, 3, 6, 7) + \sum_{\phi} (4)$$

from case (b)


$$f_1 f_2 = \sum (1) + \sum_{\phi} (0, 2)$$

$\phi \cdot 1 = 0$
 $\phi \cdot 1 = 0$
 $\phi \cdot 1 = 0$
 don't care

ex: $\rightarrow$

C	AB	00	01	11	10
0		1	1	1	0
1		1	1	1	0

$f_1 + f_2 = A' + B$

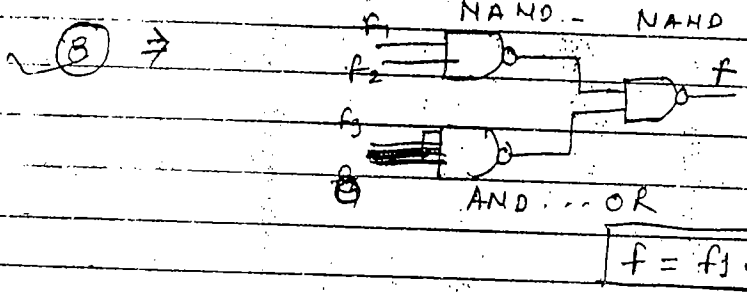

$$f_1 \cdot f_2 = \sum (1), f = \sum (1, 4, 5)$$

$$f_3 \leftarrow \sum (1, 4, 5)$$

$$\sum (4, 5)$$

by formula $f = \sum(1) + \sum(1, 4, 5) = \sum(0, 4, 5)$
 $f = \sum(1) + \sum(4, 5) = \sum(2, 4, 5)$

It is required to realise a function within basic gates (AND, OR) the only constraint is the realisation used only one inverter with respect to the following k-map identify the correct statement.

xz \ wx	00	01	11	10
00	0	1	1	0
01	1	0	0	1
11	1	0	0	1
10	0	1	1	0

$f_1 = xz' + x'z \Rightarrow$


xz \ wx	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	0	0	1	0
10	0	0	1	0

$f_2 = x'y' \Rightarrow xy$
 $(x+y)' = xy$


- (a) only f_1 is realisable.
- (b) only f_2 is realisable.
- (c) Both f_1 & f_2 are realisable.
- (d) Neither f_1 nor f_2 are realisable.

$\Rightarrow$

$f_2 = xy$

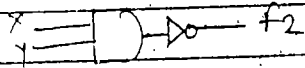

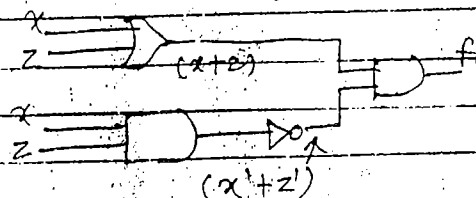$f_1 = xz' + x'z$
 $= (x+z) \cdot (x'+z')$
 $(xz)'$



Q. Consider the following three 3-variable fun.

⑤. $f_1(A, B, C) = \sum (0, 1, 3)$

⑥. $f_2(A, B, C) = \sum (3, 5, 7)$

⑦. $f_3(A, B, C) = \sum (1, 3, 7)$

In the simplification it was found there are 4 prime implicants P, Q, R, S (all are pairs).
 The prime implicant P is common to f_1 & f_3 and Q is common to f_2 & f_3 . What will be the expressions for prime implicants Q, R, S?
 R is the prime implicant of f_2 while S is prime implicant of f_1

⇒

	AB			
C	00	01	11	10
0	1	0	0	0
1	1	1	0	0

$f_1 = A'B' + A'C$

	AB			
C	00	01	11	10
0	0	0	1	1
1	1	1	1	1

$f_2 = BC + A$

	AB			
C	00	01	11	10
0	0	0	0	1
1	1	1	1	1

$f_3 = A'C + BC$

P Q R S
 A'C BC A'C A'B'

★ The more the number of variables then it more difficult to construct prime implicant.

one bit bin & gray are same

(A)

Simplify following 5-variable k-map

		ABC				ABC			
		A=0				A=1			
DE	BC	00	01	11	10	00	01	11	10
00		1				1			
01			1	1			1	1	
11									
10		1				1			

Gray codes $\rightarrow$ Unit distance, cyclic, self reflection
 Quad $\rightarrow$ after fold coincide & address = 15-16=31
 Pair $\rightarrow$

0	0	0	↑
1	0	1	↑
	1	1	↓
	1	0	↓

2-bit gray code

0	0	0
0	0	1
0	1	1
0	1	0
1	1	0
1	1	1
1	0	1
1	0	0

3-bit

$$f(A, B, C, D, E) = \sum (0, 2, 8, 10, 13, 16, 18, 21, 24, 26, 29, 31)$$

Octet = CE
 Quad = CD'E
 Pair = ABCE

VEM

VEM (Variable Entered Map)

① It's capable of representing higher variable function in a lesser variable map.

c \ AB	00	01	11	10
0	1	1	0	0
1	0	0	0	0

$f(A, B, C, D)$

① Here the contents of cells can be variables.

* Procedure for Minimisation *

Step 1 $\Rightarrow$ Make all the variables in the cell as 0
construct SOP. Zero

Step 2 $\Rightarrow$ Minterm(1)

(a) Make one variable high at a time & obtain SOP treating earlier ~~minterms~~ ^{Minterms} as don't care.

(b) Multiply above SOP with the concerned variable.

Step 3 $\Rightarrow$ Repeat the step 2 until all the variables in cell are covered.

Step 4 $\Rightarrow$ SOP of VEM is obtained by ORing previous 3

①

Step 1 $\Rightarrow$

c \ AB	00	01	11	10
0	1	1	0	0
1	1	1	0	1

c \ AB	00	01	11	10
0	0	1	0	0
1	0	1	0	1

$$SOP = \bar{A}B$$

Step 2 $\Rightarrow$ consider 0 as high

c \ AB	00	01	11	10
0	1	0	0	0
1	1	0	0	1

$$SOP = \bar{A}$$

Step 2 (b) $\Rightarrow$ As we considered 0 $\therefore$ $SOP = \bar{A} \cdot \bar{D}$

Step 2 (c) for $\bar{D}$

c \ AB	00	01	11	10
0	0	0	0	0
1	0	0	0	1

$$SOP = AC$$

Step 2 (d) for $\bar{D} \Rightarrow SOP = AC \cdot \bar{D}$

$$\therefore f(A, B, C, D) = \bar{A} \cdot \bar{D} + AC \bar{D} + \bar{A}B$$

$$= \Sigma (1, 3, 4, 5, 6, 7, 10, 14)$$

	A	B	C	D	
$\bar{A} \cdot \bar{D} \rightarrow$	0	0	0	1	1, 3, 5, 7
$AC \bar{D} \rightarrow$	1	0	1	0	10, 14
$\bar{A}B \rightarrow$	0	1	0	0	4, 5, 6, 7

② Ans: $f(A, B, C, D) = \bar{B}C + \bar{C}D + C\bar{D}$

✓
Right
Correct

Q2

B \ AC	00	01	11	10
0	0	1	1	0
1	0	0	0	0

→ Step 1 →

B \ AC	00	01	11	10
0	0	1	1	0
1	0	0	0	0

$f = \bar{B}C$

Step 2 → consider 0 as high

B \ AC	00	01	11	10
0	1	0	0	1
1	0	0	0	0

$f = \bar{B}\bar{D}$


Step 2 (b) $f = \bar{B} \cdot D$

Step 2 (a) → consider $\bar{D}$ as high

B \ AC	00	01	11	10
0	0	0	0	1
1	0	1	1	0

$f = C$

Step 2 (b) → $f = C \cdot \bar{D}$

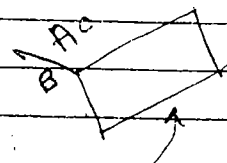

$f(A, B, C, D) = B'C + B'D + CD$

✓
Correct

A	B	C	D
0	0	1	0
0	0	0	1
0	0	1	0

8'c (6, 11)
8'd (4, 11)
c d' (2, 6)

$$A \oplus B = \bar{A}B + A\bar{B}$$

$$A \odot B = \bar{A}\bar{B} + AB$$

P.81

D/C	0	1
0	$A \oplus B$	0
1	0	$A \odot B$

$$(A+B)\bar{C}\bar{D} + (A \odot B)C\bar{D}$$

$$(\bar{A}B + AB)\bar{C}\bar{D} + (\bar{A}\bar{B} + AB)C\bar{D}$$

$$\Rightarrow \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + AB\bar{C}D$$

$$\Sigma(0, 4, 3, 15)$$

P.42 Consider the following 3-variable function $f(A, B, C) = \Sigma(0, 1, 2, 4, 5, 7)$ is realised by the following VEM: What could be the values of P, Q, R, S.

$$\Rightarrow f(A, B, C) = \Sigma(0, 1, 2, 4, 5, 7)$$

$$= \bar{A}'\bar{B}'C' + \bar{A}'B'C' + \bar{A}'BC' + \bar{A}B'C' + \bar{A}BC' + \bar{A}BC$$

B \ A	0	1
0	P	Q
1	Q	S

$$= \bar{A}\bar{B} \cdot P + \bar{A}B \cdot Q + \bar{A}B \cdot R + \bar{A}B \cdot S$$

$$P = C' + C = 1$$

$$P = 1$$

$$Q = C'$$

$$S = C$$

B \ A	0	1
0	1	R
1	Q	S

$$Q = C'$$

$$R = C' + C = 1$$

$$S = C$$

B \ A	0	1
0	1	1
1	C'	C

Apply VEM

Redundant

Step 1 $\Rightarrow$

B \ A	0	1
0	0	1
1	0	0

$f = B'$

Step 2 (a) $\rightarrow$ make c as high

B \ A	0	1
0	ϕ	ϕ
1	c'	1

$f = A$

(b) $\rightarrow f = AC$

Step 3 (a) $\rightarrow$ make c' as high

B \ A	0	1
0	ϕ	ϕ
1	1	c

(b) $\rightarrow f = A'c'$ $f = A'$

$f = B' + AC + A'c'$

$A B C$
 $\bar{A} \phi 0 \phi$
 $\{0, 1, 4, 5\}$

$\bar{A} \bar{C} 0 \phi 0$
 $\{0, 2\}$

$AC A B C$
 $1 \phi 1$
 $\{5, 7\}$

Time Complexity
 $O(2^n)$

* Tabulation Method *

This method is used to generate all possible minimal expressions & prime implicants. The time complexity of tabulation process $O(2^n)$ (exponential time complexity).

Procedure for minimisation →

Step 1 → Rearrange the minterms according to the number of 1's in its binary pattern.

ex → the min-term 8 is placed in group 1.
while 7 is placed in group 3.

8(1000)₂ → G₁ G₁

7(111)₂ → G₃ G₃

② Match the minterms of adjacent groups which are at unit distance & form the new group.

③ Repeat the step ② exhaustively until no further new groups are possible.

④ Use the implication chart & extract all minimal expressions.

Distance = no. 0-1 pair

① $f(A, B, C, D) = \sum (0, 1, 2, 4, 8, 12, 14, 15)$

⇒ step 1 ⇒

0 0 0 0	(0)	→	ϕ_1
0 0 0 1	(1)	✓	
0 0 1 0	(2)	} → ϕ_1	
0 1 0 0	(4)		
1 0 0 0	(8)		
1 1 0 0	(12)	→	ϕ_2
1 1 1 0	(14)	→	ϕ_3
1 1 1 1	(15)	→	ϕ_4

0 0 0 0	(0, 1)	P	$\phi_1 \phi_1$	Ⓟ
0 0 0 1	(0, 2)	Q	$\phi_1 \phi_2$	Ⓠ
0 0 1 0	(0, 4)		$\phi_1 \phi_4$	✓
0 1 0 0	(0, 8)		$\phi_1 \phi_8$	✓
1 0 0 0	(4, 12)		$\phi_4 \phi_{12}$	✓
1 1 0 0	(8, 12)		$\phi_8 \phi_{12}$	✓
1 1 1 0	(12, 14)	R	$\phi_{12} \phi_{14}$	Ⓡ
1 1 1 1	(14, 15)	S	$\phi_{14} \phi_{15}$	Ⓢ

- - 0 0 (0, 4, 8, 12) T ϕ_{0123} ✓ Ⓣ

Nothing (ϕ) ϕ_{0123}

ϕ ϕ_{234}

The (✓) are not valid prime implicant. P, Q, R, S are prime implicant & they form pair.
T form the quad.

Implicant chart

Prime Implicants	0	1	2	4	8	12	14	15
* P	✓	≡						
* Q	✓		✓					
R						✓	✓	
* S							✓	✓
* T	✓		✓	✓	✓			

When one tick (✓) in column is essential P. Implic.

minimal exp. = All essent + other

$$\Sigma (0, 1, 3, 4, 8, 12, 14, 15)$$

∴ one ~~intermed~~ minimal exp only $P + Q + S + T$

$$P + Q + S + T = A'B'C' + A'B'D' + ABC + CD'$$

② Using tabulation method minimize the following
 $F(A, B, C, D, E) = \Sigma (0, 2, 5, 8, 10, 13, 16, 18, 24, 26)$

0 0 0 0 0 (0) ϕ_0	0 0 0 0 0 (0, 2) ✓	0 1 0 1 0 (0, 2)
0 0 0 1 0 (2)	0 0 0 0 0 (0, 8) ✓	0 1 0 0 0 (0, 8)
0 0 0 0 0 (8) ϕ_1	0 0 0 0 0 (0, 16) ✓	0 1 0 0 0 (0, 16)
1 0 0 0 0 (16)	0 0 1 0 0 (2, 10) ✓	0 0 1 0 0 (2, 18)
0 0 1 0 1 (5)	0 0 1 0 0 (2, 18)	0 1 0 0 0 (8, 10) ✓
0 1 0 1 0 (10) ϕ_2	0 1 0 0 0 (8, 10) ✓	1 0 0 0 0 (8, 24) ✓
1 0 0 1 0 (18)	1 0 0 0 0 (8, 24) ✓	1 0 0 0 0 (16, 18) ✓
1 0 0 1 0 (18)	1 0 0 0 0 (16, 18) ✓	1 0 0 0 0 (16, 24) ✓
1 1 0 0 0 (24)	1 0 0 0 0 (16, 24) ✓	0 1 0 1 0 (5, 13) ✓
1 1 0 1 0 (26) ϕ_3	0 1 0 1 0 (5, 13) ✓	0 1 0 1 0 (10, 26) ✓
0 1 1 0 1 (13) ϕ	1 0 0 1 0 (10, 26) ✓	1 0 0 1 0 (18, 26) ✓
	1 0 0 1 0 (18, 26) ✓	1 1 0 0 0 (24, 26) ✓

Higher value in group ≠ lower value in high group
 $\therefore \phi_8 \neq \phi_5 \phi_2$

$$\begin{array}{l}
 0 - 0 - 0 \quad (0, 2, 8, 10) \checkmark \\
 - 0 0 - 0 \quad (0, 2, 16, 18) \\
 - - 0 0 0 \quad (0, 8, 16, 24) \\
 - 1 0 - 0 \quad (8, 10, 24, 26) \\
 1 - 0 - 0 \quad (16, 18, 24, 26) \checkmark \\
 - - 0 1 0 \quad (2, 10, 18, 26)
 \end{array}
 \left. \begin{array}{l} \\ \\ \\ \\ \\ \end{array} \right\} \begin{array}{l} \\ \\ \\ \\ \end{array}$$

$$\begin{array}{l}
 0 \quad 2 \quad 8 \quad 10 \quad 16 \quad 18 \quad 24 \quad 26 \\
 - - 0 - 0 \quad (0, 2, 8, 10, 16, 18, 24, 26) \rightarrow \phi \\
 \text{~~~~~} \quad \quad \quad 12, 14, 16, 18, 24, 26
 \end{array}$$

	0	2	5	8	10	13	16	18	24	26
*P			≤			≤				
*Q	≤	≤		≤	≤		≤	≤	≤	≤

Both prime implicant are essential & hence single mint

$$A'C'D'E + C'E'$$

$$P + Q \Rightarrow A'C'D'E + C'E'$$

Reduction of Implication Charts

① The implication chart is reduced by ~~reg~~ retaining the dominant rows & removing the dominant columns.

② A row P is said to be dominating Q if it covers all the minterms of Q in addition it having some more minterms. ($Q \subset P$)

③ The tickmark ($\checkmark$) concept in tabulation process is to care about row dominance.

The reduction process has reduced two prime implicants and 5 minterms. Further between m_6 & m_7 only 1 of them can be retain as both of them covered by same prime implicant.

PTM	m_1	m_2	m_3	m_4	m_5	m_6	m_7	m_8	m_9
PCs ϕ	✓		✓					✓	✓
Q		✓	✓					✓	✓
R	✓		✓	✓	✓			✓	
S					✓	✓	✓	✓	
T	✓	✓							✓
UC ϕ $\cup$		✓							✓

$$P + \cancel{Q} + R + S + T + \cancel{V}$$

	m_4	m_6	m_9
*Q			✓
*R	✓		
*S		✓	
T			


$\therefore$ all min terms are canceled by above Q, R, S
 $\therefore$ contains 1 min term as $Q + R + S$

Hazards

* Hazards *


- ① Hazards - malfunction of digital circuits
- ② Temporary hazards are resulted due to uneven delay of input signals.
- ③ Permanent hazards results due to open circuit & short circuit of connecting leads.
- ④ Test vector:- subset of combinations that influence the path.
- ⑤ ~~Family~~ ^{Fault} path:- If the digital circuit given wrong out for each element in the Test vector it is declared fault path.
- ⑥ Path Sensitization Technique:- It's used to construct Test Vector for the chosen path.

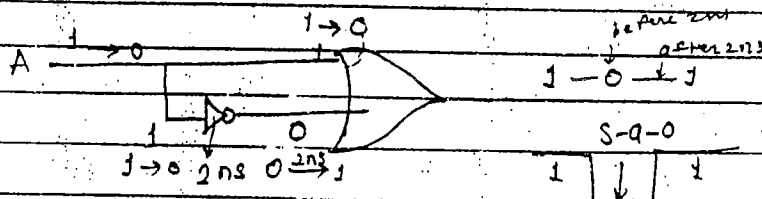- Procedure:-
- ① To activate all other paths except the tested one. (For AND/NAND are use '1' for activation)
 - ② Apply opposite logic level at tested place.
 - ③ All the input binary patterns satisfy above form test vector.



Stuck-at-zero (S-a-0) for short time & recoverable.

Stuck-at-one (S-a-1)

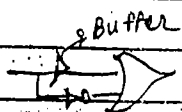




By introducing Buffer (approx. delay at approx. i/p) are the hazards

one part take i/p quickly & other after sometime then it having hazard.


which of exp. having hazards & which not have?

$$x'y' + xz', x'y' + x'z' + xy + xz, xy' + yz'$$

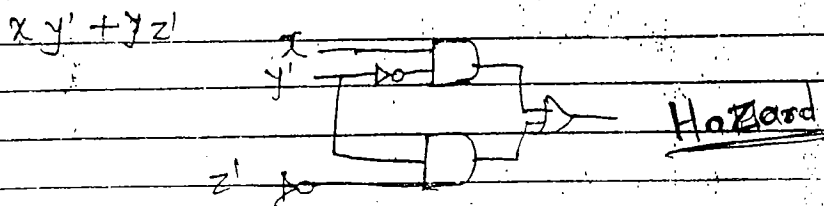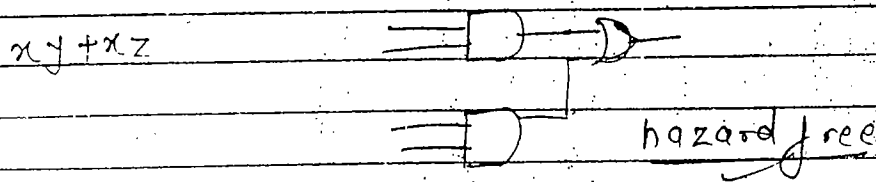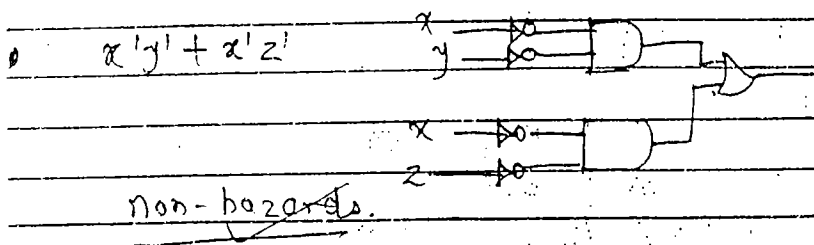
→ $x'y' + xz' \rightarrow (s-a-o)$ Hazard



Permanent Hazards $\Rightarrow$

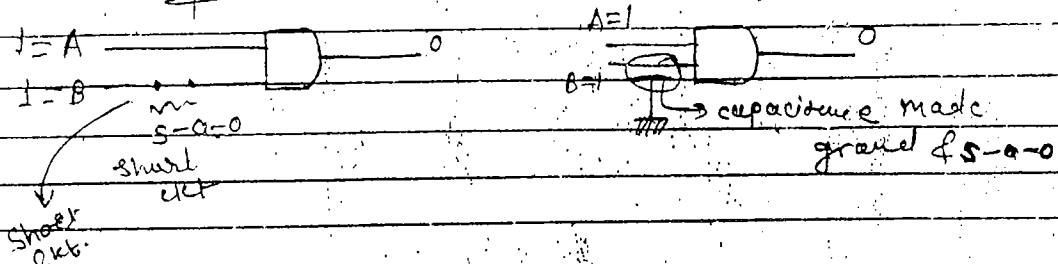


z-cohavi book for Hazards

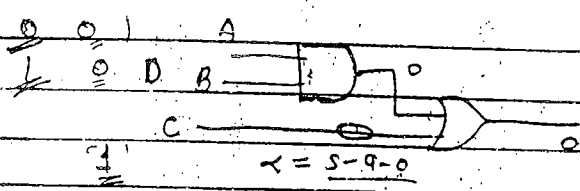

{ 011, 001, 101 }
3, 1, 5


if we get 0 ans after given 1, 3, 5
i/p then it is s-a-o hazard.

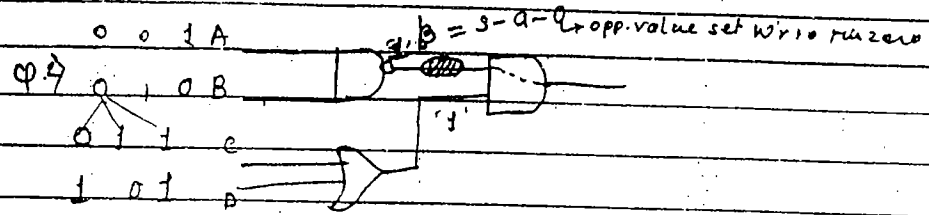Step 1 →
For AND/NAND are 1
for OR are 0
A = 1
B = 0
AB = 0
A? = 1




{ 0001, 0010, 0011, 0101, 0110, 0111, 1001, 1010, 1011 }
{ 1, 2, 3, 5, 6, 7, 9, 10, 11 }

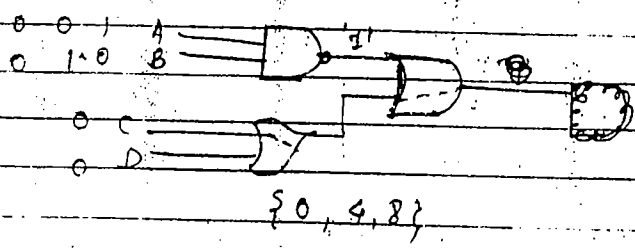8) for above construct s-a-1 test vector for input c




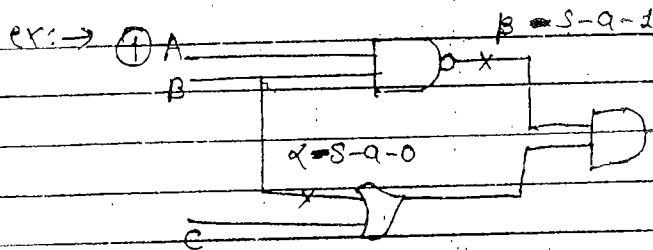**** Limitations of path Sensitization Technique :-**
The path sensitization technique is not capable of providing the test vector if there is a conflicting requirement on any specific input.





- ① Test vector is possible only for $\alpha-s-a-0$
- ② Test vector is possible only for $\beta-s-a-1$
- ③ Test vector is not possible for both
- ④ possible for both.

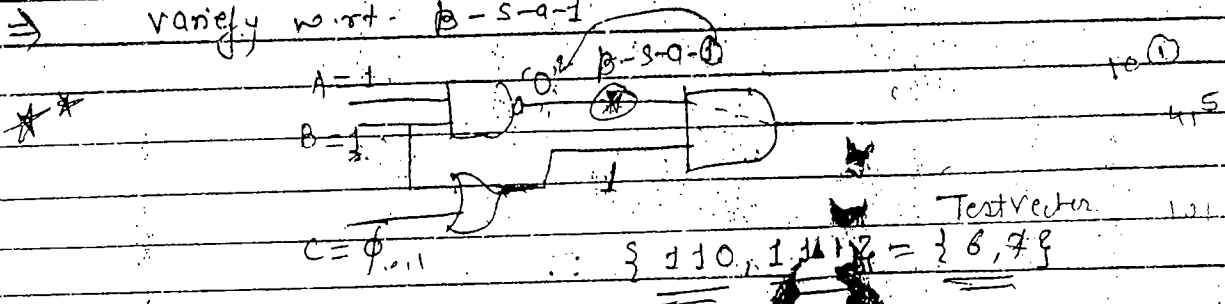$\Rightarrow$ verify w.r.t. $\beta-s-a-1$



verify w.r.t. $\alpha-s-a-0$

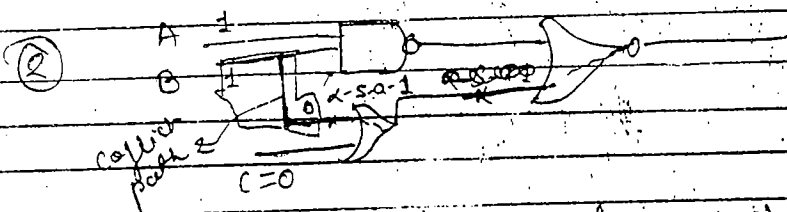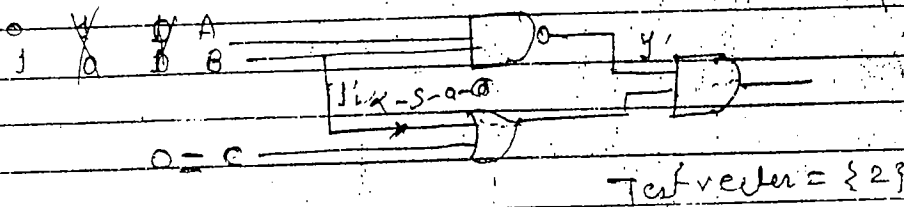

$\therefore$ B requires both 0 & 1 which are conflict req.
 $\therefore$ Test vector is not possible with path sensitization technique.


MSI Circuits

(Medium Scale Integrated ckt.)

Multiplexer	Data Selector	Many to one	8x1 2 i/p, 1
Demultiplexer	Data Distributor	one to many	1x16 3 i/p, 16
Decoder	Address selection	some to many	3x8 3 i/p, 8
Encoder	Interrupt Servicing (Decimal to Binary Conversion)	Many to some	4x2 2 i/p,

	gate Count
SSI	<10
MSI	>10 < 100
LSI	>100 < 1000
VLSI	>1000

4x1 Multiplexer


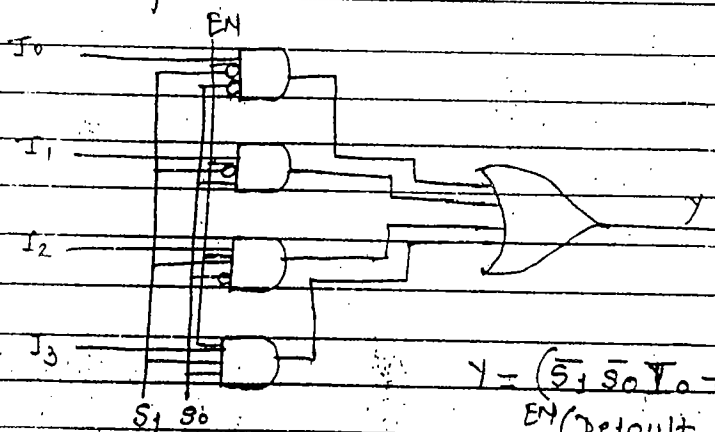


EN	S1	S0	Y
1	0	0	I0
1	0	1	I1
1	1	0	I2
1	1	1	I3
0	φ	φ	φ


$$Y = (\bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3)$$

EN (Default EN=1)

Mux is functionally complete operation.

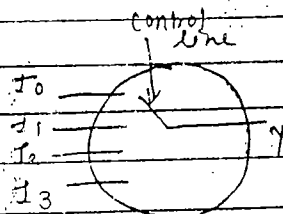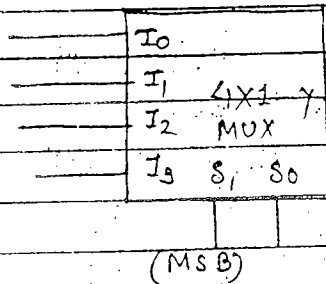

① Mux represent any funcn in SOP form.

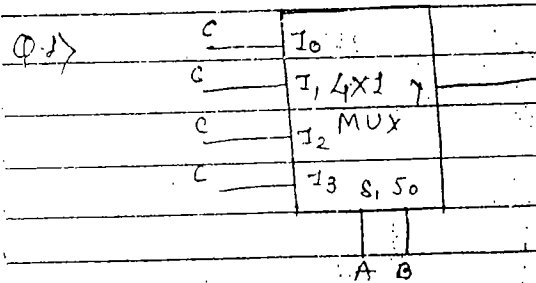

$F(A, B, C)$ is free from?

- ☒ a) C
 ☒ b) A, B
☐ c) A, C
☒ d) A, B, C

$$\begin{aligned}
 \Rightarrow Y &= (\bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB) \cdot C \\
 &= (\bar{A} + A) \cdot C \\
 &= C
 \end{aligned}$$


$\therefore$ free from = A, B

2005

$z=0$

$xy=0$

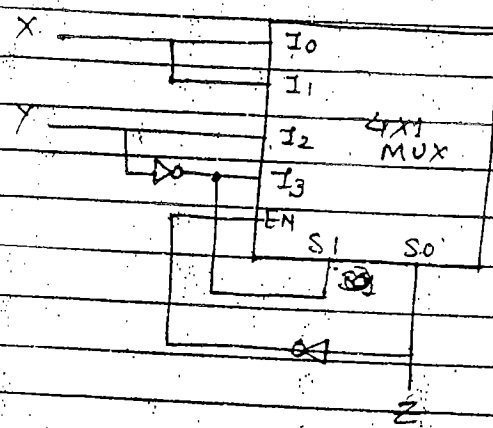Q find the funcn represented by following multiplex



- (a) xyz
- (b) $\bar{x} + \bar{y} + z$
- (c) xyz
- (d) $xy + yz + xz$

$EN (\bar{S}_0 \bar{S}_1 \bar{I}_0 + \bar{S}_0 S_1 I_1 + S_0 \bar{S}_1 \bar{I}_2 + S_0 S_1 I_3)$

$S_1 = \bar{Y}, S_0 = Z, I_0 = X, I_1 = Y, I_2 = Y, I_3 = \bar{Y}$


Q Z should be '0' only otherwise it will make EN & Mux can't be worked. i.e.

	S_1	S_0
ϕ	0	
{	0	0 I_0
	1	0 I_1

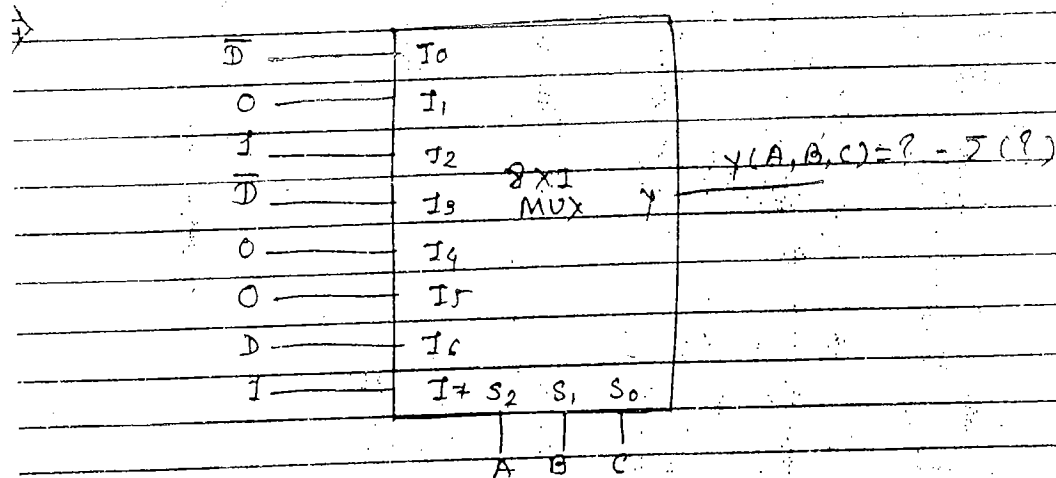Q2

$\bar{Z} (Y\bar{Z}X + Z\bar{Y}X + Z\bar{Y}Y + Z\bar{Y}\bar{Y}) = XY\bar{Z}$

Q) What is the function represented by following MUX?



a) $\Sigma(1, 4, 5, 7, 12, 13, 14, 15)$

b) $\Sigma(0, 4, 5, 6, 13, 14, 15)$


c) $\Sigma(0, 4, 5, 13, 14, 15)$

d) $\Sigma(0, 1, 3, 4, 5, 14, 15)$

S_0	S_1	S_2				A	B	C	D
0	0	0	I_0	$\overline{A}\overline{B}\overline{C}\overline{D} \rightarrow \{0\}$		0	0	0	0
0	0	1	I_1	$\overline{A}\overline{B}\overline{C}D \rightarrow \{4\}$		0	0	1	0
0	1	0	I_2	$\overline{A}\overline{B}C\overline{D} \rightarrow \{5\}$		0	1	0	0
0	1	1	I_3	$\overline{A}\overline{B}CD \rightarrow \{6\}$		0	1	1	0
1	0	0	I_4	$A\overline{B}\overline{C}\overline{D} \rightarrow \{1\}$		1	0	0	0
1	0	1	I_5	$A\overline{B}\overline{C}D \rightarrow \{5\}$		1	0	1	0
1	1	0	I_6	$A\overline{B}C\overline{D} \rightarrow \{3\}$		1	1	0	0
1	1	1	I_7	$ABC\overline{D} \rightarrow \{7\}$		1	1	1	0


$$f = \overline{S_2}\overline{S_1}\overline{S_0}I_0 + \overline{S_2}\overline{S_1}S_0I_1 + \overline{S_2}S_1\overline{S_0}I_2 + \overline{S_2}S_1S_0I_3 + S_2\overline{S_1}\overline{S_0}I_4 + S_2\overline{S_1}S_0I_5 + S_2S_1\overline{S_0}I_6 + S_2S_1S_0I_7$$

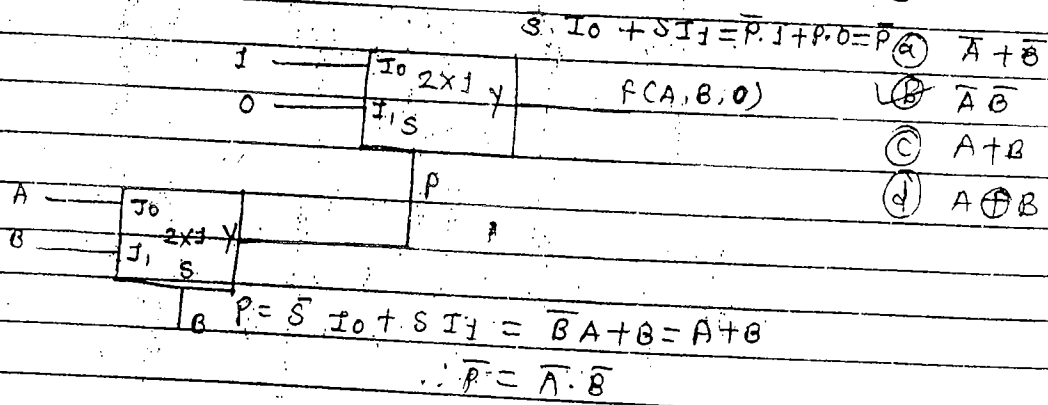④ Identify the function represented by following MUX combination.



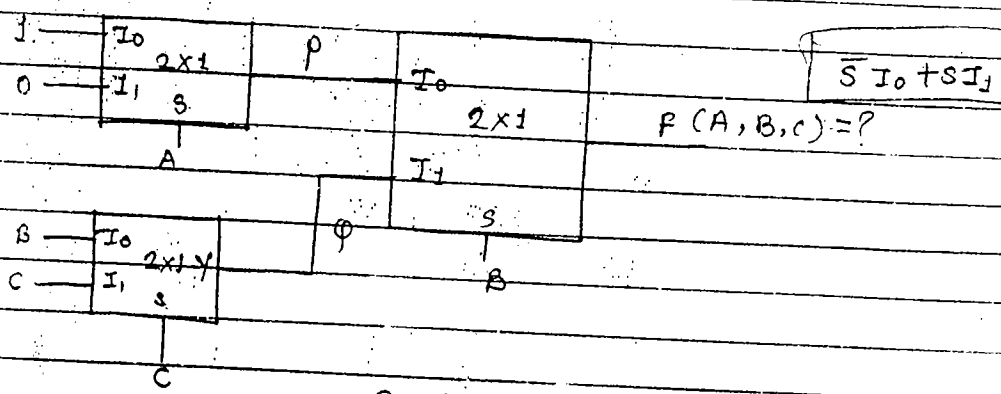- (a) $A + B$
- (b) $\bar{A} \bar{B}$
- (c) $A + B$
- (d) $A \oplus B$

⑤ What's the function represented by following MUX block?



$P = \bar{A}$

$\phi = 0$

$\therefore \bar{B} P + B \phi$

$\bar{B} (\bar{A}) + B (0)$


$= \bar{B} \bar{A} + 0$

$= \bar{A} \bar{B}$

$= \sum (0, 1, 2, 3, 6, 7)$

A	B	
0	0	
0	1	
1	0	
1	1	

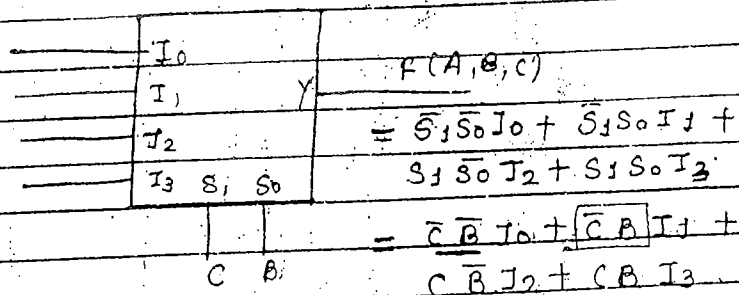4) Consider a 3 variable function $f(A, B, C) = \sum(0, 2, 3, 4, 7)$ is to be realised by the following 4×1 Mux. The select lines S_1 is given as C & S_0 given as B . What could be connections for inputs?



$$F(A, B, C) = \sum(0, 2, 3, 4, 7)$$

$$= \bar{A} \bar{B} \bar{C} + \bar{A} B \bar{C} + \bar{A} B C + A \bar{B} \bar{C} + A B C$$

$$= \bar{C} \bar{B} \bar{A} + \bar{C} B \bar{A} + C B \bar{A} + \bar{C} B A + C B A$$


$$\therefore I_0 = \bar{A} + \bar{A} = 1$$

$$I_1 = \bar{A}$$

$$I_2 = 0$$

$$I_3 = 1 = A + \bar{A}$$

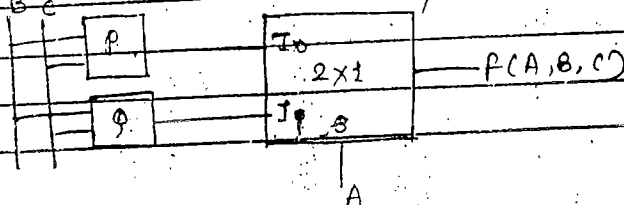5) A majority function is the one in which number of 1 inputs are more than number of 0 inputs. If the majority function of 3 variables is represented by following realisation what will be the functions denoted by P, Q?



(a) AND, OR

(b) OR, AND

(c) XOR, XNOR

(d) XNOR, XOR

is

⇒

$1\ 1\ 1 \rightarrow 7$
 $1\ 1\ 0 \rightarrow 6$
 $1\ 0\ 1 \rightarrow 5$
 $0\ 1\ 1 \rightarrow 3$
 i.e. $\Sigma(3, 5, 6, 7)$

$S T_0 + S T_1$
 $A \cdot B C + A \bar{B} C + A B \bar{C} + A B C$

$3 \rightarrow \bar{A} B C$
 $5 \rightarrow A \bar{B} C$
 $6 \rightarrow A B \bar{C}$
 $7 \rightarrow A B C$

$\bar{A} B C + A \bar{B} C$


$P = B C$
 $Q = \bar{B} C + B \bar{C} + B C = B + C$

P has to be AND operation
 AND OR operation

6) Consider a 2x1 MUX which has inputs X, Y and the select line is Z. The MUX select X when Z=0 & select Y if Z=1. If it is required to represent a two variable function $F(P, Q) = \bar{P} + Q$. What will be X, Y, Z?

- (a) $P \quad Q \quad P$ (b) $P \quad 1 \quad Q$ (c) $P \quad 1 \quad P$ (d) $Q \quad Q \quad P$ (e) $P \quad Q \quad 1$ (f) $Q \quad P \quad 1$

⇒

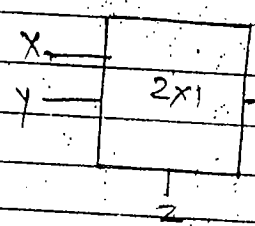


$\bar{Z} X + Z Y$
 $\bar{P} \cdot 1 + P \cdot Q = \bar{P} + PQ$

- X Y Z
 (a) P Q P = P Q
 (b) P 1 Q = $\bar{P} P + Q = P + Q$
 (c) P 1 P = P
 (d) 1 Q P = $\bar{P} + P Q = \bar{P}$

Expansion of Multiplexers.

The higher capacity MUX is constructed with combination of lower capacity MUX arranged in multiple levels.

Target	MUX	8x1
Basic	Nx1 N < M	2x1
Number of levels	$K = \log_N M$	$\log_2 8 = 3$
K		1 2 3
Number of mux in lth level	M/N^l	8/2 8/(2) ² 8/(2) ³
Total multiplexers	$\sum_{l=1}^K (M/N^l)$	4 + 2 + 1 = 7
Maximum capacity with K-levels	$N^K \times 1$	2 ³ x 1 = 8x1

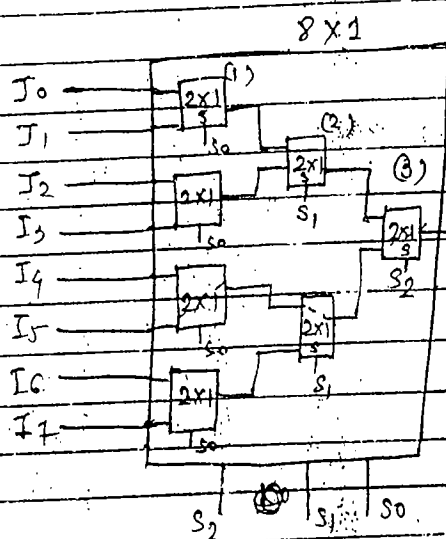

For ex: $1 \ 0 \ 1 = 5$

① How many 4x1 mux are required to construct 128 MUX?

→ Target 128x1
Basic 4x1


$$\log_4 128 = \frac{7}{2} \approx 4 = \text{No. of levels} = k$$

$$\log_{a^m} a^n = m/n$$

	1	2	3	4
Num of Mux in ith level	128 4	128 (4) ²	128 (4) ³	128 (4) ⁴
Total Mux	32	+ 8	+ 2	+ 1 = 43

Max capacity with k-level $(4)^k \times 1 = 256 \times 1$


* MOD-4 Gray Counter *

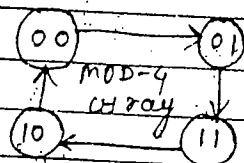


what is next state of

A	B	A _N	B _N
0	0	0	1
0	1	1	1
1	0	0	0
1	1	1	0
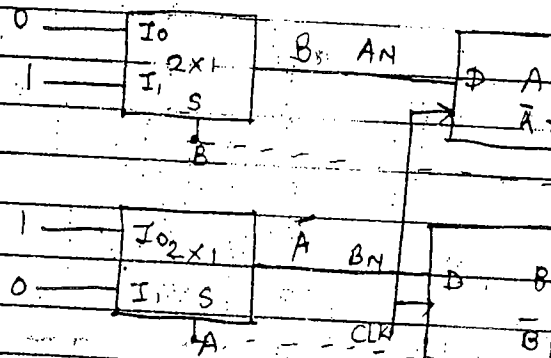
$$\begin{aligned} A_N(A, B) &= \bar{A}B + AB = B \\ B_N(A, B) &= \bar{A}\bar{B} + \bar{A}B = \bar{A} \end{aligned}$$



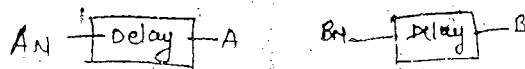
every next present state become next state after sometime present




Demultiplexer (one to many)

It is useful in the presence of multiplexed input. with the slight modification of the multiplexer b/w is converted into demultiplexer. The Dmux provides decoder after modifying its basic block. Decoders are useful for address selection & code conversion.


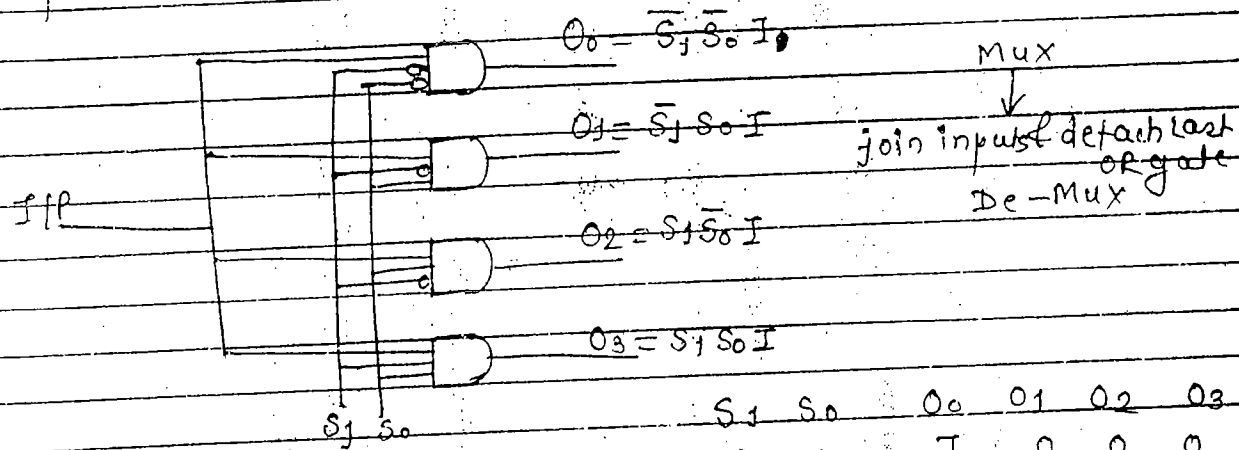
ex: $\rightarrow$ LS 74 158 (IC) $\rightarrow$ 8x8 Decoder
 Low speed $\leftarrow$ $\rightarrow$ silicon
 Low power



S_1	S_0	O_0	O_1	O_2	O_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

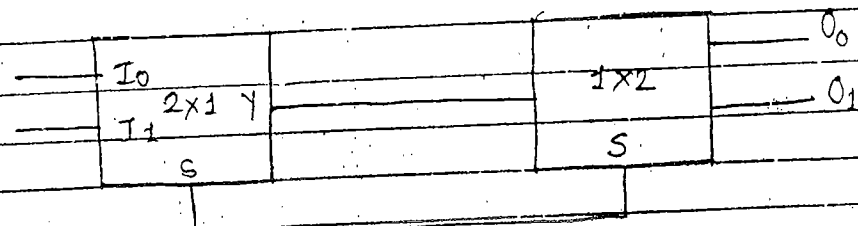

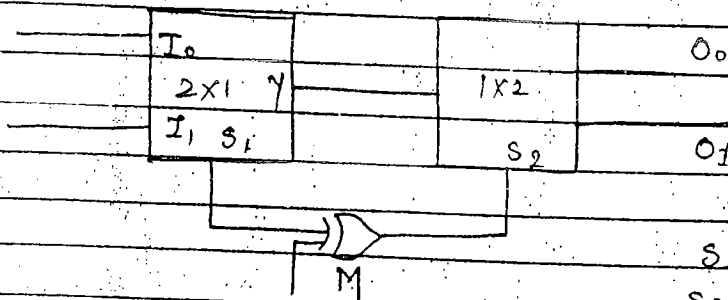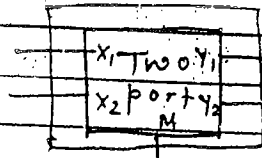$I_0 \rightarrow O_0$
 $I_1 \rightarrow O_1$




$$S_2 = M \oplus S_1$$

$$S_2 = S_1 \quad \{ M=0; \text{straight conn} \}$$

$$S_2 = \bar{S}_1 \quad \{ M=1; \text{cross conn} \}$$

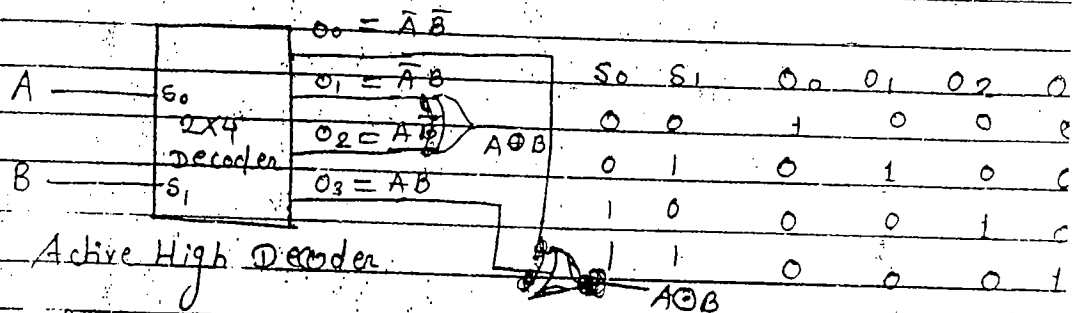
The Decoder $\Rightarrow$ If i/p of Demux is inactivated & select lines are converted into i/p then it's function as decoder.



When O_1 & O_2 are XOR'd $O_1 + O_2 = A \oplus B$
 When O_0 & O_3 are XOR'd $O_0 + O_3 = A \oplus B$

- ① one decoder can realise multiple functions.
- ② one Mux can realise only one function.

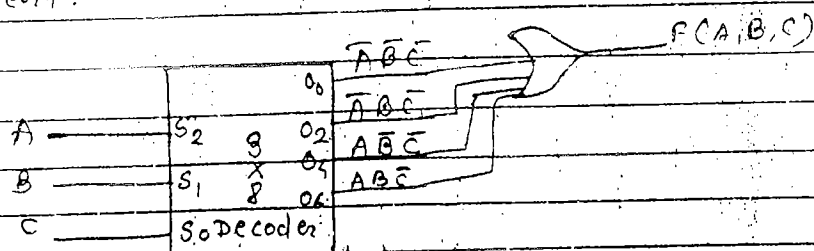① w.r. to following realisation identify the correct statement.




F is free from

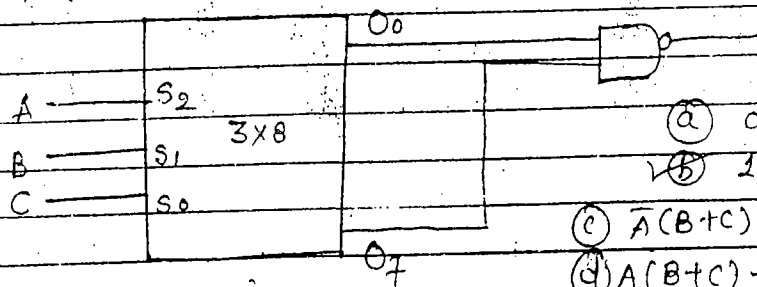- (a) one variable
- (b) 2 variables
- (c) 3 variables
- (d) not free from any variable

$$\Rightarrow F(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C = \bar{C}$$

② what will be the funcn given by the following decoder setup?




- (a) 0
- (b) 1
- (c) $\bar{A}(B+C) + A(\bar{B}+\bar{C})$
- (d) $A(B+C) + \bar{A}(\bar{B}+\bar{C})$

$$\begin{aligned} 0_0 &= 000 \\ 0_7 &= 111 \end{aligned} \quad \left. \begin{array}{l} 0_0, 0_7 = 1 \end{array} \right\}$$

$$\bar{A}\bar{B}\bar{C}$$

$$ABC$$


000

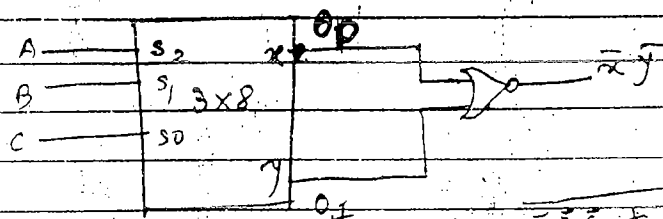

$$\overline{A} \overline{B} \overline{C} + A B C =$$

$$\begin{aligned} &= \overline{A} \overline{B} \overline{C} + A B C \\ &= (A+B+C) \cdot (\overline{A} + \overline{B} + \overline{C}) \\ &= A + (B+C) + A(\overline{B} + \overline{C}) \quad \text{OR} \quad \overline{B}(A+C) + B(\overline{C} + \overline{A}) \quad \text{OR} \\ &\quad \overline{C}(A+B) + C(\overline{A} + \overline{B}) \end{aligned}$$

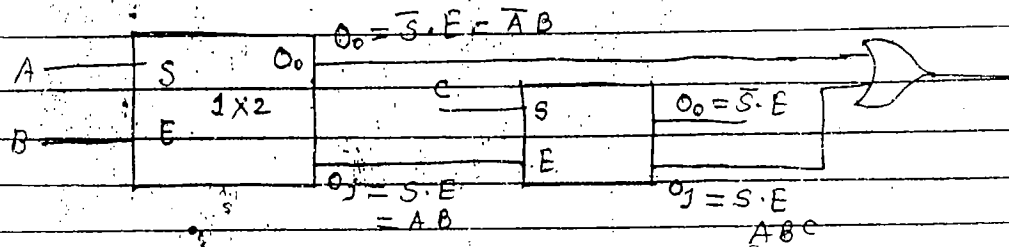
③ what is the function given by following decoder




$$\begin{aligned} &AB + ABC \\ &= B(\overline{A} + A) = B(\overline{A} + C) \\ &= \overline{A}B + BC \end{aligned}$$

2×4
 $2 + 4 = 6$
 $2 + 2 \times 4 = 10$
 $2 + 8 = 10$

* Active Low Decoder *

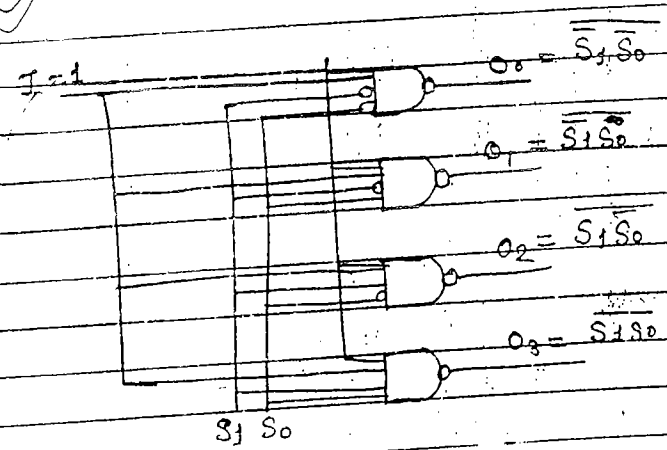


S ₁	S ₀	O ₀	O ₁	O ₂	O ₃
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

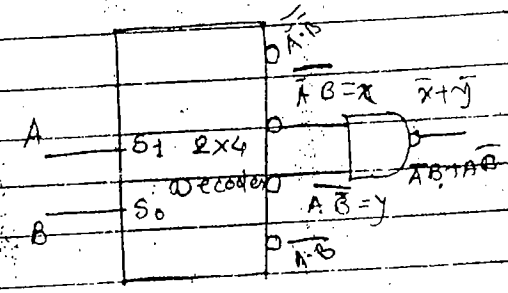

Active low decoders are preferred to Active high decoders as they require less number of universal gates.

Decoder	2×4	$n=2$
Active High	$m+n$	$m+n$
Active Low	$m+n$	$m+n$

ex: 2×4 active High Decoder

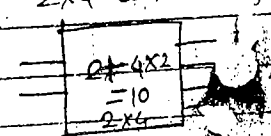


As req. less no. gates active low prefer



Active low (with bubble)

Active High


funcn represented by following decoder.

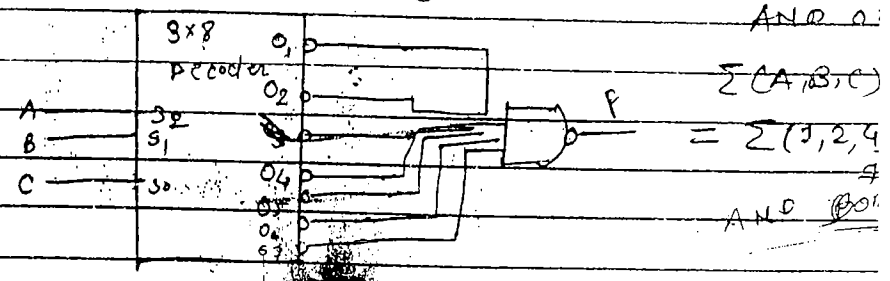

c \ AB	00	01	11	10
0	0	1	1	1
1	1	1	1	1

$$F = \bar{A}\bar{B}C + B\bar{C} + AB + A\bar{C}$$

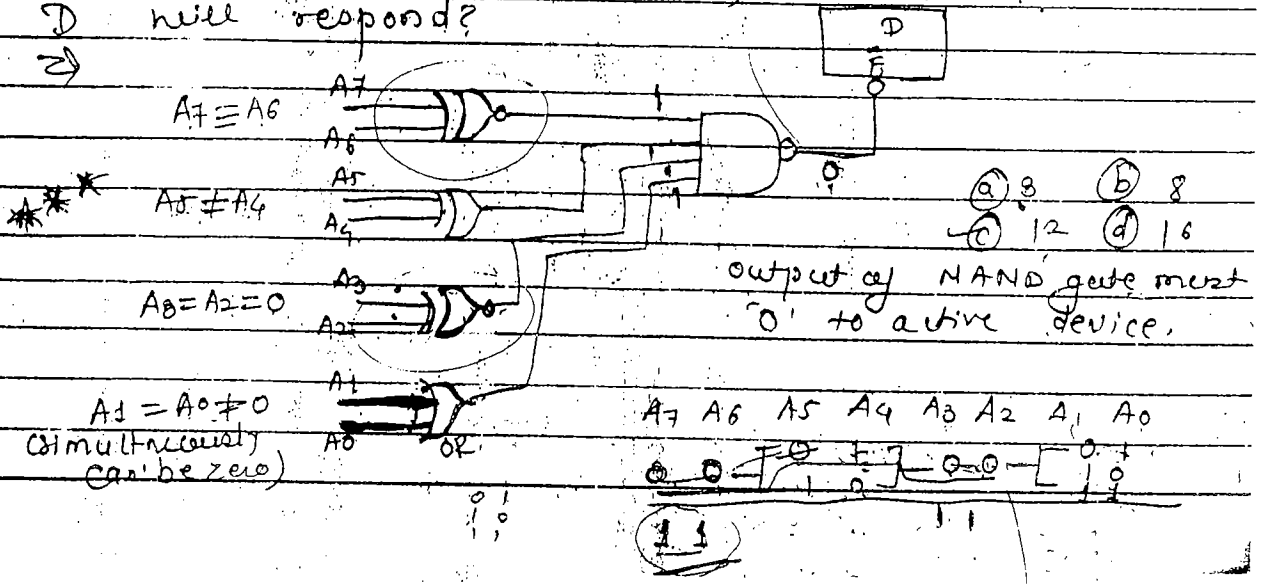Q consider an 8 bit address bus which was aim to activate device D. How many addresses does device D will respond?




- (a) 8
- (b) 8
- (c) 12
- (d) 16

2¹⁰ = 1KB

0001 0001	0010 0001 *
0001 0010	0010 0010 *
0001 0011	0010 0011

11H	21H
12H	22H
13H	23H
14H	24H
15H	25H
16H	26H
17H	27H
18H	28H
19H	29H
1AH	2AH
1BH	2BH
1CH	2CH
1DH	2DH
1EH	2EH
1FH	2FH

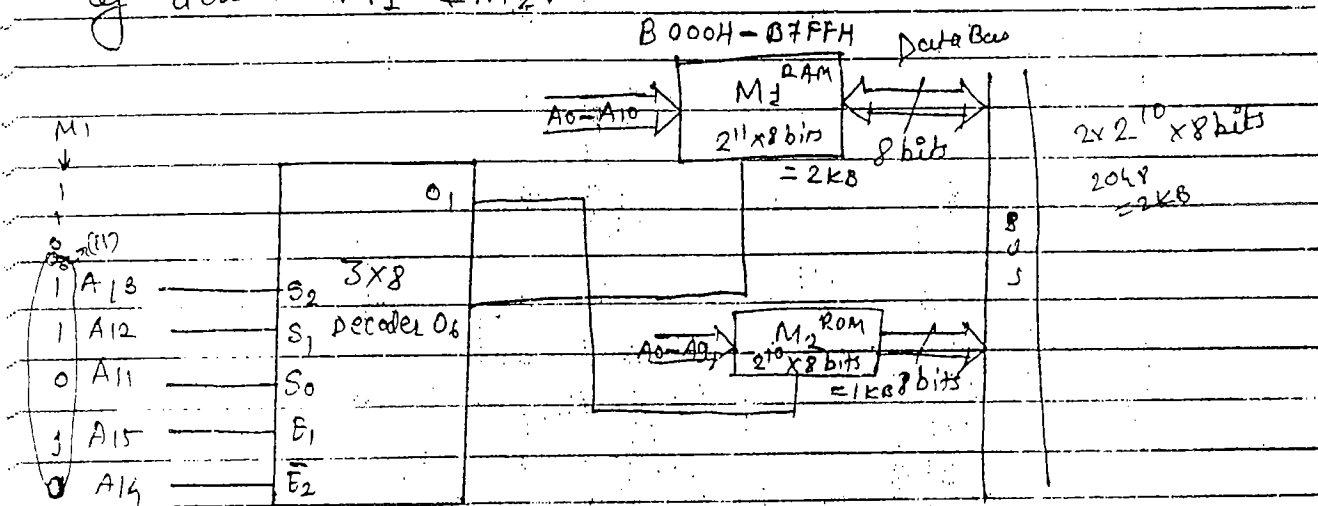consider two memory devices M_1 & M_2 which are activated by the following decoder setup?
 A 16-bit Address bus is used for this purpose. What will be the type & capacity of device M_1 & M_2 ?



- (i) Type & capacity of device
- (ii) Address range of each device

(iii) First three location address of M_1 &
last three locates address of M_2

Solⁿ ⇒ (i) To activate high decoder M_1 ~~rep~~ 06
6 represent

(M₁): B 000 H - B7 FFH

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0
M_1															
1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
M_2															

8800H to 8BFFH M_1
8C00H to 8FFFH M_2


(iv) First three addresses of M_1
B000H, B001H, B002H
last three addresses of M_2

8BFDH, 8BFEH, 8BFFH
8FFDH, 8FEEH, 8FEEH

* Expansion of the Decoders *

The higher capacity decoder is constructed using the smaller capacity decoders in multiple levels.

Target	$M \times N, N = 2^M$	3×8
Basic	$p \times \phi, \phi = 2^p \text{ \& } \phi < N$	1×2
Number of levels	$K = \frac{M}{p} = \log_{\phi} N$	$K = \log_2 8 = 3$
Number of Decoders in i th level	$\frac{N}{\phi^{K-i+1}} = x$	$\frac{8}{2^{3-1+1}} = 1, \frac{8}{2^{3-2+1}} = 2, \frac{8}{2^{3-3+1}} = 4$
Total decoders	$\sum_{i=1}^K x$	$1 + 2 + 4 = 7$
Maximum capacity capability with K -levels	$(p * K) \times \phi^K$	$(1 * 3) \times 2^3 = 3 \times 8$

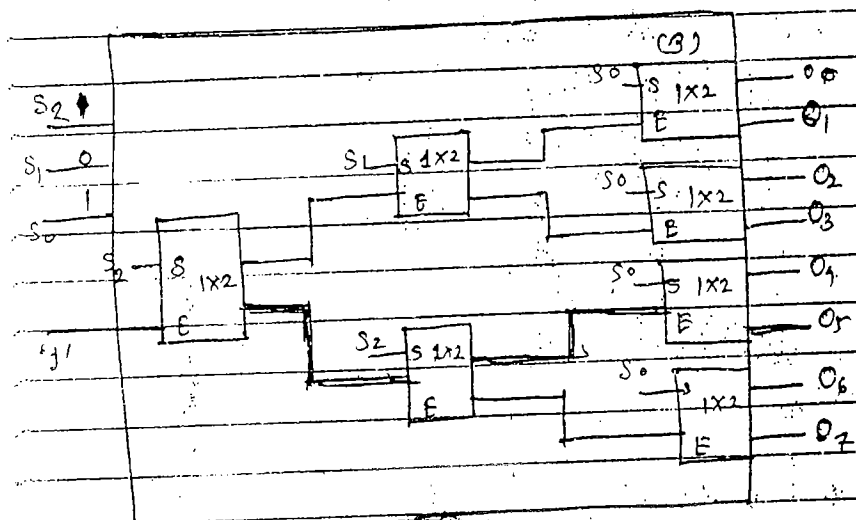

① How many 3×8 decoder are required? to construct 8×256 decoder.

Target 8×256
Basic 3×8
Level $k = 8/8 \approx 3$

1 2 3

$$\frac{4}{8} \times \frac{32}{8} \times \frac{256}{8} = 32$$


$$1 \times 4 \times 32 = 128$$

$$(3 \times 3) \times 8^3 = 9 \times 512$$

36 $\rightarrow 3 \times 8$ decoder

1 $\rightarrow 2 \times 4$ decoder

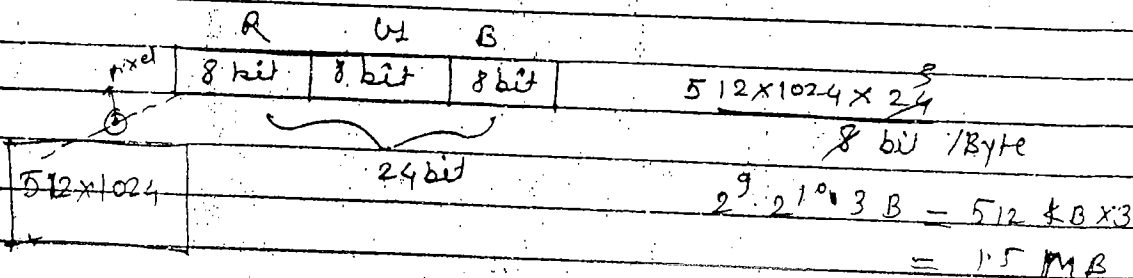② Consider a graphic system which was suppose to use the 3 primary colors with each color is having 256 levels depth. The screen that is used is having the resolution 512×1024 . What will be the memory required for frame buffer?
(frame buffer $\equiv$ maintain info for every pixel)



*


* Encoder *

The encoder used to convert decimal input to binary if they are provided with priorities they can support the interrupt servicing. In the design of encoder its needed to know the rule of encoding.

ex: → Highest suffix input is encoded with highest binary value.

The non-priority encoders doesnot support simultaneous activation of inputs. The priority encoders reduces the h/w & support simultaneous activation. The rule of assigning priorities can be taken as - highest suffix i/p is given with highest priority.

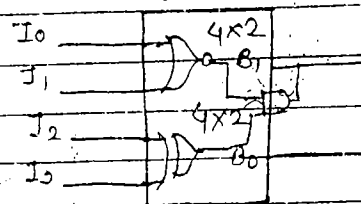The priority encoder suffer the starvation due to the static priorities.



Non-priority Encoder


I_0	I_1	I_2	I_3	B_1	B_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1


$$B_1 = I_0' I_1' I_2 I_3' + I_0' I_1' I_2' I_3$$

$$B_0 = (I_0 + I_2)' \cdot (I_1 \oplus I_3)$$

$$B_1 = I_0' I_1' (I_2 \oplus I_3)$$
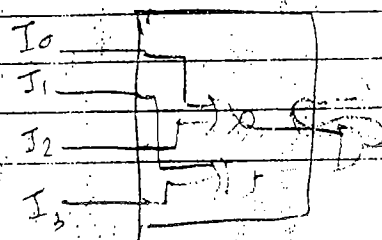
$$B_0 = (I_0 + I_1)' \cdot (I_2 \oplus I_3)$$



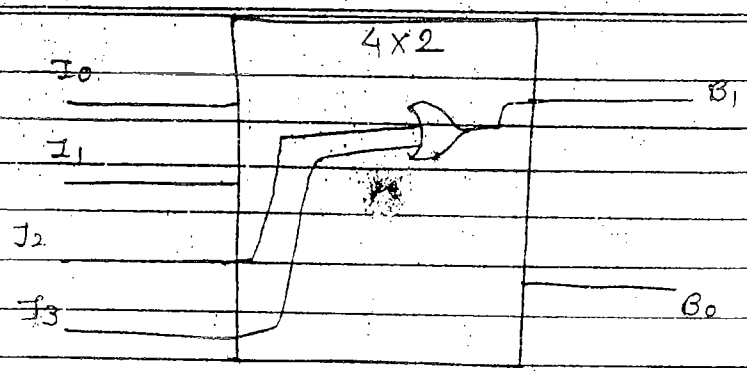

priority Encoder

I_0	I_1	I_2	I_3	B_1	B_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$$B_1 = I_2 \cdot I_3' + I_3$$


$$B_0 = (I_2 + I_3)$$

$$B_1 = I_1 I_2' I_3 + I_3$$

$$B_0 = I_1 I_2' I_3$$

Approach for static priority encoder starts from lower priority

* Sequential Circuits


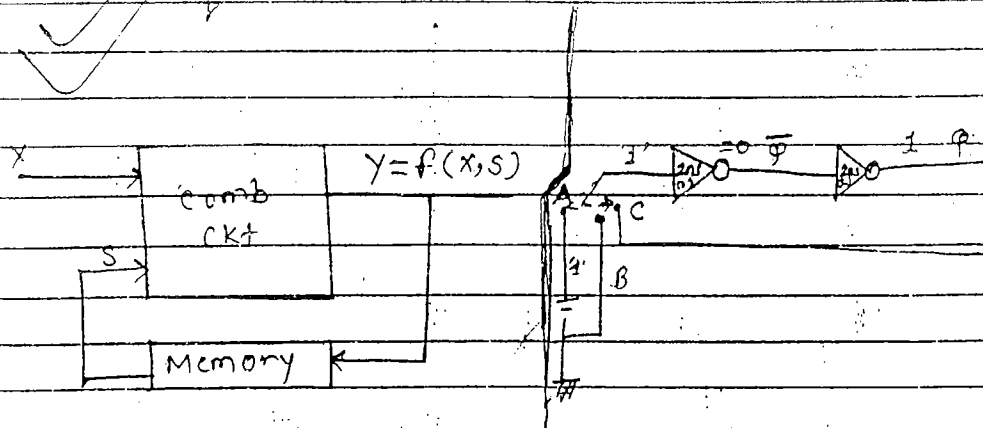


$s \rightarrow$ state $\dots \rightarrow$ previous output

operates

① valid output $\Rightarrow$ complementary o/p

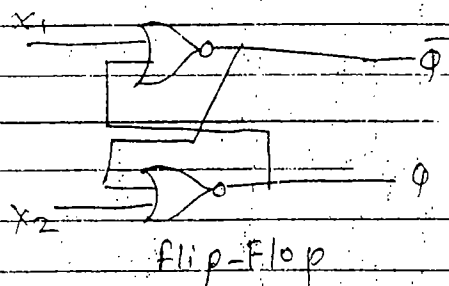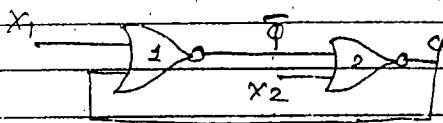② Same control input used for entry of logic '1' & '0'.



FlipFlop is basic memory element & its capable of 1-bit storage. It contains two stable

states (stable states maintain complimentary relation for valid operation). The flip-flop also called as bistable multivibrator.

① They are classified based on construction operating mode, nature of clock synchronized & nature of the funcn.

construction	NOR
	NAND

operating mode	Transparent (follow $\uparrow/\downarrow$)
	latched Mode ($Q_n = Q$)


Nature of synchronizatio	Level Triggered Flip-flop } latch
	Edge Triggered Flip-flop } synchronous flipflop

Nature of funcn	S-R (set-reset) F.F.
	J-K F.F.
	D (delay) F.F.
	T (Toggle) F.F.

features are:- ① characteristic expression
 $Q_n = f(X, Q)$

② Excitation Tables

stable state
& maintain
complement

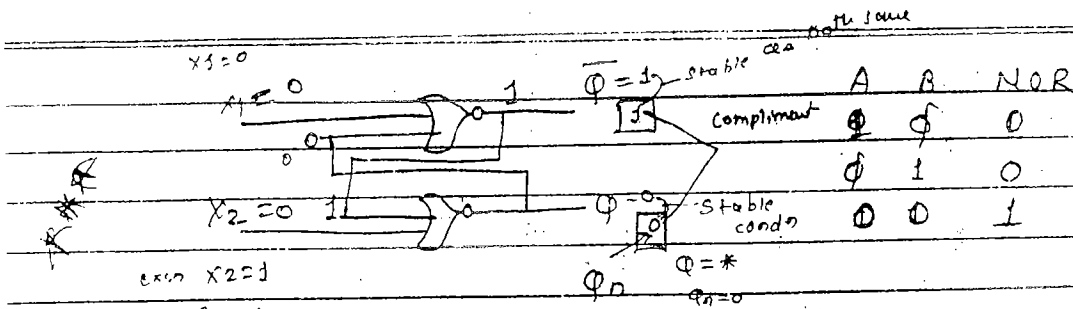

ex: X2=1


Set	Reset	State table	
X1	X2	Q	Qn
0	0	0 ^A	0
0	0	1 ^B	1
0	1	0 ^A	0
0	1	1 ^B	0
1	0	0 ^A	1
1	0	1 ^B	1
1	1	0 ^A	0
1	1	1 ^B	0

Qn = Q

Qn = 0 whatever may be Q
Qn always 0

Qn = 1 whatever may be Q
Qn always 1

invalid

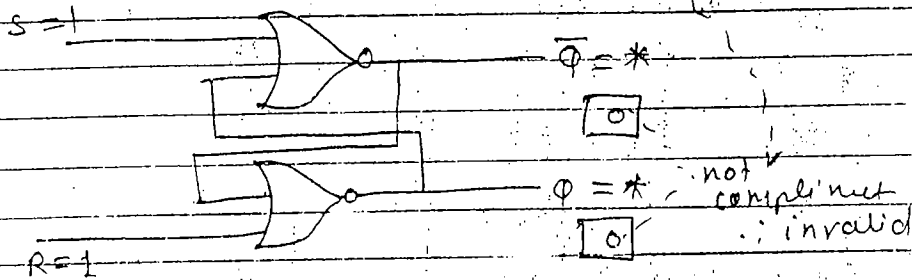

$$\therefore Q_n = f(S, R, Q) = \sum (1, 4, 5) + \sum_{\phi} (6, 7) \quad ***$$

Q \ SR	00	01	11	10
0	0	2	0	1
1	1	3	0	1

$$Q_n = S + RQ$$


$\begin{matrix} 0 & 0 \\ 0 & 1 \end{matrix} \rightarrow 00$
 $\begin{matrix} S & R \\ 0 & 0 \end{matrix}$

Excitation table of S-R flip flop
 "for getting desired change at output what values are needed at input"

$Q \rightarrow Q_0$	S	R
0 $\rightarrow$ 0	0	ϕ
0 $\rightarrow$ 1	1	0
1 $\rightarrow$ 0	0	1
1 $\rightarrow$ 1	ϕ	0


obtain above table from state table

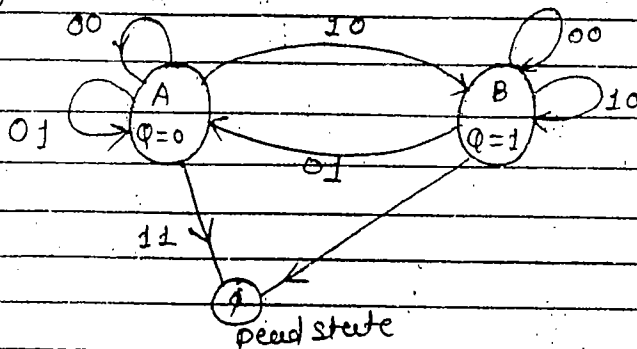State diagram of S-R flip flop $\Rightarrow$
 (from state table)



S-R NAND flip flop $\Rightarrow$ The SR-NAND behaviour is same as ~~S-R~~ $S \neq R$. It will perform oppositely when $S = R$.

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

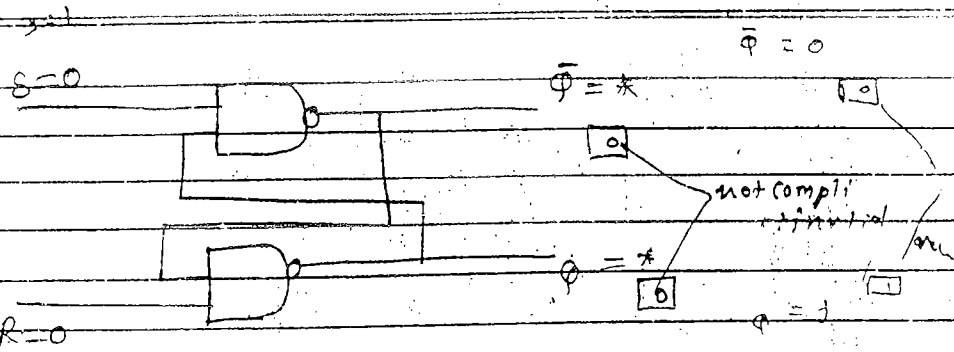

X_1	X_2	Φ	Φ_n	
0	0	0	ϕ	} invalid
0	0	1	ϕ	
0	1	0	0	} $\Phi_n = 0$
0	1	1	0	
1	0	0	1	} $\Phi_n = 1$
1	0	1	1	
1	1	0	0	} $\Phi_n = 0$ } $\Phi_n = \Phi$
1	1	1	1	



$$\Phi_n = (S, R, \Phi) = \sum (4, 5, 7) + \sum_{\phi} (0, 1)$$

$$\Phi_n = \bar{R} + S\Phi$$

Excitation Table $\Rightarrow$



$\Phi \rightarrow \Phi_n$	S	R
0 0	ϕ	1
0 1	1	0
1 0	0	1
1 1	1	ϕ

State Diagram $\Rightarrow$

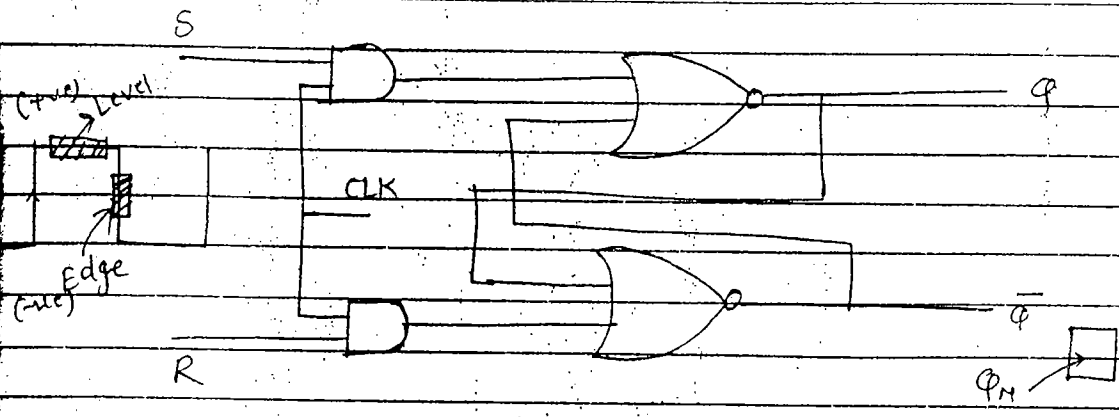
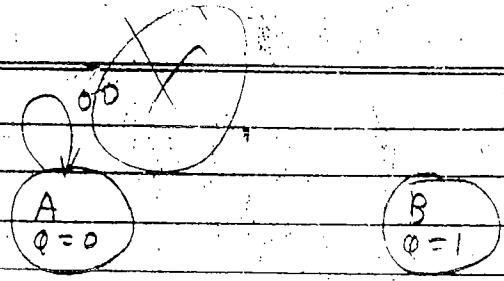


If CLK is inactive in clocked FF the flip flop retain last state ~~input~~ independent of inputs.

Level Triggerred (Latch)

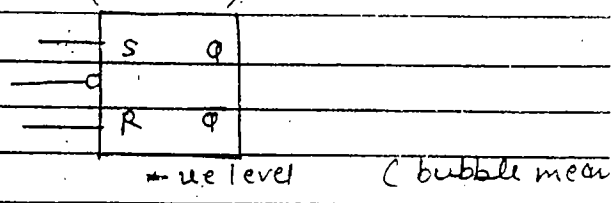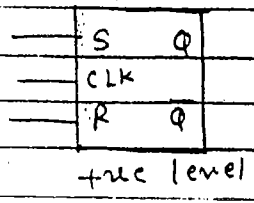


Edge Triggerred

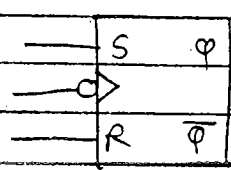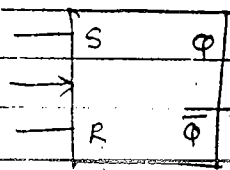

→ invalid response in LM

Transparent Mode - TM
Latched Mode - LM

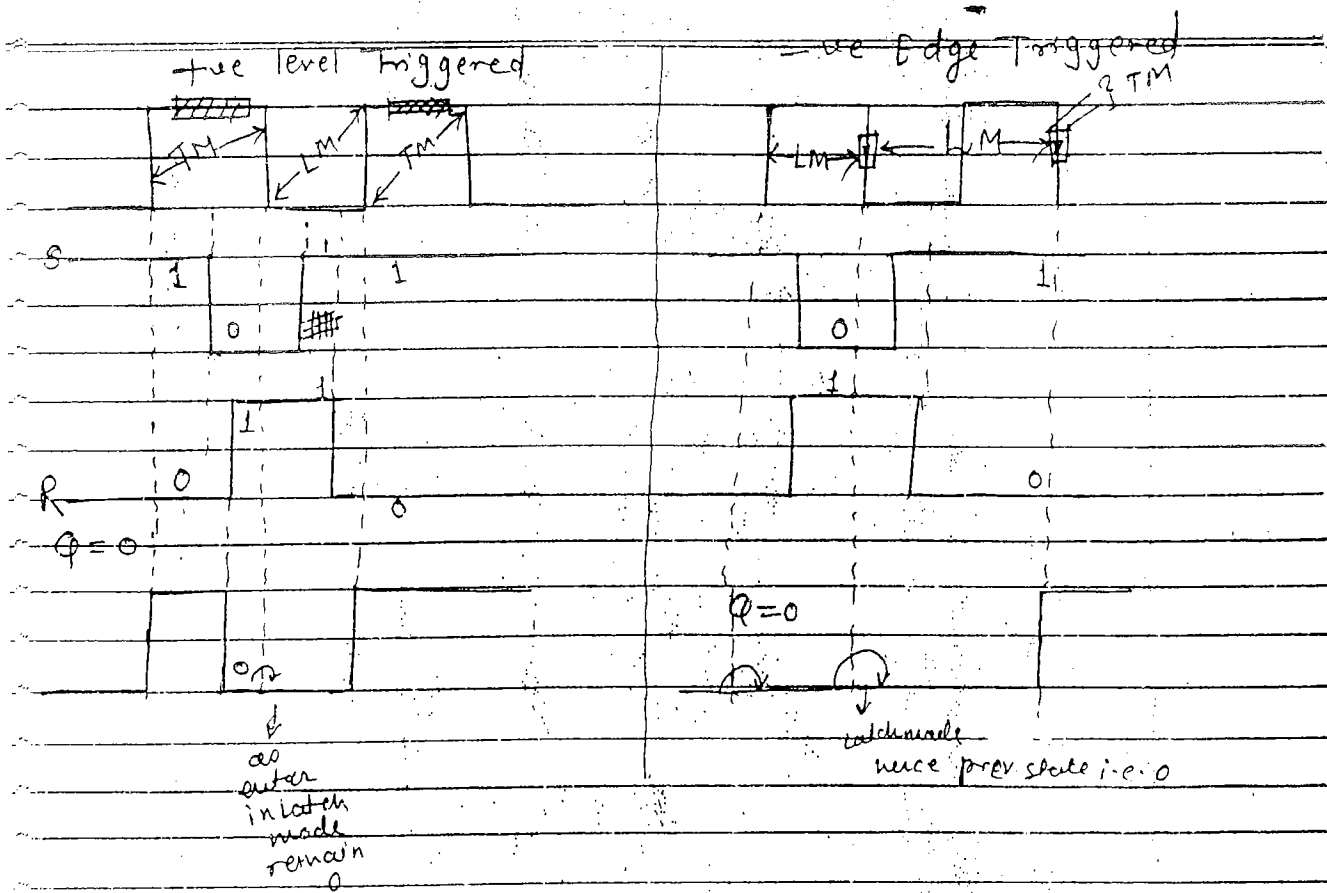

- ① The edge triggering is preferred to level triggering because it is more insensitive ^(not change) to the noise. The reason is shorter duration of transparent mode.
- ② In noisy environment edge triggered f.f. is preferred.
- ③ The o/p is more smooth in edge triggering as compared to level triggering.

* J-K Flip Flop *

This F.F. is similar to SR-Flip Flop ($J=S, K=R$). It is defined when both inputs are 1. If $J=K=1$, the F.F. complements its previous output.

The J-K flip flop can be used as two indiv. one input F.F.

- ① D-Flip Flop ($J \neq K$)
- ② T-Flip Flop ($J=K$)


State Table of J-K Flip Flop

J	K	Q	Q _n
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


$Q_n = f(J, K, Q) = \sum (1, 4, 5, 6)$

Q	JK	00	01	10	11
0	0	0	1	1	1
1	1	1	1	1	0

$Q_n = J\bar{Q} + KQ$

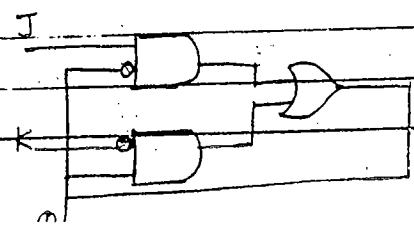


State diag $\rightarrow$

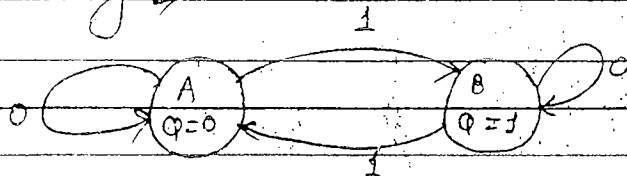

Excitation statement $\Rightarrow$ whenever there is a change at output T must be 1.

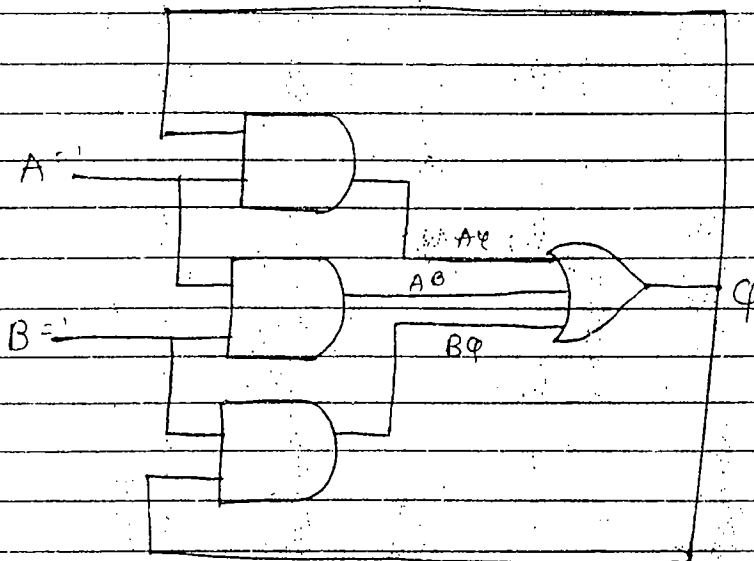① Consider the following sequential ckt. obtain the state table, char exp, state diag & excitation Table



$$Q_n = AB + Q(A + B)$$

$$A = B = 1$$

$$Q_n = 1$$

else


$$A = B = 0$$

$$Q_n = 0$$

$$A = 0, B = 1 \text{ \& } A = 1, B = 0$$

$$Q_n = Q$$


A	B	Q	Q ₀
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

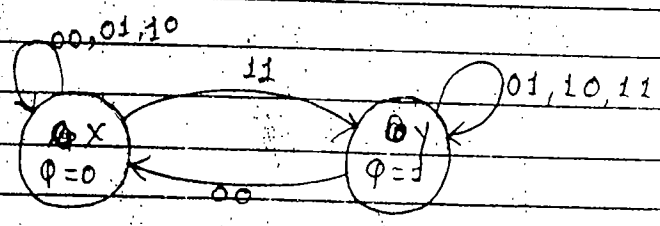

excitation Table $\Rightarrow$

Q $\rightarrow$ Q ₀	A	B
0 0	ϕ	ϕ
0 1	1	1
1 0	0	0
1 1	ϕ	ϕ

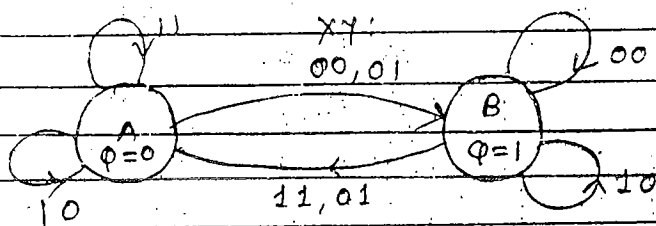Q. Convert the following state machine using JK FF.
Obtain the J & K.




partial table


X	Y	ϕ_n	J	K
0	0	1	0	0
0	1	0	1	1
1	0	0	0	0
1	1	0	0	1

$$J = \bar{X} \cdot Y + \bar{X} \cdot \bar{Y} = \bar{X}$$

$$K = \bar{X} \cdot Y + X \cdot Y = Y$$

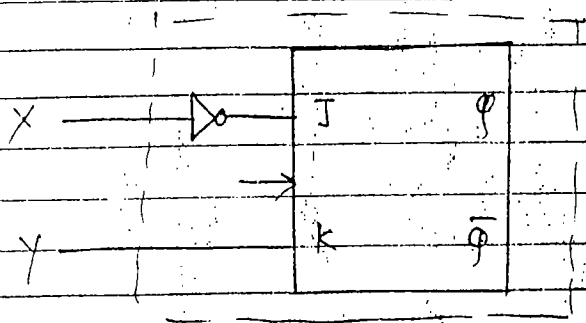

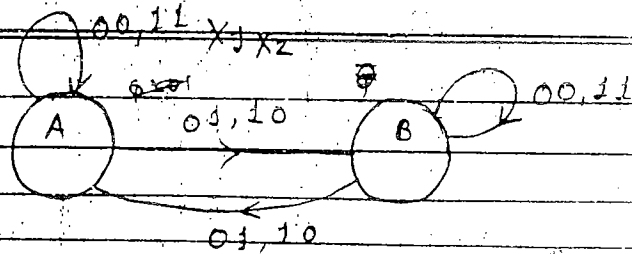Q. Consider the following state diag. which has two states A & B with two i/p's X_1 & X_2 . It is to be represented by J-K f.f. what will be the expr for J & K i/p's.



- (a) $\bar{x}_1 x_2 + x_1 \bar{x}_2, \bar{x}_1 \bar{x}_2 + x_1 x_2$
 (b) $\bar{x}_1 \bar{x}_2 + x_1 x_2, \bar{x}_1 x_2 + x_1 \bar{x}_2$
 (c) $\bar{x}_1 \bar{x}_2 + x_1 x_2, \bar{x}_1 \bar{x}_2 + x_1 x_2$
 ✓ (d) $\bar{x}_1 x_2 + x_1 \bar{x}_2, x_1 \bar{x}_2 + \bar{x}_1 x_2$


x_1	x_2	Q_0	J	K
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	0	0	0

as

is

e

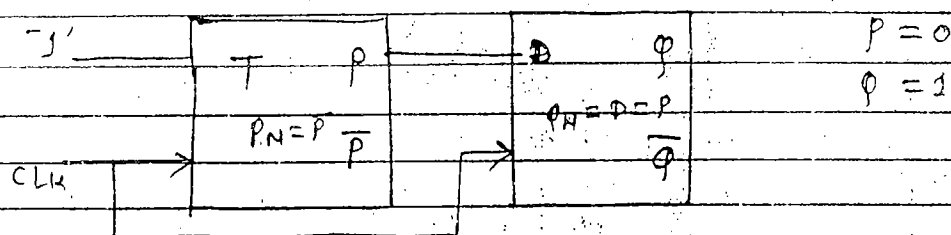Q2 Consider the following sequential ckt. which has initial value $P=0$ & $\Phi=1$. what will be the value of P & Φ after 3 clock cycle?



present state ~~next state~~


	P	Phi	$P\bar{N} = \bar{P}$	$\Phi_N = P$
0	0	1	1	0
start	0	1	1	0
1	0	0	1	0
1	1	0	0	1

(A) 00

(B) 01

(C) 10

(D) 11

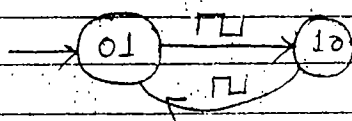

after odd clk goto 10

Q.3 Consider the following sequential machine which has two i/p's A & X. If their values for six clk cycles given by following table. what will be the o/p produced at Y?


$$Q_2 = A \times \overline{X} \overline{Q}$$

$$= A \quad \text{if } x=1$$

Diagram illustrating the states of a system with two components, A and B, and their transitions:

- State A: A self-loop labeled $0/0$.
- State B: A self-loop labeled $0/1, 1/0$.
- Transition from A to B: Labeled $1/0$ (top) and $1/1$ (bottom).
- Transition from B to A: Labeled $0/1$.

- (a) 1's Complementor
- ✓ (b) 2's Complementor
- (c) Bin to Gray Converter
- (d) Incrementer

First LSB

451

Q. Present state

Next state, Z

X=1 X=0

A	B, 0	C, 1
B	C, 0	C, 1
C	D, 0	A, 0
D	C, 0	C, 1

First
B: 10
Z: 11

Bin	Gray
00	00
01	01
11	11
10	10

2's complement $\Rightarrow$ $\lambda: 1011 \leftarrow A$ $\leftarrow A$ $\leftarrow A$ $\leftarrow A$ $\leftarrow A$ $\leftarrow A$ $\leftarrow A$ $\leftarrow A$
 $z: \$(x): 0110 \rightarrow op$

Q. > If the initial state is not known what is min i/p string? Take the machine into state c.

- (a) 01 (b) 10 (c) 101 (d) None

