

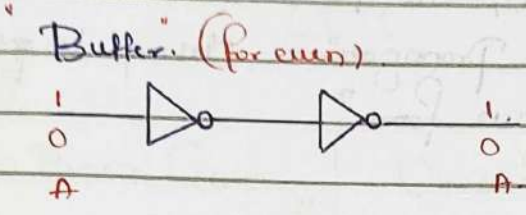
 


LOGIC GATES

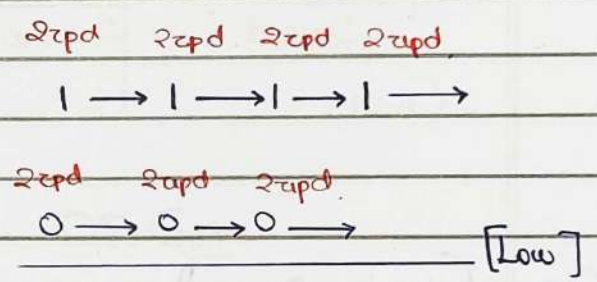1. NOT Gate [Inverter, Negation, Compliment Logic].





 No. of not gates are even - "Buffer"
No. of not gates odd - "Inverter"
[High.]



Whenever even numbers of 'not' gate in circuit (loop).

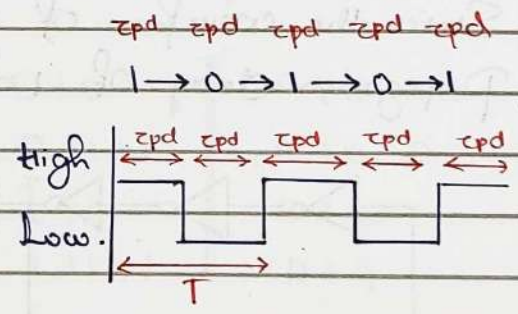 1. Basic memory element
2. Bistable multivibrator
3. DC Generator ($F = 0 Hz$)



When Odd no. of NOT Gate:

1. Astable multivibrator
2. Square wave generator
3. Clock generator
4. Free running circuit
5. Ring oscillator.

$T = 2\tau_{pd}$

$f = \frac{1}{2\tau_{pd}}$

$f = \frac{1}{T}$

$$T = 2 \times N \times t_{pd} \quad N = \text{no. of not gate in loop.}$$

$$f = \frac{1}{2Nt_{pd}}$$

* Both formulae applicable when number of NOT Gate are odd.

Q1. For the circuit given below, all NOT Gate are identical to each other and having Propagation delay $10 \mu\text{s}$. Find the frequency of generated wave form? 10^{12} .

$$N = 5 \quad t_{pd} = 10 \times 10^{-12}$$


$$f = \frac{1}{2Nt_{pd}} = \frac{1}{2 \times 5 \times 10 \times 10^{-12}} = \frac{10^{12}}{10 \times 10} \text{ Hz}$$

(odd)

$$= 10^9 \text{ Hz}$$

$$\therefore \underline{f = 10 \text{ GHz}}$$


 
Q2. Circuit given below are called Astable Multivibrator.




Note: always, For calculation of frequency consider the no. of NOT gate in loop.

HW

  Q3. Sketch the waveform of y if all not gate are identical and having Propagation delay of 1 microsecond.



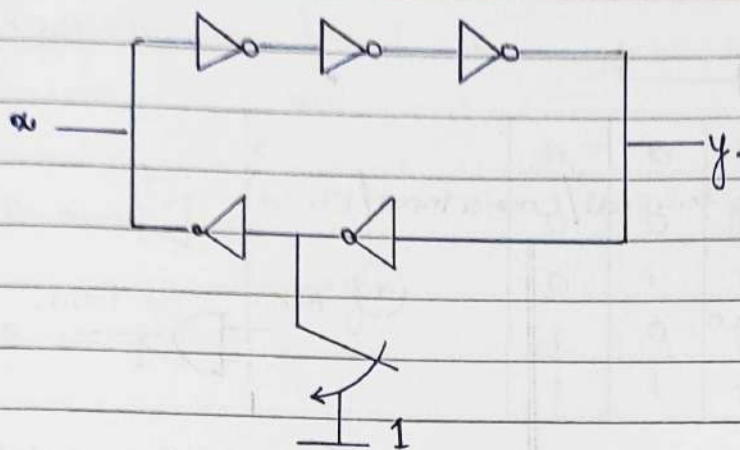Q4. For the circuit given below x and y condition will be - x and y both toggle.



Odd no of NOT gate in the loop
∴ x and y will toggle

Basic Gate

- NOT
- AND
- OR


Universal Gate

- NAND
- NOR

Exclusive Gate

- X-OR
- X-NOR


AND Gate

 

$A = \{1, 2, 3, 4\}$ $B = \{2, 3, 4\}$
 $A \cap B = \{2, 3, 4\}$

$0 \cdot 0 = 0$ $A \cdot A = A$
 $0 \cdot 1 = 0$ $A \cdot 1 = A$
 $1 \cdot 0 = 0$ $A \cdot 0 = 0$
 $1 \cdot 1 = 1$ $A \cdot \bar{A} = 0$


OR Gate

 

$A = \{1, 2\}$ $B = \{3, 4\}$
 $A \cup B = \{1, 2, 3, 4\}$


$0 + 0 = 0$ $A + A = A$
 $0 + 1 = 1$ $A + 0 = A$
 $1 + 0 = 1$ $A + 1 = 1$
 $1 + 1 = 1$ $A + \bar{A} = 1$

AND Gate [Intersection]


 


A	B	$y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table

 


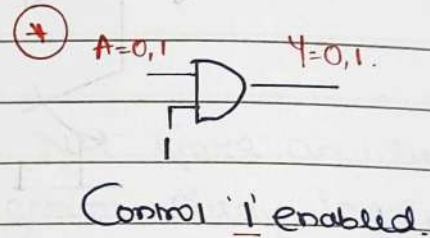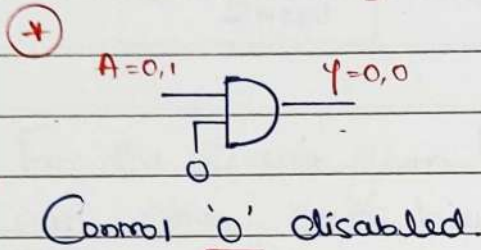floating terminal / Control Input / Strobe






* Commutative Law : $A \cdot B = B \cdot A$
 * Associative Law : $(A \cdot B) \cdot C = A \cdot (B \cdot C)$

 
} AND is both commutative and associative.



TTL = Transistor Transistor Logic.

   


"Diode"

 

$V_p > V_n \rightarrow$ Forward bias \rightarrow Short circuit
 $V_p < V_n \rightarrow$ Reverse bias \rightarrow Open circuit.

Circuit diagram: [AND]

 


A	B	D _A	D _B	y
0	0	FB	FB	0
0	1	FB	Re	0
1	0	Rb	Fb	0
1	1	Re	Re	1

Note:

- * Whenever logic are designed by TTL the floating terminal always connect as high.
- * Whenever logic are designed by ECL (Emitter Coupled Logic) then floating terminal always connect as low.
- * Noise Margin: Maximum noise added to the input which will not affect the output are called Noise margin.
- * Fan out: The number of logic driven by the logic are called fan out.
- * Fan in: Number of input of a logic are called fan in.
- * ECL is the fastest logic among all the logic family.


OR Gate.

 

2. Truth Table.

A	B	y
0	0	0
0	1	1
1	0	1
1	1	1

3. Enable/Disable.



 


4. Commutative: $A + B = B + A$

5. Associative: $A + (B + C) = (A + B) + C$




ECL - Emitter Coupled Logic.

 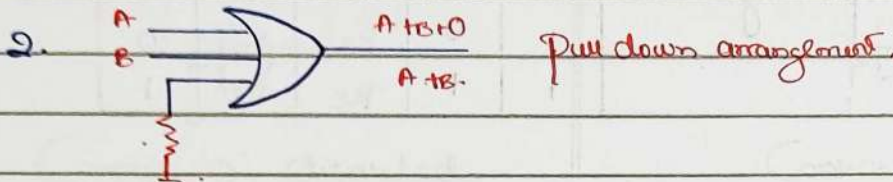 


Q1. Output at $S=0$ is B

$\rightarrow f = B$

 

Q2. $f=1$ for combination of A, B, S

 

[None of the options are correct.]

De Morgan's Law


$\overline{AB} = \overline{A} + \overline{B}$

$\overline{A+B} = \overline{A} \cdot \overline{B}$


Q3. For the given truth table.

A	B	f
0	0	0
0	1	1
1	0	1
1	1	1


Select the respective Combinat. diagram

 

 
Q4. A logical circuit is as shown below, which of the following circuit can be used to get the desired expression.



 Q5. The logic circuit shown below, is equivalent to.



NAND Gate.


 


2. Truth Table.


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

4. Commutative law. ✓

5. Associative law. ✗

  

3. Enable/Disable.

 


Control '0' disabled.

Control '1' enabled


NAND follows commutative law but does not follow associative law.

Transistor

 


Input = 1
Input = 0

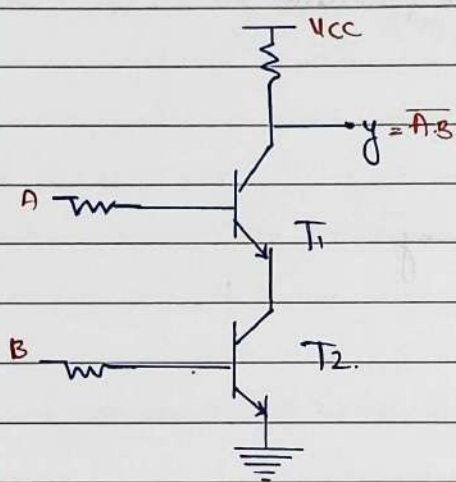ON = Saturation → Short Circuit
OFF = Cutoff → Open Circuit





A	B	T ₁	T ₂	y
0	0	Cutoff	Cutoff	1
0	1	Cutoff	Saturation	1
1	0	Saturation	Cutoff	1
1	1	Saturation	Saturation	0

eg.:

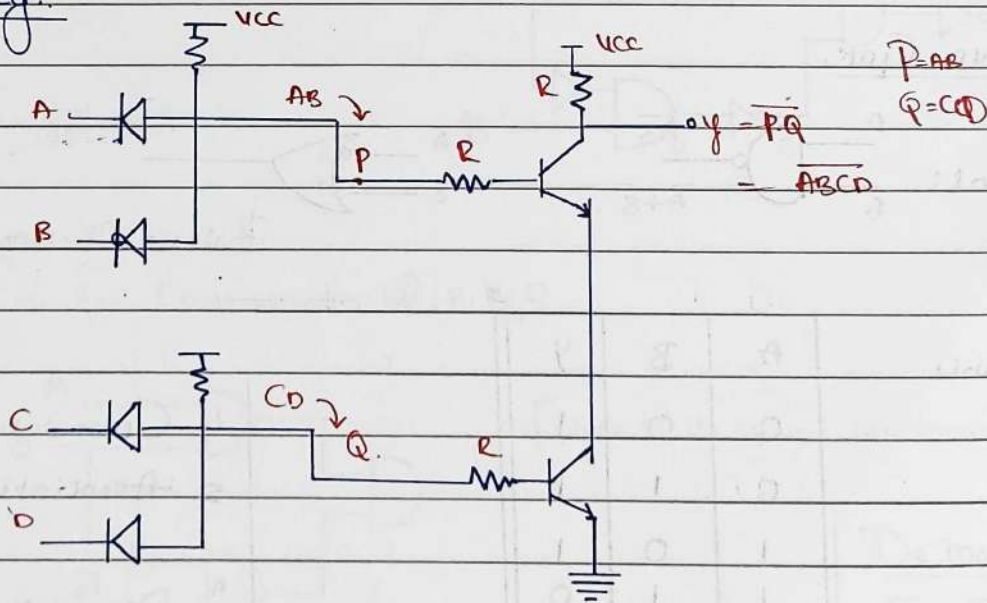

NOR Gate

  


Bubbled AND = NOR

2. Truth Table:


A	B	y
0	0	1
0	1	0
1	0	0
1	1	0

3. Enable/Disable

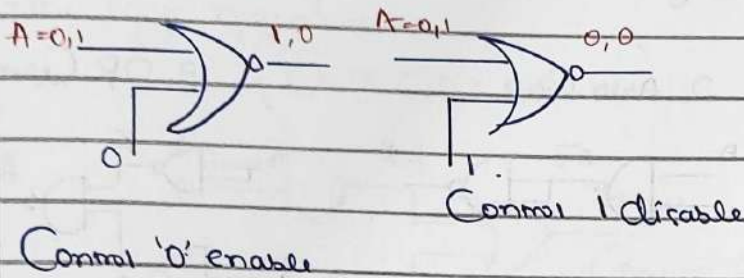

4. Commutative Law ✓

5. Associative Law. ✗

 

A	B	T ₁	T ₂	y
0	0	Cutoff	Cutoff	1
0	1	Cutoff	Saturation	0
1	0	Saturation	Cutoff	0
1	1	Saturation	Saturation	0

Note: NAND, NOR are called "Universal logic".

Q1. Which of the following option is called universal logic?

Ans. Both NAND and NOR. (option given)

Q2. Which of the following is called Universal logic? [MCQ]

Ans. NAND (if both are given choose NAND)


Q3. Which of the following Option(s) is/are called universal logic? [MCQ]

Ans. $(A+B)$, $(\bar{A} \cdot \bar{B})$, $(A+B)$, $A \cdot \bar{B}$.


- $\bar{A} \cdot \bar{B}$
- $\bar{A} + \bar{B}$
- $\bar{A} + B$
- $A + \bar{B}$
- $\bar{A} \cdot B, A \cdot \bar{B}$
- Multiplexer
- Decoder + OR logic

Universal Logic.

X-OR Gate:

 


X-NOR Gate

 

Q2 Find the minimum no. of two input NAND Gate required to implement the logic given below.

$$f(A, B, C, D) = AB + CD$$

 

Create using AOT approach and make it with NAND by adding inverter ('o') to balance out! approach..

∴ 3 NAND Gate required

No. of NAND and NOR Gate Required:

Case (1) : $A \cdot B \cdot \bar{C} \cdot D \cdot E \dots$

$$\rightarrow \text{NAND} = (2n - 2) + k$$

n = total no. of variables

k = no. of Compliment Variables

$$\rightarrow \text{NOR} = (3n - 3) + k$$

n = no. of variables

k = no. of Compliment Variables

eg: $f = A \cdot \bar{B} \cdot C$

$n=3, k=1$


$$\text{NAND} = (2 \cdot 3 - 2) + 1 = 5$$

$$\begin{aligned} \text{NOR} &= (3 \cdot 3 - 3) + 1 \\ &= 6 - 1 = 5 \end{aligned}$$

eg: $f = \bar{A} \cdot B \cdot C \cdot D \cdot E$

$n=5, k=1$
 
$$\text{NAND} = (2 \cdot 5 - 2) + 1 = 9$$



Case (2) : $A + B + \bar{C} + D \dots$

$$\text{NAND} = (3n - 3) - k$$


$$\text{NOR} = (2n - 2) + k$$

eg: $f = \bar{A} + B, n=2, k=1$


$$\begin{aligned} \text{NAND} &= (3 \cdot 2 - 3) - 1 \\ &= 2 \end{aligned}$$

$$\begin{aligned} \text{NOR} &= (2 \cdot 2 - 2) + 1 \\ &= 3 \end{aligned}$$

eg: $\bar{A} + B$

 


Case (3) $f = AB + CD$ [Sum of product]

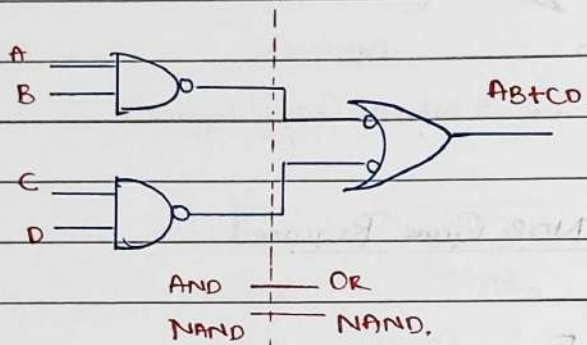


Note: Whenever in the problem the minimum number of NAND Gate are asked then write in SOP form and implement it by AOI and this is exactly equal to NAND NAND implementation.


Q. $f = A\bar{B} + CD$

 

 
$f = AB + CD + E$ $f = x + E$ ($AB + CD$)



 
Q. $f = \underbrace{AB + CD}_x + EF$
 $x \rightarrow 3 + 3$




Q. $\bar{A}\bar{B} + CD$

 

Q1. $f = \bar{A}\bar{B}C$

 


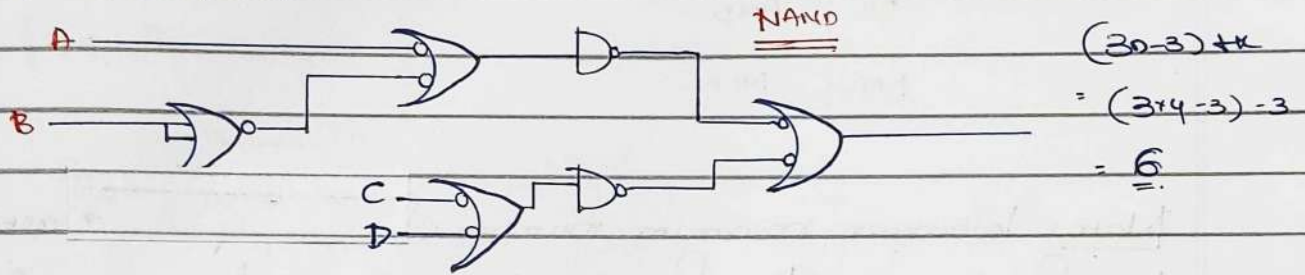Q2. $f = \bar{A} + B + \bar{C} + \bar{D}$



 
Q3. $f = AB + BC + CD + DA$

$f = B(A+C) + D(A+C)$
 $f = Bx + Dx, \quad A+C = x$




Case (4). Most Important.

 Q1. $\bar{A}B + A\bar{B} \rightarrow \text{XOR}$



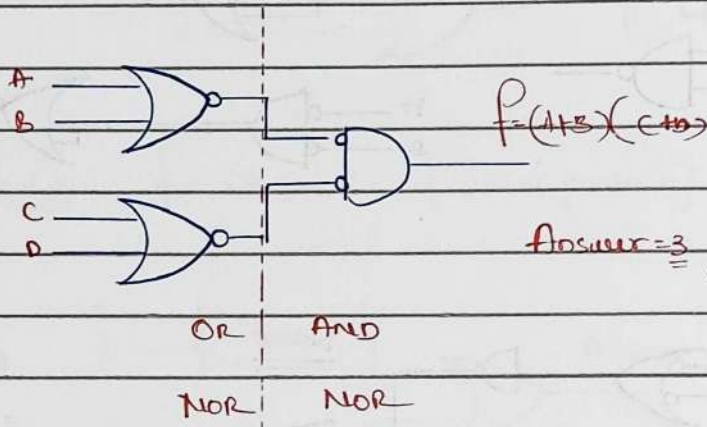
Case (5) $F = (A+B) \cdot (C+D) \rightarrow$ Product of Sum Form.



Answer = 3

Note: Whenever minimum number of NOR Gate are asked, write the function in Pos form and implement by using AND which is AND-OR Implementation which is exactly equal to NOR NOR implementation.

XOR Gate.

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


Truth Table

$A \oplus A = 0$
 $A \oplus 0 = A$
 $A \oplus 1 = \bar{A}$
 $A \oplus \bar{A} = 1$


eg::

$A \oplus B = C$
 $A \oplus C = B$
 $B \oplus C = A$
 $A \oplus B \oplus C = 0$

Enable/Disable

 


"Buffer"

 


"Inverter"

$\rightarrow A \oplus A = 0$ (for even)


$A \oplus A \oplus A = A$ (for odd)

 

Q1. Find the output y .

 


Q2. Find the output y .

 


- XOR Gate follows commutative as well as associative law
 $A \oplus B = B \oplus A$ → commutative law
 $A \oplus B \oplus C = (A \oplus B) \oplus C$ → associative law

- X-OR Gate output will be high when odd number of 1's are connected in the inputs.

ABC	$A \oplus B \oplus C$	$(A \oplus B) \oplus C$
000	0	0
001	1	1
010	1	1
011	0	0
100	1	1
101	0	0
110	0	0
111	1	1

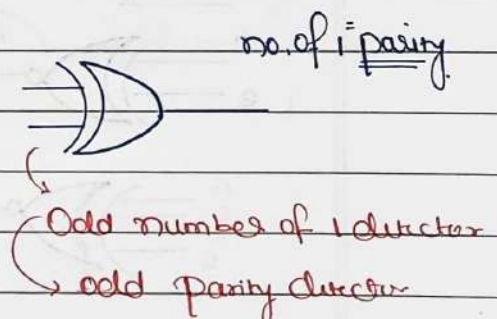

 X-NOR Gate:

$$A \oplus B = A \odot B = \overline{A \oplus B} = \overline{A \oplus B}$$

A	B	A ⊙ B
0	0	1
0	1	0
1	0	0
1	1	1

Truth Table

$$A = B \quad y = 1$$

$$A \neq B \quad y = 0$$


* It is also called as "even parity detector / Equivalence logic / Equal detector / Coincidence logic".

$$A \odot A = 1$$


$$A \odot 1 = A$$

$$A \odot \overline{A} = 0$$

$$A \odot 0 = \overline{A}$$

 


"Inverter".

 

"Buffer".

eg.:

  
 

 $x=0$ - Astable multivibrator

 $x=1$ - Bistable multivibrator.

* X-NOR Gate follows commutative as well as associative law.


* For even number of variable and even number of inputs.

Case 1:




Output will be high for even no of inputs are high.

Case 2:

 

	A	B	C	$(A \odot B) \odot C$	$A \odot (B \odot C)$
1.	0	0	0	0	0
2.	0	0	1	1	1
3.	0	1	0	1	1
4.	0	1	1	0	0
5.	1	0	0	1	1
6.	1	0	1	0	0
7.	1	1	0	0	0
8.	1	1	1	1	1

 $(A \odot B) \odot C = A \odot (B \odot C)$
 ↳ Associative Law.




* $A \odot B = \overline{A \oplus B}$
 $A \odot B \odot C \odot D = \overline{A \oplus B \oplus C \oplus D}$
 } for even! = variables

* $(A \odot B) \odot C = A \oplus B \oplus C$



$((A \odot B) \odot C) \odot D = A \oplus B \oplus C \oplus D$

 * Output will be high for ~~even~~ odd no of 1's in the input.






* Output will be high for even no of 1's in input.

Magic

  

   $A \oplus X = \overline{A}X + AX$
 $\overline{A}B + A\overline{B}$
 $\overline{A}B + AB = \overline{A \odot B}$



Same!

* $A \odot B = \overline{A \oplus B} = \overline{A \oplus \overline{B}} = \overline{A \oplus B} = \overline{A \oplus B}$

* $A \oplus B = \overline{A \odot B} = \overline{A \odot \overline{B}} = \overline{A \odot B} = \overline{A \odot B}$

Q1. The boolean function given: $f(A, B) = A \oplus B \oplus AB$
Which statement is/are correct?

$$\begin{aligned}
 f(A, B) &= (A \oplus B) \oplus AB \\
 &= \chi \oplus AB && A \oplus B = \chi = \bar{A}B + A\bar{B} \\
 &= \bar{\chi} \cdot AB + \chi \cdot \bar{AB} && \bar{A \oplus B} = \bar{\chi} = A \odot B = \bar{A}\bar{B} + AB \\
 &= [\bar{A}\bar{B} + AB] \cdot AB + [A\bar{B} + \bar{A}B] \cdot [\bar{A} + \bar{B}] \\
 &= \bar{A}\bar{B} \cdot AB + AB \cdot AB + \bar{A}B \cdot \bar{A} + A\bar{B} \cdot \bar{B} + \bar{A}B \cdot B + AB \cdot \bar{B} \\
 &= AB + \bar{A}B + AB \\
 &= AB + \bar{A}B + \bar{B}B \\
 &= A[\bar{B} + B] + \bar{A}B \\
 &= A \cdot 1 + \bar{A}B \Rightarrow \underbrace{A + \bar{A}B}_{A + \bar{A}B} = (A + \bar{A})(A + B) = \underline{A + B} \text{ (OR)}
 \end{aligned}$$

Ans: \rightarrow It is a OR Gate

\rightarrow It requires 3 NAND Gate to implement the function.

A	B	AB	$A \oplus B \oplus C$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1



$f = A + B$

Q2. Minimized expression will be $Y = A \oplus (A + B)$

$$\begin{aligned}
 A + B &= \chi \\
 A \oplus \chi &\rightarrow \text{Associative law} && A \oplus (A + B) \\
 &\text{does not follow} && (A \oplus A) + (A \oplus B) \\
 &\text{by } \chi\text{-OR Gate out} && 0 + A \oplus B \\
 &\text{OR Gate.} && A \oplus B. \\
 \bar{A} \chi + A \bar{\chi} & && \\
 \bar{A} [A + B] + A [\bar{A} + \bar{B}] & && \\
 \bar{A} \cdot A + \bar{A} \cdot B + A \cdot \bar{A} + A \cdot \bar{B} & && \\
 = \underline{\underline{\bar{A}B}} & &&
 \end{aligned}$$

A	B	A	χ (A+B)	$A \oplus \chi$	$A \oplus (A + B)$
0	0	0	0	0	
0	1	0	1	1	
1	0	1	1	0	
1	1	1	1	0	

eg::

  f will be 1.

Laws of Boolean Algebra

Boolean function: It is the combination of inputs on which output depends.

eg: $f(A, B) = \underline{AB} + \underline{\bar{A}\bar{B}}$

No. of variables = 2

No. of terms = 2, Literals = 4

Function.

SOP

POS

Sum of Product
(Minterm)Product of Sum
(Maxterm)

Standard Canonical Form

Each term should contain all the variables

eg: $f(A, B) = \bar{A}B + A\bar{B}$ ✓
 $f(A, B) = A + \bar{A}B$

Decimal	ABC	Min Term	Max Term	Functions
0	000	$\bar{A}\bar{B}\bar{C}$	$A+B+C$	1
1	001	$\bar{A}\bar{B}C$	$A+B+\bar{C}$	0
2	010	$\bar{A}B\bar{C}$	$A+\bar{B}+C$	1
3	100	$A\bar{B}\bar{C}$	$A+\bar{B}+\bar{C}$	1
4	100	$A\bar{B}\bar{C}$	$\bar{A}+B+C$	0
5	101	$A\bar{B}C$	$\bar{A}+B+\bar{C}$	0
6	110	$AB\bar{C}$	$\bar{A}+\bar{B}+C$	0
7	111	ABC	$\bar{A}+\bar{B}+\bar{C}$	1

Standard Canonical SOP form:

$$\begin{aligned}
 f(A,B,C) &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} \\
 &= m_0 + m_2 + m_3 + m_7 \\
 &= \sum m(0, 2, 3, 7) \\
 &= \Sigma(0, 2, 3, 7)
 \end{aligned}$$

Standard Canonical POS form:

$$\begin{aligned}
 F(A,B,C) &= (A+B+C)(\bar{A}+B+C)(\bar{A}+B+\bar{C})(\bar{A}+\bar{B}+C) \\
 &= \pi_1 \cdot \pi_9 \cdot \pi_2 \cdot \pi_6 \\
 &= \pi M(1, 4, 5, 6) \\
 &= \pi(1, 4, 5, 6)
 \end{aligned}$$

Q1. No. of terms present in Standard Canonical form (SOP)?

Ans.

$$\begin{aligned}
 f(A,B,C) &= A+BC \\
 &= A(\bar{B}+B)(\bar{C}+C) + (\bar{A}+A)BC \\
 &= A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C + ABC + \bar{A}BC \\
 \therefore & \text{ 5 terms are present.}
 \end{aligned}$$

① Distribution Theorem

$$\begin{aligned}
 &(A+B)(A+C) \\
 &= A.A + A.C + AB + BC \\
 &= A + AC + AB + BC
 \end{aligned}$$

$$= A[1+C+B] + BC$$

$$= A \cdot 1 + BC$$

$$= A + BC$$

$$A + BC = (A+B) \cdot (A+C)$$

$$\text{eg: } A + \overline{A}B$$

$$(A + \overline{A})(A + B)$$

$$= 1(A+B)$$

$$= A+B$$

$$Q_2. f(A, B) = \overline{A} + \overline{A}B$$

$$= (\overline{A} + A)(\overline{A} + B)$$

$$= \overline{A} + B$$

2. Consensus Theorem

$$f(A, B, C) = AB + \overline{A}C + BC$$

$$= AB + \overline{A}C + (\overline{A}B + A)BC$$

$$= AB + \overline{A}C + \overline{A}BC + ABC$$

$$= AB[1+C] + \overline{A}C[1+B]$$

$$= AB + \overline{A}C$$

$BC \rightarrow$ Redundant term

* 3 variable function

* each term consist of 2 variables.

* each variable repeated twice except one

* One variable repeated in form of complement.

$$\text{eg: } AB + \overline{B}C + AC$$

$$\Rightarrow AB + \overline{B}C$$

$AC \rightarrow$ redundant.

3. Transpose Theorem

$$(A+B)(\overline{A}+C)$$

$$= A\overline{A} + AC + \overline{A}B + BC$$

$$= AC + \overline{A}B + BC$$

$$= AC + \overline{A}B$$

$$(A+B)(\overline{A}+C)$$

$$= AC + \overline{A}B$$

4. De Morgans Law

$$\overline{ABC} = \overline{A} + \overline{B} + \overline{C}$$

$$\overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

Q1. Find min. no of NAND Gate required to implement $f(A, B, C) = A + ABC + \overline{A}BC$.

$$A[1+BC+\overline{B}C] = A$$

\therefore 0 NAND Gate required.

Q2. Find the minimum no. of NAND gate required to implement the boolean function

Ans $f(A,B,C) = A + ABC + ABC$
 $= A [1 + BC + BC]$
 $= A$
 \therefore 0 NAND Gate required

Q3. Minimize the expression $f(A,B) = A + AB$

Ans $= A [1 + B]$
 $= A$


Q4. Minimize the expression $f(A,B) = \bar{A}\bar{B} + \bar{A}B + AB$

Ans $= \bar{A} [\bar{B} + B] + AB$
 $= \bar{A} + AB = (\bar{A} + A) (\bar{A} + B)$
 $= \bar{A} + B$

Q5. Minimize the expression $f(A,B) = \bar{A}\bar{B} + \bar{A}B + AB + AB$

Ans $= \bar{A} [\bar{B} + B] + A [\bar{B} + B]$
 $= \bar{A} + A \Rightarrow 1$

$n=1$	}	$n=2$	}	<table border="1" style="border-collapse: collapse; text-align: center;"> <tr><td>$\bar{A}\bar{B}$</td><td>$\bar{A} + \bar{B}$</td><td>A</td><td>0</td></tr> <tr><td>$\bar{A}B$</td><td>$\bar{A} + B$</td><td>\bar{A}</td><td>1</td></tr> <tr><td>$A\bar{B}$</td><td>$A + \bar{B}$</td><td>B</td><td>$\bar{A}B + AB$</td></tr> <tr><td>AB</td><td>$A + B$</td><td>\bar{B}</td><td>$\bar{A}\bar{B} + AB$</td></tr> </table>	$\bar{A}\bar{B}$	$\bar{A} + \bar{B}$	A	0	$\bar{A}B$	$\bar{A} + B$	\bar{A}	1	$A\bar{B}$	$A + \bar{B}$	B	$\bar{A}B + AB$	AB	$A + B$	\bar{B}	$\bar{A}\bar{B} + AB$
$\bar{A}\bar{B}$	$\bar{A} + \bar{B}$	A	0																	
$\bar{A}B$	$\bar{A} + B$	\bar{A}	1																	
$A\bar{B}$	$A + \bar{B}$	B	$\bar{A}B + AB$																	
AB	$A + B$	\bar{B}	$\bar{A}\bar{B} + AB$																	
A	4	$\bar{A}\bar{B}$	16 different terms																	
\bar{A}		$\bar{A}B$																		
1		$A\bar{B}$																		
0		AB																		
		<div style="display: flex; justify-content: space-around; width: 100%;"> minterms maxterms </div>																		

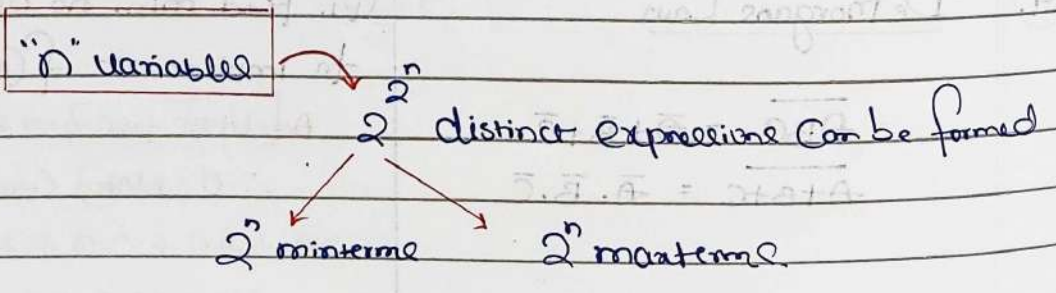

Q6. Minimize the expression $f(A, B) = \bar{A}B + A\bar{B} = A \oplus B$.
 Ans. Already minimized

Q7. Minimize the expression: $f(A, B) = AB + \bar{A}C + BC$
 ↪ function written in wrong format.

$$\begin{aligned} \text{eg: } f(A, B, C) &= \overset{001}{\bar{A}\bar{B}C} + \overset{010}{\bar{A}B\bar{C}} + \overset{100}{A\bar{B}\bar{C}} + \overset{111}{ABC} \\ &= \sum (1, 2, 4, 7) \\ &= A \oplus B \oplus C \quad (\text{Already Minimized}) \end{aligned}$$

$$\begin{aligned} \text{eg: } f(B, A) &= \overset{01}{\bar{A}B} + \overset{10}{A\bar{B}} + \overset{11}{AB} = \sum m(1, 2, 3) \times \\ &\quad \uparrow \uparrow \\ &= B\bar{A} + \bar{B}A + BA = \sum m(1, 2, 3) \checkmark \end{aligned}$$

↪ note the order, function should be written in same order.

Q8. Minimize the expression: $f(A, B, C) = \bar{A}\bar{B} + \bar{A}C + \bar{B}C$
 Ans. $= \bar{A}C + \bar{B}C$

Q9. Minimize the expression: $f(A, B, C) = (A+B)(A+C)(\bar{B}+C)$
 Ans. $= (A+B)(\bar{B}+C)$

Q10. Write the function for truth table and minimize it.

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	1

SOP form:

$$Y = \bar{A}\bar{B} + \bar{A}B\bar{C} + A\bar{B}C + AB$$

$$Y = \bar{A}\bar{B} + \bar{A}B + AB$$

$$Y = \bar{A}\bar{B} + A(\bar{B}+B)$$

$$Y = \bar{A}\bar{B} + A = (A+\bar{A})(A+\bar{B})$$

$$Y = A + \bar{B}$$

Pos:

$$Y = (A+B+1) \cdot (A+B\bar{C}) \cdot (\bar{A}+1)$$

$$(A+B+1)$$

$$= 1(A+B) \cdot 1 \cdot 1$$

$$= \underline{A + \bar{B}}$$

Q11. Write the function for truth table and minimize it.

Ans.

A	B	Y
0	0	C
0	1	\bar{C}
1	0	1
1	1	1

Sol:

$$y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B} + AB$$

Q12. Two way switch is an example of which logic?

Ans. X-OR

Q13. If we have 4 variable, then total different expressions will be?

Ans.

$$2^{2^n} = 2^{2^4} = 2^{16} = 2^6 \times 2^{10} = \underline{\underline{64K}}$$

Q14. $A + BC + \bar{A}C$ is equal to :

$$A + BC + \bar{A}C$$

$$= (A + \bar{A})(A + C) + BC$$

$$= A + C + BC$$

$$= A + C [1 + B]$$

$$= \underline{\underline{A + C}} \quad (\text{not in option!})$$

eg: $f = AB + \bar{A}\bar{B} + ABC + \bar{A}\bar{B}\bar{C}$

$$= AB[1 + C] + \bar{A}\bar{B}[1 + \bar{C}]$$

$$= AB + \bar{A}\bar{B} \quad \text{--- (Semi minimized)} \rightarrow AB + \bar{A}\bar{B} + \bar{A}\bar{B}C$$

Modified Venned Diagram

↳ It is also known as "K-map".

Minimization by K-map

* Based on graycode

* Graycode:


Binary → B₃ B₂ B₁ B₀



Graycode → G₃ G₂ G₁ G₀

eg: Binary: 0110101
Gray code: 0101111

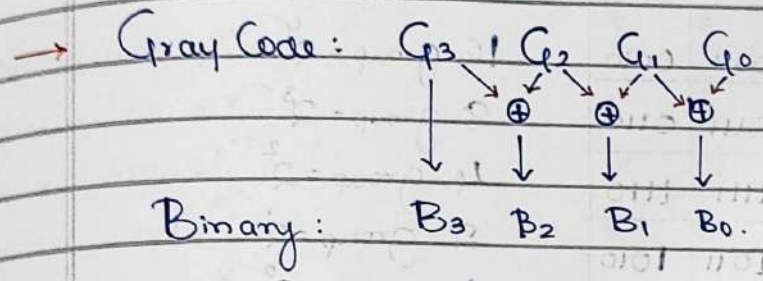
eg: Binary: 111001011
Gray code: 100101110



eg: Gray Code: 1101011
Binary: 1001101

Gray Code: Gray code is the code in which successive numbers differ by 1 bit.

Decimal	Binary	Gray Code
0	00	00
1	01	01
2	10	11
3	11	10

 

1. Unity Hamming distance code
2. Cyclic code
3. Reflecting code

Decimal	Binary	Gray Code
0	000	000
1	001	001
2	010	011
3	011	010
4	100	110
5	101	111
6	110	101
7	111	100

* eg: $f(A, B)$

MSB (Most significant bit) LSB (Least significant bit)

	\bar{B}	B
\bar{A} 0	$\bar{A}\bar{B}$ 00 ①	$\bar{A}B$ 01 ②
A 1	$A\bar{B}$ 10 ③	AB 11 ④

→ $f(A, B, C)$

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A} 0	000 0	001 1	011 3	010 2
A 1	100 4	101 5	111 7	110 6

$f(A, B, C, D)$

* Group can be formed in order of 2^n .

		$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	00	0000	0001	0011	0010
$\bar{A}B$	01	0100	0101	0111	0110
AB	11	1100	1101	1111	1110
$\bar{A}\bar{B}$	10	1000	1001	1011	1010

- 16 group = 2^4 → 4 variable reduce
- 8 group = 2^3 → 3 variable reduce
- 4 group = 2^2 → 2 variable reduce
- 2 group = 2^1 → 1 variable reduce
- 1 group = 2^0 → 0 variable reduce


Rule of Minimization:

Termen celi minimise

Cy Baba Rule: Kam se kam group banana hai and bade se bade group banana hai.

Variable celi minimize.

Quad (making group)

 

And many similar combinations possible

etc.

Q1. $f(A, B) = \bar{A}\bar{B} + \bar{A}B + AB = \sum m(0, 1, 3)$

		\bar{B}	B
\bar{A}	0	1	1
A	1	0	1

$f(A, B) = \bar{A}\bar{B} \cdot 1 + \bar{A}B \cdot 1 + A\bar{B} \cdot 0 + AB \cdot 1$
 $\Rightarrow \bar{A}\bar{B}$

Q2 $f(A,B) = \bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB = \sum m(0,1,2,3)$

	\bar{B}	B
\bar{A}	1	1
A	1	1

$\Rightarrow 1$

Q3 $f(A,B,C) = \sum m(0,1,3,6,7)$

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
	00	01	11	10
\bar{A}	1	1	1	0
A	0	0	1	1

$\bar{A}\bar{C}$ (grouping 0,1,2,3)
 $\bar{A}B$ (grouping 0,1)
 $A\bar{C}$ (grouping 3,7)
 AB (grouping 3,7)

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
	00	01	11	10
\bar{A}	1	1	1	0
A	0	0	1	1

$$= \bar{A}\bar{B} + \bar{A}B + \bar{A}BC$$

Semi minimized
expression.

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
	00	01	11	10
\bar{A}	1	1	1	0
A	0	0	1	1

$\bar{A}\bar{B}$ (grouping 0,1)
 AB (grouping 3,7)
 BC (grouping 3,7)

$$= \bar{A}\bar{B} + AB + BC$$

Question Practice Session

Q1. If $x \odot y = \bar{x} + y$ and $z = x \odot y$ Then $z \odot y$ will be:

$$\begin{aligned} z \odot y &= \bar{z} + y = \overline{x \odot y} + y \\ &= \overline{\bar{x} + y} + y = \bar{x} \cdot \bar{y} + y \\ &= \bar{x} \cdot \bar{y} + y \\ &= (\bar{x} + y)(\bar{y} + y) \\ &= \underline{\underline{\bar{x} + y}} \end{aligned}$$

Q2. If $A * B = AB + \bar{A}\bar{B}$ and $C = A * B$. Then which one is correct?

$$A \odot B = AB + \bar{A}\bar{B}$$

$$C = A \odot B$$

$$(A \odot B) \odot (A \odot B)$$

$$B \odot C = A$$

$$x \odot x = 1$$


(i) $A = B * C$ ✓

(ii) $B = A * C$ ✓

(iii) $A \odot B \odot C = 1$ ✗


(iv) $A = B$ ✗

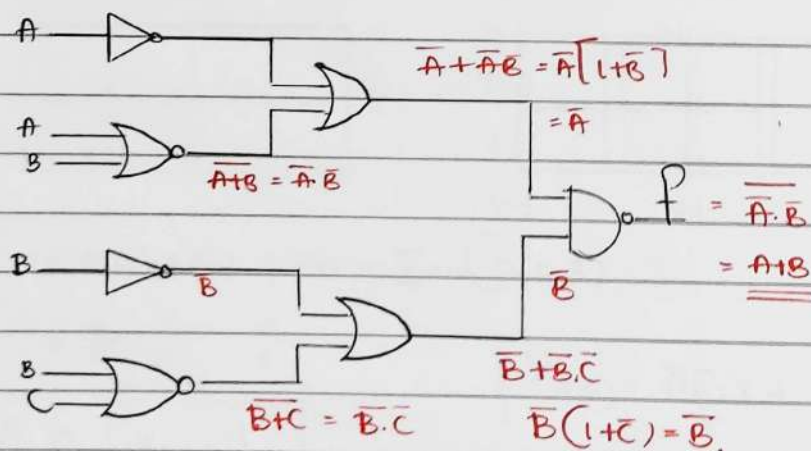Q3. The output for the given logic circuit will be:




$$\Rightarrow \underline{\underline{F = A+B}}$$

 Q4. Consider the given logic circuit with the inputs A, B and C then $f(A, B, C)$ will be.



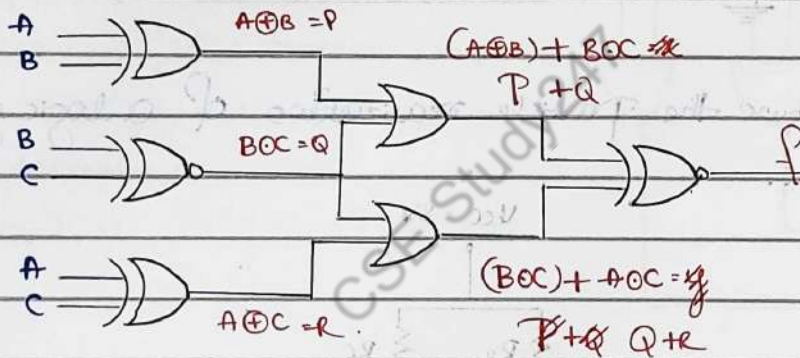Q5. The output for the given logic circuit will be:



$$f = \bar{P}\bar{Q}\bar{R} + P\bar{Q}\bar{R} + P\bar{Q}R + P\bar{Q}R + Q\bar{R}$$

$$f = \bar{P}\bar{Q}\bar{R} + Q[P + R] + PR$$

$$f = \bar{P}\bar{Q}\bar{R} + Q + PR$$

$$= \bar{P}\bar{Q}\bar{R} + Q + PR$$

$$= (\bar{P}\bar{Q} + Q) + PR$$

$$f = \bar{P}\bar{R} + PR + Q \Rightarrow (\bar{P}\bar{R}) + Q$$


A \ BC	00	01	11	10
0	1		1	
1	1		1	

$$f = \bar{P}\bar{R} + PR$$


$$= \underline{\underline{B \oplus C}}$$

ABC	P A ⊕ B	Q B ⊕ C	R A ⊕ C	x	y	x ⊕ y
000	0	1	0	1	1	1
001	0	0	1	0	1	0
010	1	0	0	1	0	0
011	1	1	1	1	1	1
100	1	1	1	1	1	1
101	1	0	0	1	0	0
110	0	0	1	0	1	0
111	0	1	0	1	1	1

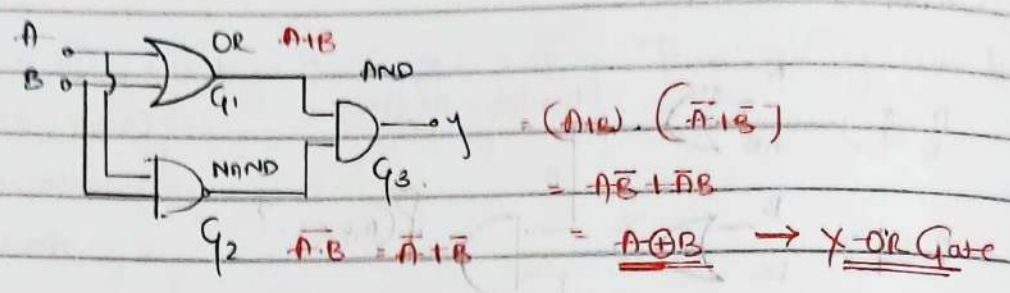Q6. The following logic gate circuit equivalent to




Note:

 


A	Transistor	Y
0	cutoff	1
1	Saturation	0

} NOT Gate!

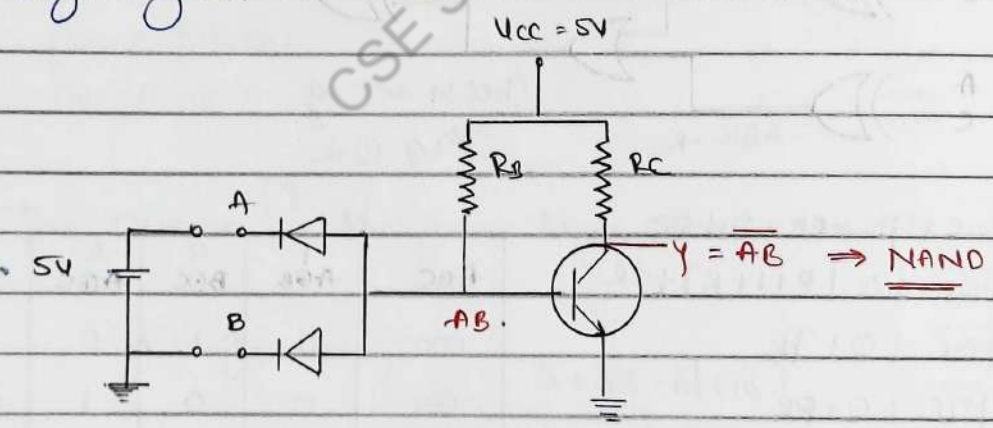
Q7. Figure shows the particle realization of a logic gate. Identify the logic gate.



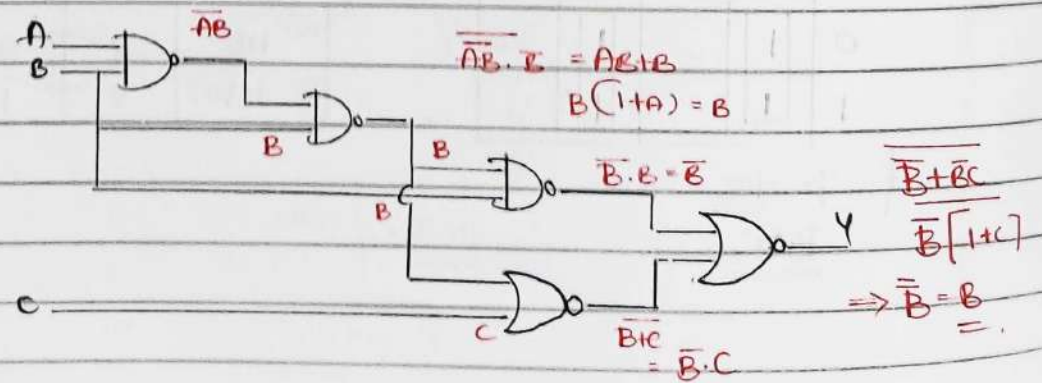Q8. For the logic circuit shown, the simplified boolean expression for the output y is.




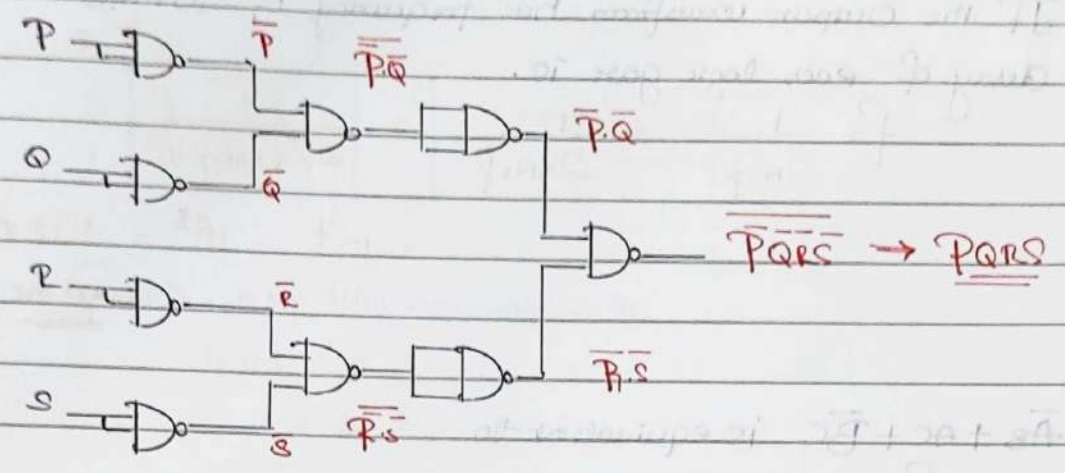Q13. For the circuit shown in fig. the boolean expression for the output y in terms of inputs P, Q, R and S is.



Q14. $A_3, A_2, A_1, A_0, B_3, B_2, B_1, B_0$ is shown in figure. To get output $y=0$, choose one pair of correct input numbers.

$\Rightarrow 0010, 1011$

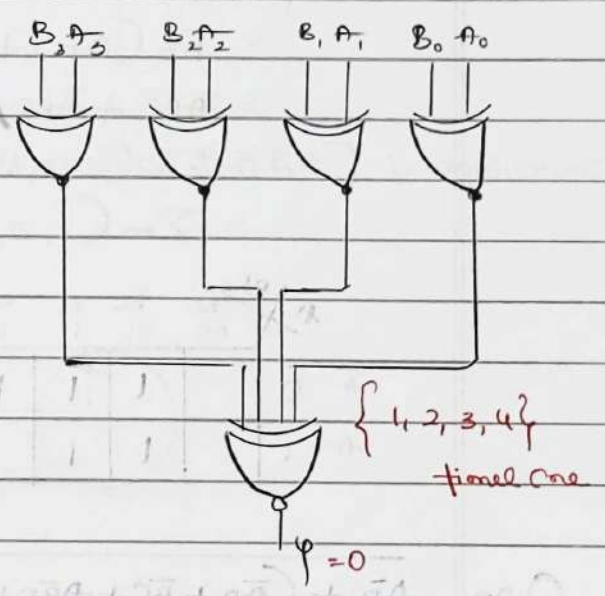


Q15. The minimum number of two input NAND gate required to implement $y = abcd$ is.

$y = abcd$

$NAND = (2^n - 2) + k = (2^{(4)} - 2) + 0 = 6$

 Q16. All the logic gates in the circuit shown below, have equal finite propagation delay.



Q17. The circuit can be used as a clock generator, if $x=1$

Q18. If the output waveform has frequency of 10 MHz the propagation delay of each logic gate is.

$$f = \frac{1}{2N \tau_{pd}} = \frac{1}{2 \times N \times \tau_{pd}} = \frac{1}{2 \times 5 \times 10 \times 10^6}$$

$$= \frac{10^{-7}}{10} = 10^{-8} = 10 \times 10^{-9}$$

$$= \underline{\underline{10 \text{ ns}}}$$

Q19. $\overline{AB} + AC + \overline{BC}$ is equivalent to

$$f = \overline{AB} + AC + \overline{BC}$$

$$= \overline{AB} (\overline{C} + C) + A (\overline{B} + B) C + (\overline{A} + A) BC$$

$$= \overline{AB} \overline{C} + \overline{AB} C + A \overline{B} C + ABC + \overline{A} BC + A \overline{B} C$$

$$= \sum m (2, 3, 5, 7, 1)$$

$$= \sum m (1, 2, 3, 5, 7)$$

A \ BC	\overline{BC} 00	$\overline{B}C$ 01	$B\overline{C}$ 11	BC 10	
\overline{A} 0		1	1	1	$\Rightarrow C + \overline{AB}$
A 1		1	1		

Q20. $\overline{AB} + (\overline{A}B + \overline{B}C + A\overline{B}D + A\overline{B}\overline{D})$ is equal to

$$\overline{AB} + \overline{A}B + \overline{B}C + A\overline{B}D + A\overline{B}\overline{D}$$

$$\overline{AB} [1 + D + \overline{D}] + \overline{A}B + \overline{B}C$$

$$\overline{AB} + \overline{A}B + \overline{B}C$$

$$\overline{A} \cdot \overline{A}B \cdot \overline{B}C$$

$$(\overline{A} + A) (\overline{A} + B) (B + \overline{C})$$

$$(\overline{A} \cdot A + \overline{A}B + AB + BB) (B + \overline{C})$$

$$(\overline{A}B + AB) (B + \overline{C})$$

$$\overline{A}B B + AB B + \overline{A}B \overline{C} + AB \overline{C}$$

$$AB [1 + \overline{C}] + \overline{A}B \overline{C}$$

$$\Rightarrow \underline{\underline{AB + \overline{A}B \overline{C}}}$$

Q21. $(\overline{A} + \overline{B})(\overline{B} + C)$ is equal to :

$$\overline{A} \overline{B} + \overline{B} C$$

$$= \overline{A} \overline{B} + \overline{B} C$$

$$\Rightarrow \underline{\underline{B(A + C)}}$$

Q22. $\bar{A}\bar{B} + AC + \bar{B}C$ is equivalent to

$$\bar{A}\bar{B}(\bar{C}+C) + A(\bar{B}+B) + (\bar{A}+A)\bar{B}C$$

$$\Sigma_m(0, 1, 5, 7)$$

A \ BC	00	01	11	10
0	1	1		
1		1	1	

$$\Rightarrow \underline{\bar{A}\bar{B} + AC}$$

Q23. $(A+B)(A+C)(A+\bar{C})$ is equivalent to

$$(A+BC)(A+\bar{C})$$

$$= A + BC\bar{C}$$

$$\Rightarrow \underline{A}$$

HW

Q24. A logical function is given as

$$F(A, B, C, D) = \bar{B}\bar{C} [A + B\bar{C}D + \bar{B}CD + \bar{A}\bar{B}\bar{C}] \text{ is equivalent to}$$

Q25. $f(A, B, C) = \Sigma_m(0, 1, 3, 5, 6, 7)$

A \ BC	00	01	11	10
0	1	1	1	
1		1	1	1

$$= \bar{A}\bar{B} + AB + C$$

Q26. $f(A, B, C) = \Sigma_m(0, 2, 4, 6)$

A \ BC	00	01	11	10
0	1			1
1	1			1

$$\bar{C} \Rightarrow \bar{C}$$

Q27. $f(A, B, C) = \Sigma_m(0, 3, 5, 6)$

A \ BC	00	01	11	10
0	1		1	
1		1		1

Q28 $f(A, B, C, D) = \sum (0, 2, 4, 6, 10, 11, 13, 15)$

AB \ CD	00	01	11	10
$\bar{A}\bar{B}$ 00	1			1
$\bar{A}\bar{B}$ 01	1			1
$\bar{A}\bar{B}$ 11		1	1	
$\bar{A}\bar{B}$ 10			1	1

$\bar{A}\bar{D}$ 11 $\Rightarrow \bar{A}\bar{D} + ABD + \bar{A}\bar{B}C$
 ABD
 $\bar{A}\bar{B}C$

Q29 $f(A, B, C, D) = \sum m (0, 1, 2, 4, 6, 9, 10, 11, 12, 13, 15)$

AB \ CD	00	01	11	10
$\bar{A}\bar{B}$ 00	1	1		1
$\bar{A}\bar{B}$ 01	1			1
$\bar{A}\bar{B}C$ $\bar{A}B$ 11	1	1	1	
$\bar{A}\bar{B}$ 10		1	1	1

$\bar{A}\bar{D}$
 $\Rightarrow \bar{A}\bar{D} + AD + \bar{A}\bar{B}C + \bar{A}\bar{B}C + \bar{A}\bar{B}C$
 $\bar{A}\bar{B}C$ AB $\bar{A}\bar{B}C$

Q30 $f(A, B, C, D) = \sum m (1, 5, 6, 7, 11, 12, 13, 15)$

AB \ CD	00	01	11	10
$\bar{A}\bar{B}$ 00		1		
$\bar{A}\bar{B}$ 01		1	1	1
$\bar{A}\bar{B}$ 11	1	1	1	
$\bar{A}\bar{B}$ 10			1	

$\Rightarrow \bar{A}\bar{B}C + \bar{A}\bar{C}D + \bar{A}B + AD$

Q31 $f(A, B, C, D) = \sum m (1, 2, 5, 6, 8, 10, 12, 13, 14, 15)$

AB \ CD	$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$C\bar{D}$ 11	CD 10
$\bar{A}\bar{B}$ 00		1		1
$\bar{A}\bar{B}$ 01		1		1
$\bar{A}\bar{B}$ 11	1	1	1	1
$\bar{A}\bar{B}$ 10	1			1

$\Rightarrow AB + \bar{C}\bar{D} + \bar{A}\bar{D} + \bar{A}\bar{C}D$
 Quad $\bar{A}\bar{D}$

Q.32 $f(A,B,C,D) = \sum m(1,5,6,7,11,12,13,15)$

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	1	1	1
10	1	1	1	1
11	1		1	1

$\Rightarrow \bar{A} + B + C + \bar{D}$

eg::

AB \ CD	00	01	11	10
00	1	1		1
01		1	1	
11	1	0		1
10	1	0		1

$\Rightarrow \bar{B}\bar{D} + B\bar{C}\bar{D} + \bar{A}B\bar{D} + A\bar{C}\bar{B} + \bar{A}\bar{B}C$

$\Rightarrow \bar{B}\bar{D} + B\bar{C}\bar{D} + \bar{A}B\bar{D} + A\bar{C}\bar{D} + \bar{A}\bar{C}D$

Don't Care Conditions:

Combination of inputs on which the output may or maynot depends are called don't care conditions.

$f(A,B) = \bar{A}B + AB$

Q.1 $f(A,B,C) = \sum m(0,1,6,7) + \sum d(3)$

A \ BC	00	01	11	10
0	1	1	X	
1			1	1

$\Rightarrow \bar{A}B + AB$

$f(A,B,C) = \sum m(0,1,2) + \sum d(3,6)$

A \ BC	00	01	11	10
0	1	1	X	1
1				X

eg::

A \ BC	00	01	11	10
0	1	X	X	X
1			X	X

$\Rightarrow \bar{A}$

A \ BC	00	01	11	10
0	X	1	1	
1		X	1	X

$\Rightarrow C$

Q2. $f(A, B, C, D) = \sum m(0, 2, 4, 6, 7, 8, 10, 11, 12, 14, 15) + \sum d(1, 3)$

AB \ CD	00	01	11	10
00	1	x	x	1
01	1		1	1
11	1		1	1
10	1		1	1

$\Rightarrow C + \bar{D}$

eg.:

AB \ CD	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	AB
$\bar{A}\bar{B}$	00	01	11	10
$\bar{A}B$	00	1	x	1
$\bar{A}\bar{B}$	01		1	x
AB	11	x	1	
$A\bar{B}$	10	x		1

$\Rightarrow \bar{A}\bar{B} + \bar{B}\bar{D} + BCD$

AB \ CD	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	AB
$\bar{A}\bar{B}$	00	01	11	10
$\bar{A}\bar{B}$	00	1	1	
$\bar{A}B$	01	1	x	1
AB	11	x	1	1
$A\bar{B}$	10		1	

$\Rightarrow \bar{A}\bar{B}\bar{C} + BC + ACD$

Q3. $F(A, B, C) = \prod m(0, 1, 3, 6, 7) = \sum m(2, 4, 5)$

M1:

A \ BC	$B\bar{C}$	$B\bar{C}$	$B\bar{C}$	$\bar{B}C$
\bar{A}	00	01	11	10
$\bar{A}\bar{A}$	0	0	0	1
$\bar{A}A$	1	1	0	0

M2 (Method 2)

A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	00	01	11	10
$\bar{A}\bar{A}$	0	0	0	1
$\bar{A}A$	1	1	0	0


Pos. $\left\{ \begin{aligned} F &= (A+B) \cdot (\bar{A}+\bar{B}) \cdot (A+\bar{C}) \\ F &= (A+B) \cdot (\bar{A}+\bar{B}) \cdot (\bar{B}+\bar{C}) \end{aligned} \right.$

SOP $\left\{ \begin{aligned} f &= \bar{A}\bar{B} + \bar{A}B\bar{C} \end{aligned} \right.$

$\bar{F} = \bar{A}\bar{B} + AB + \bar{A}C$

$F = \overline{\bar{A}\bar{B} + AB + \bar{A}C}$

 $F = (A+B) \cdot (\bar{A}+\bar{B}) \cdot (A+\bar{C})$



Q4. $f(A, B, C, D) = \sum m(0, 1, 3, 6, 7, 10, 11)$ minimize it in Pos form
 $= \prod M(2, 4, 5, 8, 9, 12, 13)$

		CD			
		$C\bar{D}$	$C\bar{D}$	$\bar{C}\bar{D}$	$\bar{C}D$
		00	01	11	10
$A\bar{B}$	00	1	1	1	0
$A\bar{B}$	01	0	0	1	1
$\bar{A}\bar{B}$	11	0	0	0	0
$\bar{A}\bar{B}$	10	0	0	1	1

$F = (\bar{B}+C) (\bar{A}+\bar{B}) (\bar{A}+C) (A+B+\bar{C}+D)$

		CD			
		$C\bar{D}$	$C\bar{D}$	$\bar{C}\bar{D}$	$\bar{C}D$
		00	01	11	10
$A\bar{B}$	00	0	0		
$A\bar{B}$	01	0	1	0	X
$\bar{A}\bar{B}$	11		X	X	
$\bar{A}\bar{B}$	10		0	0	X

$F = (A+C\bar{D}) \cdot (B+C\bar{D}) (\bar{B}+\bar{C}+\bar{D}) (\bar{A}+\bar{D})$

Variable inside the K-map.

eg:

		\bar{B}	B
		0	1
\bar{A}	0	C	C
A	1		

$\rightarrow \bar{A}\bar{B}C + \bar{A}BC$
 $= \bar{A}\bar{B}C + \bar{A}B.C = \bar{A}C(\bar{B}+B)$
 $= \bar{A}C$

eg:

		\bar{B}	B
		0	1
\bar{A}	0	1	C
A	1		

$f(A, B, C) = \bar{A}\bar{B}.1 + \bar{A}BC$
 $= \bar{A}[\bar{B}+BC]$
 $= \bar{A}[(\bar{B}+B) \cdot (\bar{B}+C)]$
 $= \bar{A}(\bar{B}+C)$

Method 1

Boolean Algebra

Method 4

Case 1: $C=0$

		\bar{B}	B
		0	1
\bar{A}	0	1	0
A	1	0	0

$= \bar{A}\bar{B}C$

Case 2: $C=1$

		\bar{B}	B
		0	1
\bar{A}	0	1	1
A	1	0	0

$\Rightarrow \bar{A}C$

$\bar{A}\bar{B}C + \bar{A}C$
 $\Rightarrow \bar{A}[C + \bar{B}C]$
 $\Rightarrow \bar{A}[(\bar{B}+C)]$
 $\Rightarrow \bar{A}(\bar{B}+C)$

Method 2

$$f(A,B,C) = \bar{A}\bar{B}(C+1) + \bar{A}BC$$

$$= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC$$

$$= \sum m(0,1,3) = \prod M(2,4,5,6,7)$$

A \ B	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
	00	01	11	10
\bar{A} 0	1	1	1	0
A 1	0	0	0	0

Sop $f = \bar{A}\bar{B} + \bar{A}C$
 $= \underline{\underline{\bar{A}(B+C)}}$

A \ B	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
	00	01	11	10
\bar{A} 0	1	1	1	0
A 1	0	0	0	0

Pos $= \underline{\underline{\bar{A}(B+C)}}$

Method 3

A \ B	\bar{B}	B
	0	1
\bar{A} 0	1	C
A 1		

$\rightarrow \underline{\underline{\bar{A}(B+C)}}$

Q1.

A \ B	\bar{B}	B
	0	1
\bar{A} 0	1	C
A 1		C

A \ B	0	1
	C=0	C=1
\bar{A} 0	1	
A 1		

A \ B	0	1
	C=0	C=1
\bar{A} 0	1	1
A 1		1

$\underline{BC + \bar{A}(B+C)}$

$\bar{A}\bar{B}\bar{C}$

$(\bar{A}+B)C$

$\bar{A}\bar{B}\bar{C} + \bar{A}C + BC$
 $\Rightarrow \bar{A}(\bar{B}\bar{C} + C) + BC$
 $\Rightarrow \underline{\underline{\bar{A}(B+C) + BC}}$

Q2.

A \ B	\bar{B}	B
	0	1
\bar{A} 0		1
A 1	C	C

A \ B	\bar{A}	A
	0	1
\bar{A} 0		1
A 1	0	0

A \ B	\bar{B}	B
	0	1
\bar{A} 0		1
A 1	1	1

$AC + B(\bar{A}+C)$

$(\bar{A}\bar{B}\bar{C})$

$(A+B)C$

$\Rightarrow \underline{AC + \bar{A}B + BC}$

$\bar{A}\bar{B}\bar{C} + AC + BC$
 $\Rightarrow \underline{AC + B(\bar{A}\bar{C} + C) = \underline{AC + B(\bar{A} + C)}}$

Implicants and Prime Implicants

- Implicants: The total number of min-terms in the boolean expression are called implicants. Or in kmap the total no. of 1 is called implicants.
- Prime Implicants: Total number of possibilities of formation of group are called prime implicants.
- Essential Prime Implicants / Selective PE: If there are two answers for a boolean expression then the terms common in both the answers are called essential prime implicants.
- Reduced Prime Implicants: The terms that are not essential prime implicants are called reduced prime implicants.

Q1. $f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$
 $= \sum m(0, 1, 3, 6, 7)$

		$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	0	1	1	1	
A	1			1	1

$$\Rightarrow \bar{A}\bar{B} + AB + \bar{A}C$$

Implicants = 5

Prime Implicants = 4

Essential prime

implicants =

		$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	0	1	1	1	
A	1			1	1

$$\Rightarrow \bar{A}\bar{B} + AB + BC$$

SPI = 1

RPI = 1

$$PI \{ \bar{A}\bar{B}, AB, \bar{A}C, BC \}$$

Q2. $f(A, B, C) = \sum m(2, 3, 4, 5, 7)$
 $PI \{ \bar{A}\bar{B}, \bar{A}B, BC, AC \}$

Q5. $f(A, B, C, D) = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$

		CD			
	AB	00	01	11	10
00			1		
01			1	1	1
11		1	1	1	
10				1	

$$P_2 \{ \bar{A}\bar{C}D, \bar{A}BC, ACD, \bar{A}BC, BD \}$$

$$\text{Implicants} = 8$$

$$P_1 = 5$$

$$EPI = 4$$

$$SPI = 0$$

$$RPI = 1$$

$$\Rightarrow \bar{A}\bar{C}D + \bar{A}BC + ACD + \bar{A}BC$$

$$EPI \{ \bar{A}\bar{C}D + \bar{A}BC + ACD + \bar{A}BC \}$$

Q6.

		BC			
	A	00	01	11	10
0		1	1	1	
1			1	1	1

$$P_1 \{ \bar{A}\bar{B} + AB + C \}$$

$$\Rightarrow \bar{A}\bar{B} + AB + C$$

$$\text{Implicants} = 6$$

$$P_1 = 3$$

$$EPI = 3$$

$$SPI = 0$$

$$RPI = 0$$


HW

Q7.

		CD			
	AB	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
		00	01	11	10
$\bar{A}\bar{B}$	00	1	1		
$\bar{A}B$	01		1	1	
AB	11			1	1
$A\bar{B}$	10				1

Q8.

		CD			
	AB	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
		00	01	11	10
$\bar{A}\bar{B}$	00	1	1		
$\bar{A}B$	01	1	1		1
AB	11		1	1	1
$A\bar{B}$	10			1	1

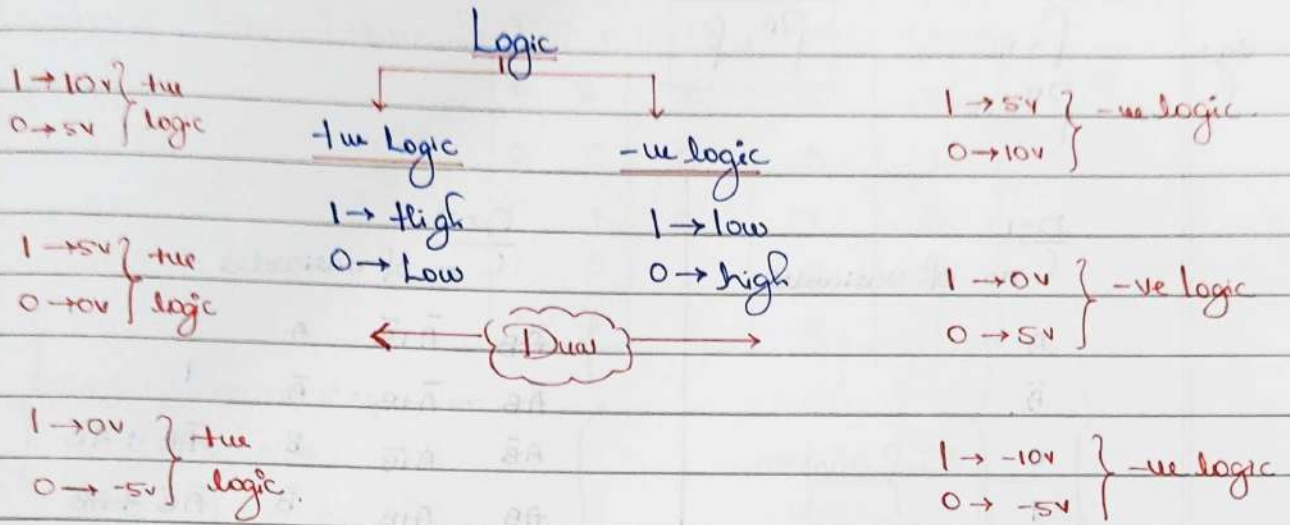

AND Case (+ve)

A	B	Y		A	B	Y
0	0	0	Logic (conversion) ↓ Dual	1	1	1
0	1	0		1	0	1
1	0	0		0	1	1
1	1	1		0	0	0

OR

Dual ⇒ +ve logic ↔ -ve logic

- | | | | |
|----|----------------------|-----------------------------------|-------------------|
| 1 | 1 ↔ 0 | 0 ↔ 1 | $f = A \cdot 1$ |
| 2 | AND ↔ OR | $A \leftrightarrow A$ | $f^0 = A + 0 = A$ |
| 3 | • ↔ + | $\bar{A} \leftrightarrow \bar{A}$ | |
| 4 | NAND ↔ NOR | | |
| 5 | X-OR ↔ X-NOR | | |
| 6 | Buffer ↔ Buffer | | |
| 7. | Inverter ↔ Inverter. | | |

eg: $f = AB + CD + \bar{E}F$ $f^0 = (A+B) \cdot (C+D) \cdot (\bar{E}+F)$	$f = \overline{ABC + DEF}$ $f^0 = \overline{(A+B+C) \cdot (D+E+F)}$
---	--

eg: $f = AB + CD$ $f^0 = (A+B) \cdot (C+D)$

↙ $f^{00} = AB + CD$

$f^{00} = f$

Q9.

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	00	01	11	10
$\bar{A}B$	01	1	1	
$A\bar{B}$	11	1		1
AB	10	1		1

$\Rightarrow \bar{B}\bar{D} + \bar{A}\bar{D} + \bar{A}\bar{D}$ (Ance 1)
 $\Rightarrow \bar{A}\bar{B} + \bar{A}\bar{D} + \bar{A}\bar{D}$ (Ance 2)

Implicants = 10
 PI = 4
 EPI = 2
 SPI = 1
 RPI = 1

Q10. Let a function F which has 3 input variables (x, y, z) . The function F will be high only when at least two of the input variables are set to high. Draw the K-map for the given function. Let the number of PI in K-map = 'a' and the no. of EPI in K-map = 'b'. Find the quadratic mean of 'a' and 'b'.

Ans:

	x	y	z	f
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

$$f(x, y, z) = \sum m(3, 5, 6, 7)$$

x \ yz	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
\bar{x}	00	01	11	10
x	0		1	
1		1	1	1

$$a = \text{PI} = 3$$

$$b = \text{EPI} = 3$$

$$f = xy + yz + xz$$

Quadratic mean:

$$= \sqrt{\frac{a^2 + b^2}{2}} = \sqrt{\frac{3^2 + 3^2}{2}} = \underline{\underline{3}}$$

Q11. Find the number of prime implicants & essential prime implicants in the given K.

yz	00	01	11	10
00	1			
01		1		1
11	1			
10		1		1

$\text{PI} = 6$
 $\text{EPI} = 6$

Q3.

	A \ BC	00	01	11	10
0		1	1	1	
1		1		1	1

$f(A,B,C) = \sum m(0,1,3,4,6,7)$

$\Rightarrow \bar{B}\bar{C} + \bar{A}C + AB$

Implicants = 6

PI = 6

EPI = 0 (term common in both)

SPI = 3

RPI = 3.

PI { $\bar{A}\bar{B} + BC + \bar{A}C + \bar{B}\bar{C} + AC + AB$ }

	A \ BC	00	01	11	10
0		1	1	1	
1		1		1	1

$\Rightarrow \bar{A}\bar{B} + BC + \bar{A}C$

Q2
(continued)

	A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A} 0				1	1
A 1		1	1	1	

$\Rightarrow A\bar{B} + \bar{A}B + AC$

Implicants = 5

PI = 4

EPI = 2

SPI = 1

RPI = 1.

EPI

	A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A} 0				1	1
A 1		1	1	1	

$\Rightarrow A\bar{B} + \bar{A}B + BC$

PI { $A\bar{B} + \bar{A}B + AC + BC$ }

Q4. $f(A,B,C) = \sum m(0,2,3,4,5,7)$

	A \ BC	00	01	11	10
0		1		1	1
1		1	1	1	

$\Rightarrow \bar{B}\bar{C} + AC + \bar{A}B$

Implicants = 6

PI = 6

EPI = 0

SPI = 3

RPI = 3

	A \ BC	00	01	11	10
0		1		1	1
1		1	1	1	

$\Rightarrow \bar{A}\bar{C} + BC + \bar{A}\bar{B}$

PI { $\bar{B}\bar{C} + AC + \bar{A}B + \bar{A}\bar{C} + BC + \bar{A}\bar{B}$ }

eg. $f = A$
 $f^D = \bar{A}$ $f^D = f$ \rightarrow Self Dual.

$n=1$ (no. of variables)	$n=2$ (no. of variables)
$\left. \begin{array}{c} A \\ \bar{A} \\ 0 \\ 1 \end{array} \right\}$ Self dual = 2	$\left. \begin{array}{cccc} \bar{A}\bar{B} & \bar{A}B & A & 0 \\ \bar{A}B & A\bar{B} & \bar{A} & 1 \\ A\bar{B} & A\bar{B} & B & \bar{A}B + A\bar{B} \\ AB & AB & \bar{B} & \bar{A}\bar{B} + A\bar{B} \end{array} \right\}$ Self dual = 4

* n variables $\rightarrow 2^{2^n}$ Expressions $\rightarrow 2^{2^n - 1}$ Self dual expressions.

Combinational Circuit.


- * A circuit without feedback or memory are called Combinational Circuit.
- * Static Circuit.

Designing of Combinational Circuit:

- Step 1: Find the number of inputs and outputs.
- Step 2: Write the truth table
- Step 3: Write the logical expression
- Step 4: Minimize the logical expression.
- Step 5: Hardware implementation.

Comparator

1. Design a one bit Comparator.

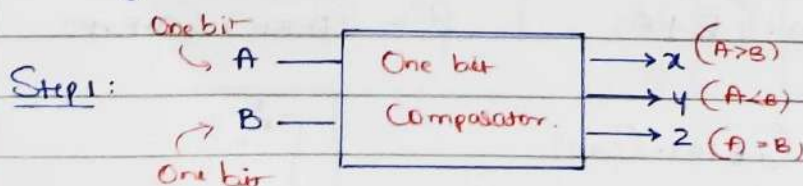

Step 2: Truth Table




		(A>B)	(A<B)	(A=B)
A	B	X	Y	Z
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

Step 3: Logical expression:

$$X(A > B) = \bar{A}B$$

$$Y(A < B) = \bar{A}B$$

$$Z(A = B) = \bar{A}\bar{B} + AB = A \odot B$$

 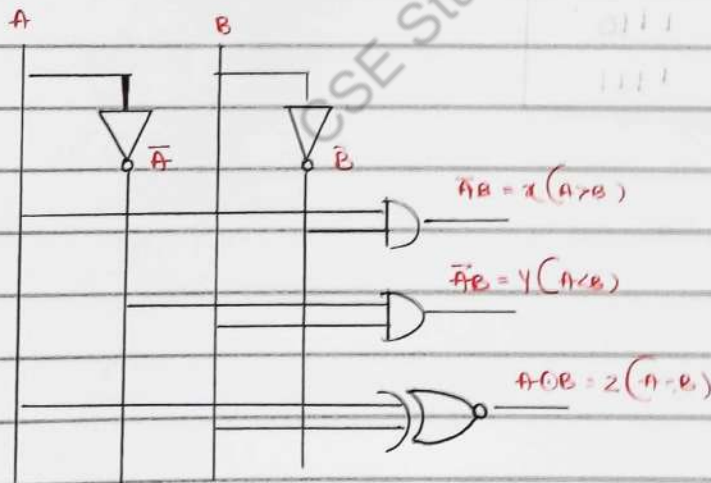 Step 4: Minimization (Already minimized)Steps: Hardware implementationTwo Bit Comparator:

Decimal	Binary	Step 2	A ₁	A ₀	B ₁	B ₀	X	Y	Z
0	0000	Truth	0	0	0	0	0	0	1
1	0001	Table	0	0	0	1	0	1	0
2	0010		0	0	1	0	0	1	0
3	0011		0	0	1	1	0	1	0
4	0100		0	1	0	0	1	0	0
5	0101		0	1	0	1	0	0	1
6	0110		0	1	1	0	0	1	0
7	0111		0	1	1	1	0	1	0
8	1000		1	0	0	0	1	0	0
9	1001		1	0	0	1	1	0	0
10	1010		1	0	1	0	0	0	1
11	1011		1	0	1	1	0	1	0
12	1100		1	1	0	0	1	0	0
13	1101		1	1	0	1	1	0	0
14	1110		1	1	1	0	1	0	0
15	1111		1	1	1	1	0	0	1

Step 3 Logical expression:

$$X (A > B) = \sum m (4, 8, 9, 12, 13, 14)$$

$$Y (A < B) = \sum m (1, 2, 3, 6, 7, 11)$$

$$Z (A = B) = \sum m (0, 5, 10, 15)$$

Step 4 Minimization

for X

		$\bar{B}_1\bar{B}_0$	\bar{B}_1B_0	$B_1\bar{B}_0$	B_1B_0
A_1A_0	00				
A_1A_0	01	1			
A_1A_0	11	1	1		1
A_1A_0	10	1	1		

for Y

		$\bar{B}_1\bar{B}_0$	\bar{B}_1B_0	$B_1\bar{B}_0$	B_1B_0
A_1A_0	00		1	1	1
A_1A_0	01			1	1
A_1A_0	11				
A_1A_0	10				1

Semiminimised

$$\begin{aligned} X(A > B) &= A_1 \bar{B}_1 + \bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 B_1 \bar{B}_0 \\ &= A_1 \bar{B}_1 + (\bar{A}_1 \bar{B}_1 + A_1 B_1) A_0 \bar{B}_0 \\ &= A_1 \bar{B}_1 + (A_1 \odot B_1) A_0 \bar{B}_0 \end{aligned}$$

Pr. 2:
A₁ A₀ B₁ B₀

	00	01	11	10
00	1			
01		1		
11			1	
10				1

Minimised

$$\begin{aligned} X(A > B) &= A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0 \\ &= A_1 \bar{B}_1 + (A_1 + B_1) A_0 \bar{B}_0 \end{aligned}$$

$$Z(A = B) = (A_1 \odot B_1) \cdot (A_0 \odot B_0)$$

Semi Minimised

$$\begin{aligned} Y(A < B) &= \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1 B_0 + A_1 \bar{A}_0 B_1 B_0 \\ &= \bar{A}_1 B_1 + (\bar{A}_1 \bar{B}_1 + A_1 B_1) \bar{A}_0 B_0 \\ &= \bar{A}_1 B_1 + (A_1 \odot B_1) \bar{A}_0 B_0 \end{aligned}$$

Minimised

$$Y(A < B) = \bar{A}_1 B_1 + (\bar{A}_1 + B_1) \bar{A}_0 B_0$$

H.W.Step 5

Hardware Implementation

CSE Study247

Comparators

<u>One bit Comparator</u>	<u>Two bit combinations</u>	<u>Three bit comparators</u>
Total Conditions = 4	Total conditions = 16	Total combinations = 64
Equal Condition = 2	Equal condition = 4	Equal condition = 8
Unequal condition = 2	Unequal " = 12	Unequal " = 56
Greater = less Cond = 1	Greater = less " = 6	Greater = less " = 28


'N' bit Comparators

$$\text{Total Condition} = 2^{2n}$$

$$\text{Equal Condition} = 2^n$$

$$\text{Unequal Condition} = 2^{2n} - 2^n$$

 
$$\text{Greater = less} = \frac{2^{2n} - 2^n}{2}$$



$$X (A > B) = A_1 \bar{B}_1 + (A_1 \odot B_1) A_0 \bar{B}_0$$

$$Y (A < B) = \bar{A}_1 B_1 + (A_1 \odot B_1) \bar{A}_0 B_0$$

 
$$Z (A = B) = (A_1 \odot B_1) \cdot (A_0 \odot B_0)$$




$$X (A > B) = A_2 \bar{B}_2 + (A_2 \odot B_2) A_1 \bar{B}_1 + (A_2 \odot B_2) (A_1 \odot B_1) A_0 \bar{B}_0$$

$$Y (A < B) = \bar{A}_2 B_2 + (A_2 \odot B_2) \bar{A}_1 B_1 + (A_2 \odot B_2) (A_1 \odot B_1) \bar{A}_0 B_0$$

$$Z (A = B) = (A_2 \odot B_2) (A_1 \odot B_1) (A_0 \odot B_0)$$

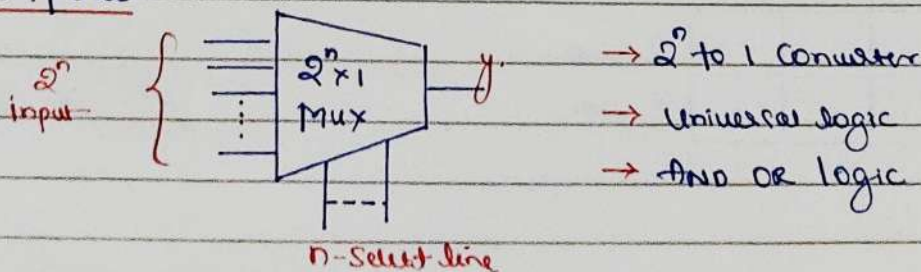Multiplexer

Q1. Design a 2x1 Mux.

 


Step 2:


S_0	Y
0	I_0
1	I_1

Step 3: $Y = \bar{S}_0 I_0 + S_0 I_1$

Step 4: Already Minimized

 

Q2. Design a 4x1 Mux.

 


Step 2:

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


Step 3: $Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$

Step 4: No minimization

 


Type: 1 Designing of higher order mux by using lower order mux.

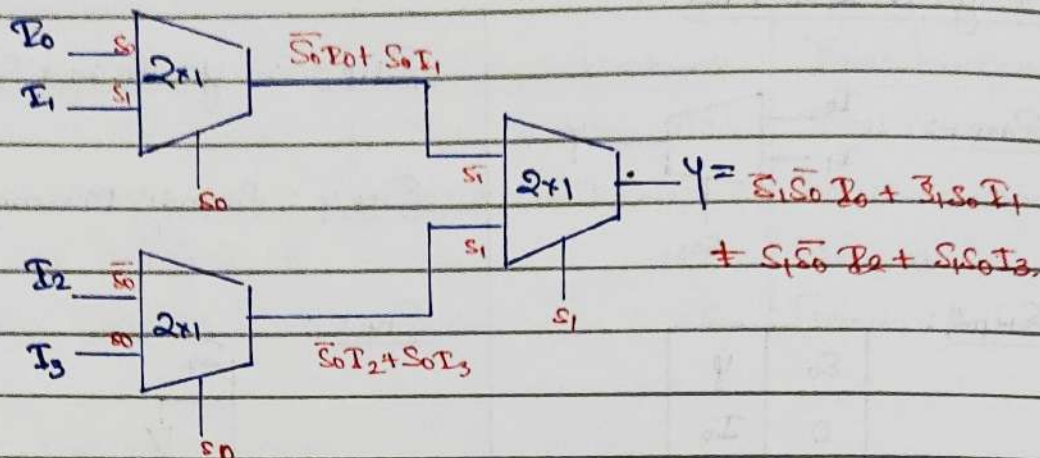eg. $2 \times 1 \text{ Mux} \xrightarrow{\frac{4^2}{2} + \frac{2^1}{2}} 4 \times 1 \text{ mux}$
 $2 + 1 = 3$



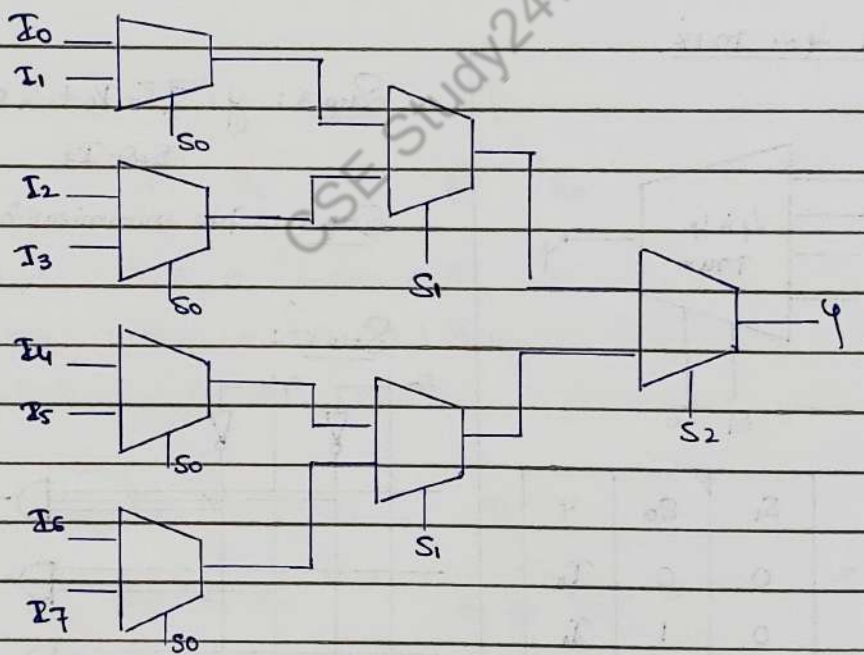eg: 2 2x1 mux $\frac{8}{2} + \frac{4}{2} + \frac{2}{2}$ 8x1 mux
 $4 + 2 + 1 = 7.$




eg: 3 2x1 mux $\frac{16}{2} + \frac{8}{2} + \frac{4}{2} + \frac{2}{2}$ 16x1 mux
 $8 + 4 + 2 + 1 = 15$

2x1 mux 63 → 64x1 mux

2x1 mux $2^n - 1$ → 2^n x1 mux


Q1. 4×1 Mux $\frac{8}{4} + \frac{8}{4} \rightarrow 8 \times 1$ Mux
 2 select line $2+1=3$ 3 select line

Method 1

 


Select line = 2

Method 2

 



Select line = 1

Method 3

 

Select variable = One

  4×1 Mux $\rightarrow 8 \times 1$ Mux
 3 Select variable





Select line = 2












Select line

Select variable = 2

Select var = 1

Type 2: Mux As a universal logic.

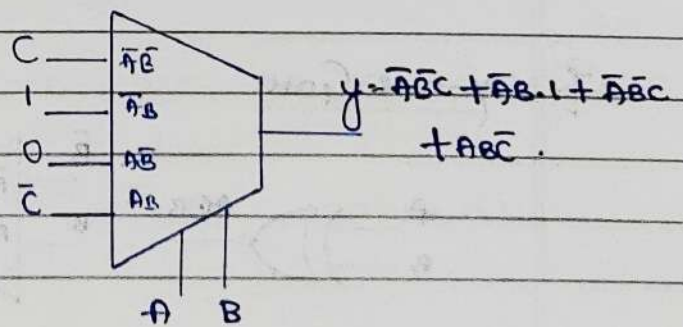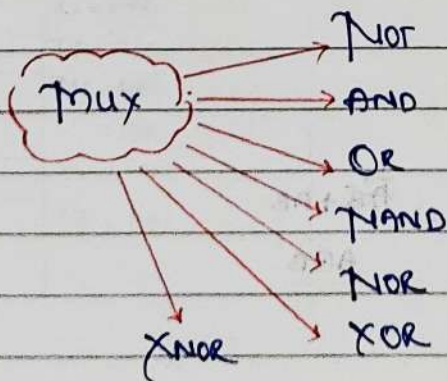

    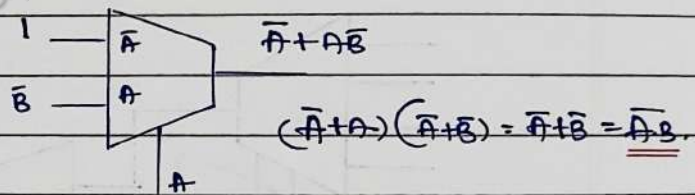      1. NOR Gate2. AND Gate3. OR Gate4. NAND Gate5. NOR Gate6. X-OR Gate7. X-NOR Gate


Note: To design NOT, AND, OR \rightarrow One 2xi mux required
 To design NAND, NOR, XOR, XNOR, \rightarrow Two 2xi mux required.

Type 3 Minimization.

Q1. Find the output f:


	A \ B	00	01	11	10
0		1	1		1
1				1	

 $\Rightarrow \bar{A}C + \bar{A}\bar{B} + ABC$



$$\begin{aligned}
 f(A,B,C) &= \bar{A}\bar{B}.1 + \bar{A}\bar{B}C + \bar{A}B.0 + AB.C \\
 &= \bar{A}\bar{B} + \bar{A}\bar{B}C + ABC \\
 &= \bar{A}\bar{B}(\bar{C} + C) + \bar{A}\bar{B}C + ABC \\
 &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + ABC \\
 &= \sum m(0,1,2,7)
 \end{aligned}$$

Q2. Find output of "f."

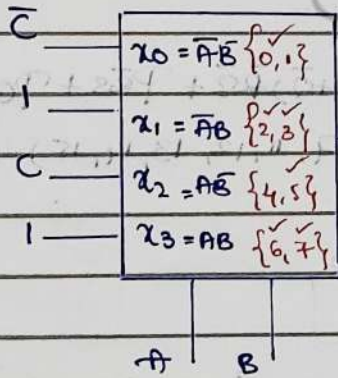


$f(A,B,C)$

$$\begin{aligned}
 &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B} + \bar{A}B\bar{C} + AB \\
 &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}(\bar{C} + C) + \bar{A}B\bar{C} + AB(\bar{C} + C) \\
 &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C} + ABC \\
 &= \sum m(0,2,3,5,6,7)
 \end{aligned}$$

	A \ B	00	01	11	10
0		1		1	1
1			1	1	1

$\Rightarrow B + \bar{A}\bar{C} + AC$

Q3.

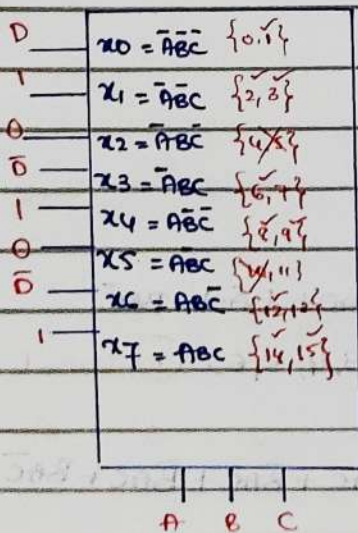


$$\begin{aligned}
 f(A,B,C,D) &= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C + \bar{A}B\bar{C}D + \bar{A}B\bar{C} + \bar{A}B\bar{C}D \\
 &\quad + ABC \\
 &= \sum m(1,2,3,6,8,9,12,14,15)
 \end{aligned}$$

AB \ C	00	01	11	10
00		1	1	1
01				1
11	1		1	1
10	1	1		

Spain

Q.4 find $f = ?$

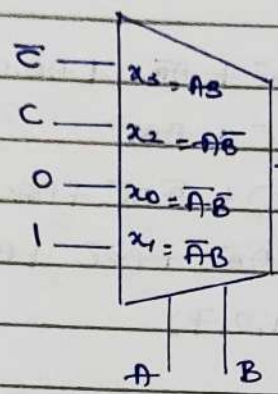

A \ BC	B-barC-bar	B-barC	BC	BC-bar
	00	01	11	10
A-bar	0		1	1
A	1	1		1

$\Rightarrow \underline{\underline{A\bar{B} + B\bar{C} + A\bar{B}C}}$

$$f(A,B,C) = A\bar{B}\bar{C} + A\bar{B}C + \bar{A}B$$


$$= A\bar{B}\bar{C} + A\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC$$

$$= \sum m(2, 3, 5, 6)$$

$\rightarrow P(\bar{Q} + Q)\bar{R}\bar{S}$

$P\bar{Q}\bar{R}\bar{S} = 1000$
 $PQ\bar{R}\bar{S} = 1100$

Q.5

 


$$f(P,Q,R,S) = (P + \bar{Q})\bar{R}\bar{S} + \bar{P}RS + P\bar{Q}RS + P\bar{R}S$$

$$= \sum m(0, 8, 9, 11, 12, 13, 14, 15)$$

PQ \ RS	00	01	11	10
00	1			
01				
11	1	1	1	1
10	1	1	1	

$\Rightarrow P\bar{Q} + P\bar{S} + \bar{Q}\bar{R}\bar{S}$

Q.6.

 


$$f(A,B,C) = \bar{B}\bar{A}\bar{C} + \bar{B}\bar{A}C + \bar{B}A + B\bar{A}\bar{C}$$


$$= \sum m(0, 3, 4, 5, 6) \text{ (1) method}$$

$$f(A,B,C) = \bar{B}\bar{A}\bar{C} + \bar{B}\bar{A}C + \bar{B}\bar{A}\bar{C} + \bar{B}\bar{A}C + B\bar{A}\bar{C} \text{ (2) method}$$


Type 4: Cascading of Mux:

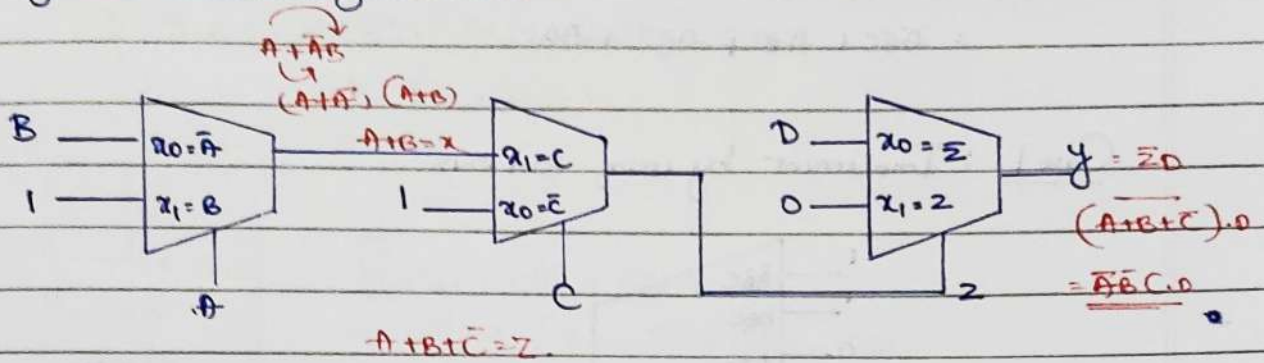


Q1. Find the output of y.

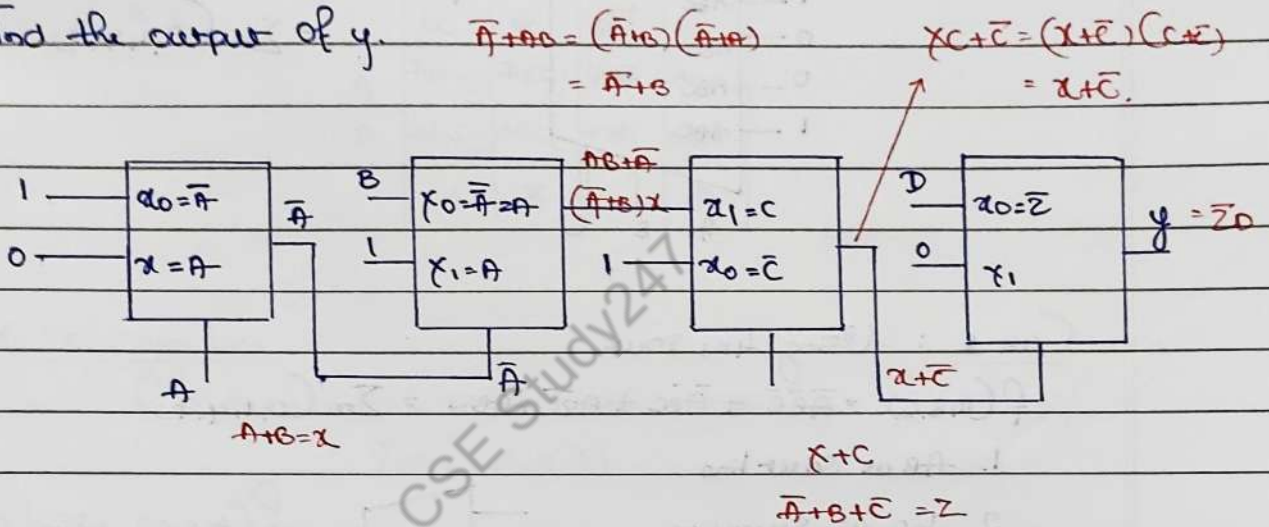

Note:

 

Type 5: Implementation of Function:

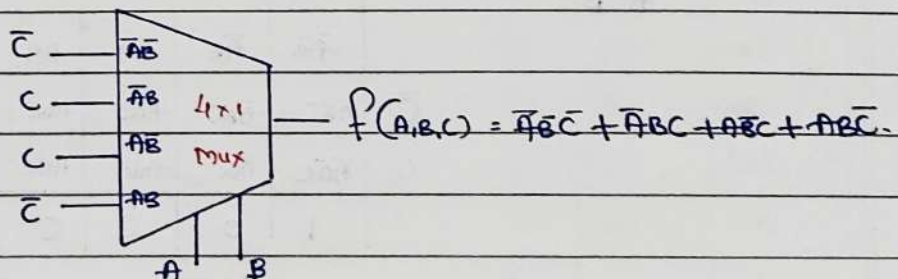

Ex 1. $f(A,B,C) = \sum m(0,1,4,7)$
 $= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$


Case I : Implement by using 8x1 mux



Case II : Using 4x1 Mux


$$f(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC = \sum m(0,1,4,7)$$

 1. AB as select line
2. BC as select line
3. AC as select line



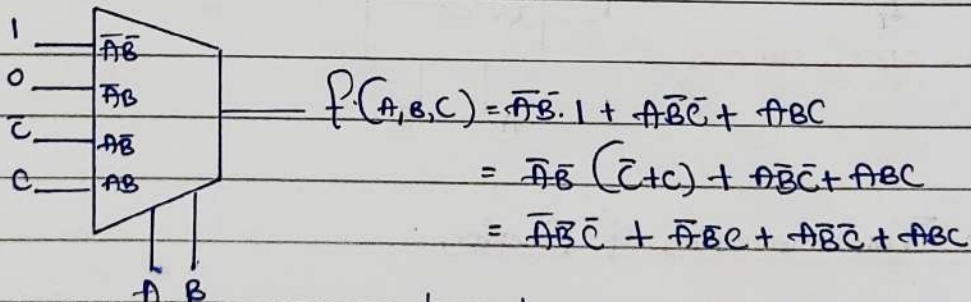1. AB as select line

$$f(A,B,C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC = \sum m(0,1,4,7)$$




	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	AB
\bar{C}	$\bar{A}\bar{B}\bar{C}$ (0)	$\bar{A}B\bar{C}$ (1)	$A\bar{B}\bar{C}$ (4)	$AB\bar{C}$ (5)
C	$\bar{A}\bar{B}C$ (2)	$\bar{A}BC$ (3)	$A\bar{B}C$ (6)	ABC (7)
	1	0	\bar{C}	C

2. BC as Select Line

$$f(A, B, C) = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + AB\bar{C}$$

$$= \sum m(0, 1, 4, 7)$$

 

$$f(A, B, C) = \bar{B}C + \bar{A}BC + AB\bar{C}$$

$$= (\bar{A} + A)\bar{B}C + \bar{A}BC + AB\bar{C}$$


$$= \bar{A}\bar{B}C + A\bar{B}C + \bar{A}BC + AB\bar{C}$$

	$\bar{B}C$	$\bar{B}\bar{C}$	BC	$B\bar{C}$
\bar{A}	$\bar{A}\bar{B}C$ (0)	$\bar{A}\bar{B}\bar{C}$ (1)	$\bar{A}BC$ (2)	$\bar{A}B\bar{C}$ (3)
A	$A\bar{B}C$ (4)	$A\bar{B}\bar{C}$ (5)	ABC (6)	$AB\bar{C}$ (7)
	1	\bar{A}	0	A

3. AC is select line

$$f(A, B, C) = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$$

$$= \sum m(0, 1, 4, 7)$$

 

$$f(A, B, C) = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$$


	$\bar{A}C$	$\bar{A}\bar{C}$	AC	$A\bar{C}$
\bar{B}	$\bar{A}\bar{B}C$ (0)	$\bar{A}\bar{B}\bar{C}$ (1)	$AB\bar{C}$ (4)	$A\bar{B}\bar{C}$ (5)
B	$\bar{A}BC$ (2)	$\bar{A}B\bar{C}$ (3)	ABC (6)	$AB\bar{C}$ (7)
	\bar{B}	\bar{B}	B	B

Case III: Using 2 & 1 Mux

(i) A as select line

$$f(A, B, C) = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$$

$$= \sum m(0, 1, 4, 7)$$

 

$$\bar{A}\bar{B} + A(\bar{B}C + BC)$$

$$\bar{A}\bar{B}(\bar{C} + C) + A\bar{B}C$$

$$+ ABC$$


$$= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C$$

$$+ ABC$$

$$= f(A, B, C) + ABC$$

	\bar{A}	A
$\bar{B}C$	$\bar{A}\bar{B}C$ (0)	ABC (4)
$\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$ (1)	$A\bar{B}\bar{C}$ (5)
BC	$\bar{A}BC$ (2)	$A\bar{B}C$ (6)
BC	$\bar{A}BC$ (3)	ABC (7)
	\bar{B}	$B\bar{C}$

(ii) B as select line

 

$$f(A,B,C) = \sum m(0,1,4,7)$$

	\bar{B}	B
$\bar{A}\bar{C}$	$\bar{A}\bar{B}\bar{C}$ (0)	$\bar{A}B\bar{C}$ (2)
$\bar{A}C$	$\bar{A}\bar{B}C$ (1)	$\bar{A}BC$ (3)
AC	$A\bar{B}C$ (4)	$AB\bar{C}$ (6)
$\bar{A}C$	$\bar{A}BC$ (5)	ABC (7)
	$\bar{A}C + \bar{A}\bar{B}C + \bar{A}BC$	AC

$$= \bar{A}(C + \bar{B}C + BC)$$

$$= \bar{A}(C)$$

$$= \bar{A}C$$

HW


(iii) C as select line $f(A,B,C) = \sum m(0,1,4,7)$

Q1. $f(A,B,C,D) = \sum m(0,1,3,5,7,9,12,15)$

1. ABD is select line
2. ACD is select line

→ 16x1 mux, 8x1 mux, 4x1 mux
2x1 mux
(AB, AC, AD as select line
A as select line.

Type-6: Delay in Mux

 

$$T_{AND} = 1\mu s, T_{mux} = 2\mu s$$

Case 1: $D=0$

$$T = T_{AND} + T_{mux}$$

$$= 1\mu s + 2\mu s$$


$$T = \underline{\underline{3\mu s}}$$

Case 2: $D=1$

$$T = T_{mux}$$


$$T = \underline{\underline{2\mu s}}$$

DE-mux: DE-mux is called And Logic

 

Q1. Design 1x2 DE-mux

Step 1:

 

Step 2:


s_0	y_0	y_1
0	I	0
1	0	I

Step 3:

$$y_0 = \bar{s}_0 I$$

$$y_1 = s_0 I$$


Step 4:

 

Step 4:

Q2. Design a 1x4 DEMUX?

Step 1:

 

Step 2:

s_1	s_0	y_0	y_1	y_2	y_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

Step 3:

$$y_0 = \bar{s}_1 \bar{s}_0 I$$


$$y_1 = \bar{s}_1 s_0 I$$

$$y_2 = s_1 \bar{s}_0 I$$

$$y_3 = s_1 s_0 I$$

Step 4:

Steps:

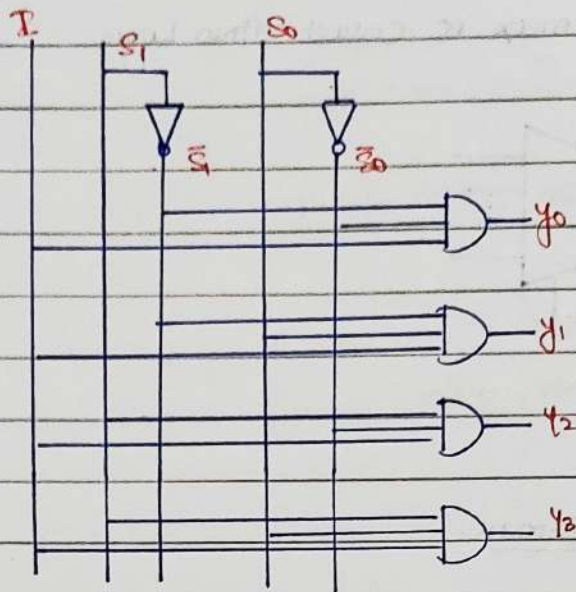


HW

- Q. Design a 1x8 DEMUX
- Q. Design a 1x16 DEMUX

Encoder:

 
Any circuit which is used to convert any code into Binary is called Encoder.



- 1) 4x2 Encoder (Quad to Binary)
- 2) 8x3 Encoder (Octa to Binary)
- 3) 16x4 Encoder (Hexa to Binary)

Q. Design a 4x2 Encoder.

Step 1:

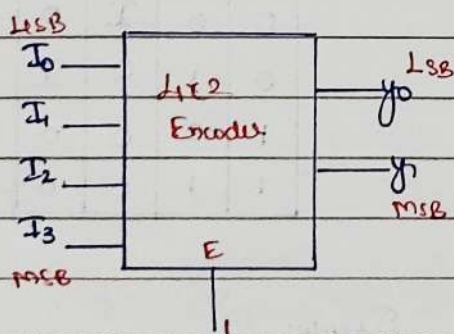


Step 2:

I ₃	I ₂	I ₁	I ₀	Y ₁	Y ₀
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Step 3: $y_0 = I_1 + I_3$
 $y_1 = I_2 + I_3$


Step 5:

 

Step 4:



Q. Design a 8x3 Encoder.

 

HW



Q. Design a 16x4 Encoder

Step 2:

I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	y_2	y_1	y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Step 3: $y_0 = I_1 + I_3 + I_5 + I_7$
 $y_1 = I_2 + I_3 + I_6 + I_7$
 $y_2 = I_4 + I_5 + I_6 + I_7$


Step 5:

  

Step 4:

Note: Priority Encoder

LSB Priority Encoder

 

(M.S.B)	I_3	I_2	I_1	I_0 (L.S.B)	Y_1	Y_0
X	X	X	1	0	0	0
X	X	1	0	0	0	1
X	1	0	0	1	0	
1	0	0	0	1	1	

weighted, self-complementing

Decimal	BCD	Excess-3 code	4 2 2 1	Gray Code
0	0000	0011	0 0 0 0	
1	0001	0100	0 0 0 1	
2	0010	0101	0 0 1 0	
3	0011	0110	0 0 1 1	
4	0100	0111	0 1 1 0	
5	0101	1000	1 0 0 1	
6	0110	1001	1 1 0 0	
7	0111	1010	1 1 0 1	
8	1000	1011	1 1 1 0	
9	1001	1100	1 1 1 1	

Decimal → Weighted code
 → Self Complementing

$10^3 \ 10^2 \ 10^1 \ 1$
 $a_3 \ a_2 \ a_1 \ a_0$

$r \rightarrow$ Base (radix)

Complement

$(r-1)'s$

$r's$ Complement

$r=2$

1's

2's

$r=8$

7's

8's

$r=10$

9's

10's

BCD → Weighted Code
 → Not a Self Complementing Code.

→ Binary Coded Decimal

→ Each decimal numbers are represented by 4 bits.


eg: $\left\{ \begin{array}{l} \text{Decimal - 0} \\ \text{BCD - 0000} \end{array} \right\}$ $\left\{ \begin{array}{l} \text{Decimal - 9} \\ \text{BCD - 1001} \end{array} \right\}$ $\left\{ \begin{array}{l} \text{Decimal - 29} \\ \text{BCD - 0010001} \end{array} \right\}$

Excess - 3 code:

- It is not a weighted code
- Self complemented code


Decoder: Circuit which is used to convert Binary into any other code.

 1. 2x4 Decoder
2. 3x8 Decoder
3. 4x16 Decoder.



2x4 Decoder. E-1

Step 1:

 

Step 2:

I_1	I_0	y_3	y_2	y_1	y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Step 3:

$$y_0 = \bar{I}_1 \bar{I}_0$$


$$y_1 = \bar{I}_1 I_0$$

$$y_2 = I_1 \bar{I}_0$$


$$y_3 = I_1 I_0$$

Step 4: minimization

Step 4:

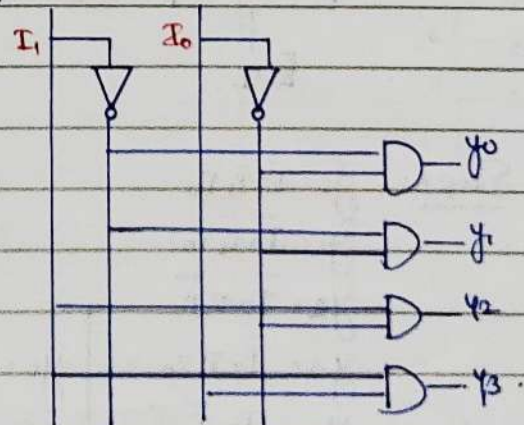

Example:

 

eg:

		$\bar{A}\bar{B}$		A	B	F
(LSB) B	$\bar{A}\bar{B} 0$	0	$\Sigma m(1,2)$	0	0	0
	$\bar{A}B 1$	0	$\Sigma m(0,2,3)$	0	1	1
(MSB) A	$A\bar{B} 2$	0	$\Sigma m(0,1,3)$	1	0	1
	$AB 3$	0	$\Sigma m(0,1,2)$	1	1	1


Pos =

$$F = (A+B) = \pi m(0)$$

SOP

$$F = \Sigma m(1,2,3)$$

3x8 Decoder

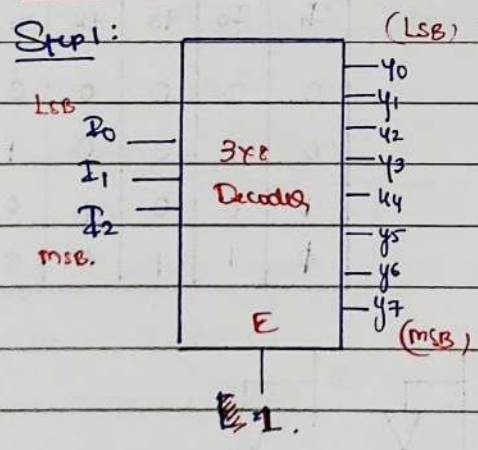

Step 2:

	I2	I1	I0	Y2	Y6	Y5	Y4	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1	0	0	0	0
1	0	0	1	0	0	1	0	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0

Step 3:

$$y_0 = \bar{I}_2 \bar{I}_1 \bar{I}_0$$

$$y_1 = \bar{I}_2 \bar{I}_1 I_0$$

$$y_2 = \bar{I}_2 I_1 \bar{I}_0$$

$$y_3 = \bar{I}_2 I_1 I_0$$

$$y_4 = I_2 \bar{I}_1 \bar{I}_0$$

$$y_5 = I_2 \bar{I}_1 I_0$$

$$y_6 = I_2 I_1 \bar{I}_0$$


$$y_7 = I_2 I_1 I_0$$

Step 4: Minimization

Step 5: Hardware Implementation

HW


Design 4x16 Decoder

 


Q.1 2×4 Decoder $\xrightarrow[\substack{S=2^4 \\ 4 \quad 3}]{}$ 3×8 Decoder
 ↑ input ↑ output

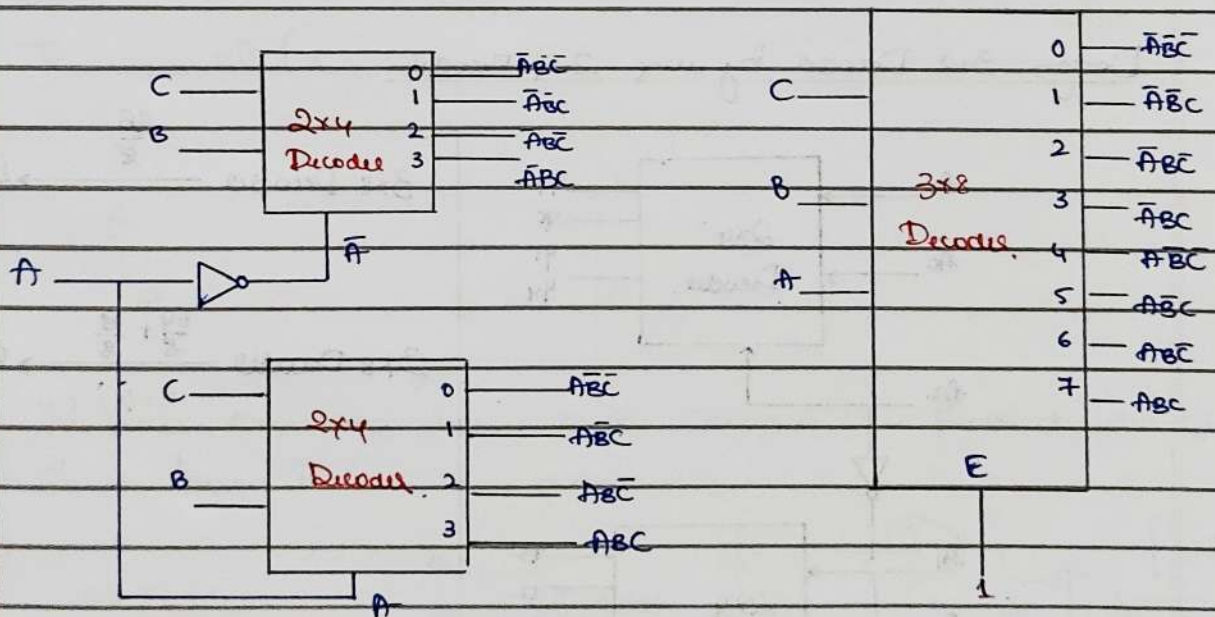Q.2 2×4 Decoder $\xrightarrow[\substack{4+1=5}]{}$ 4×16 Decoder


$2 \times 4 \rightarrow 3 \times 8$ Decoder



2x4 Decoder → 4x16 Decoder

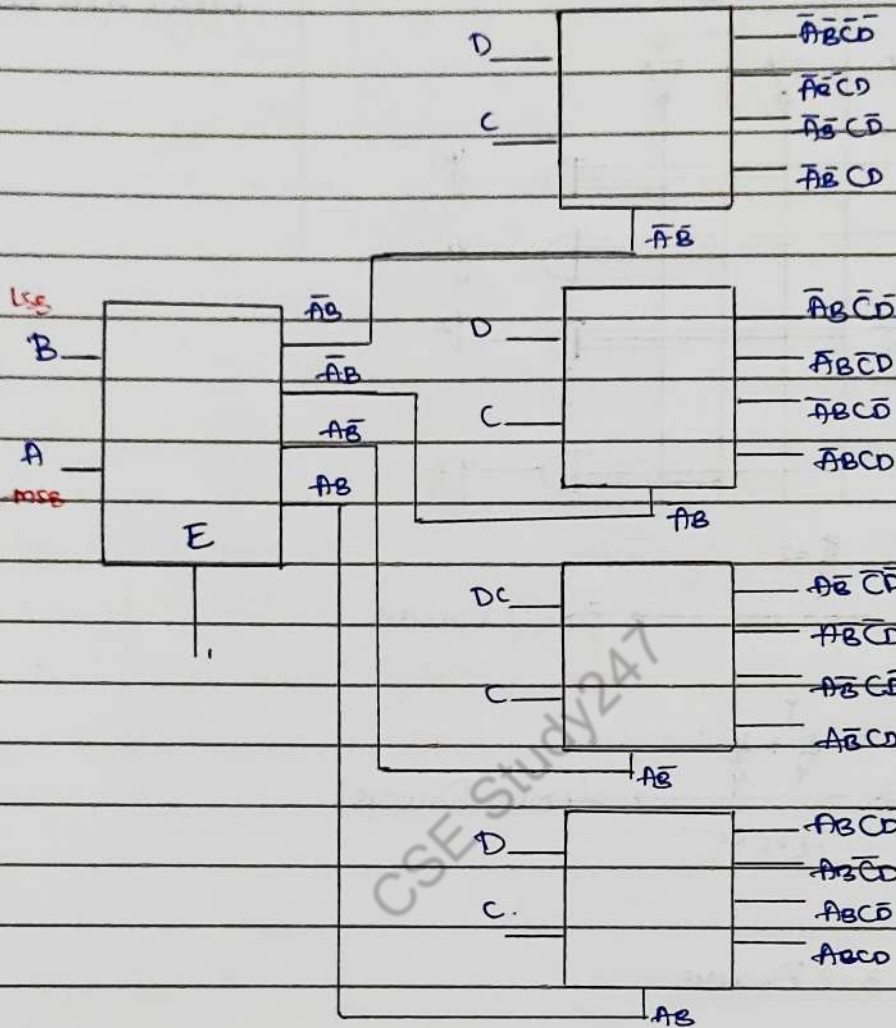


Design 3x8 Decoder by using 2x4 Decoder

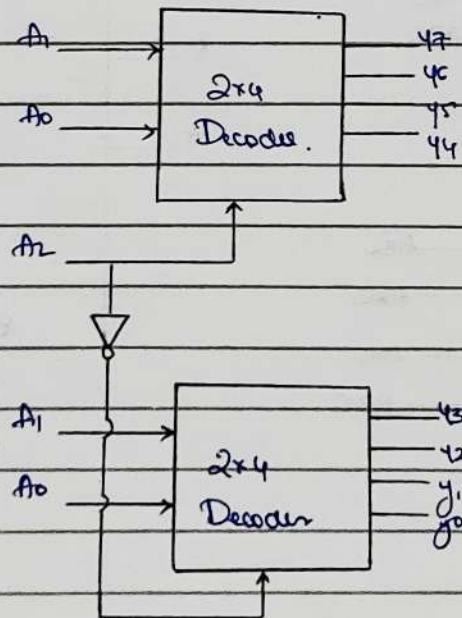

3x8 Decoder $\frac{16^0}{2} = 8$ → 4x16 Decoder

3x8 Decoder $\frac{8^0}{2} + \frac{8^0}{2} = 9$ → 6x64 decoder

3x8 Decoder \rightarrow 8x64 Decoder

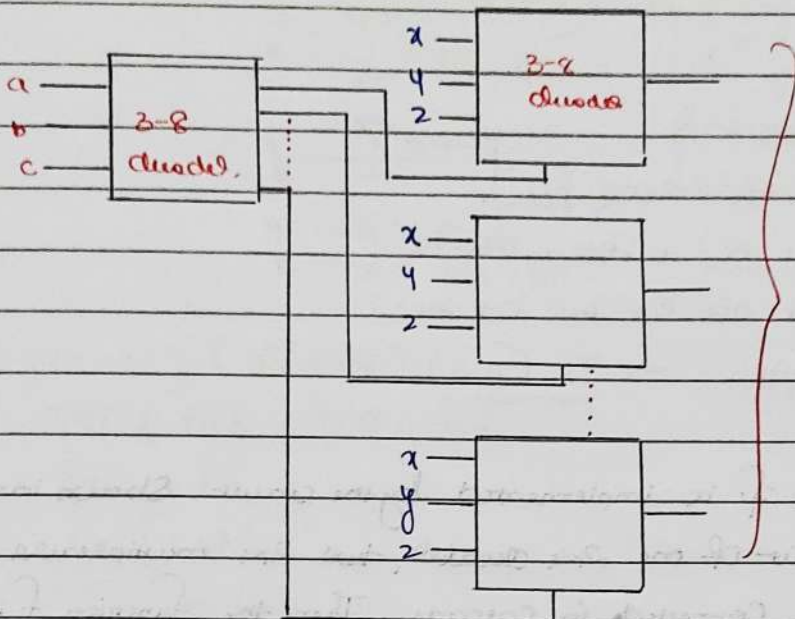


H.W.
Design Binary to decimal decoder.

Q.1 A logic circuit consist of 2x4 decoders as shown in the figure. The output are as follows:

- $D_0 = 1$ when $A_0 = 0, A_1 = 0$
- $D_1 = 1$ when $A_0 = 1, A_1 = 0$
- $D_2 = 1$ " $A_0 = 0, A_1 = 1$
- $D_3 = 1$ " $A_0 = 1, A_1 = 1$

The value of (x, y, z) is.

 

Ans


1, 1


A_1	A_0	Y
0	0	$D_0 = 1$
0	1	D_1
1	0	D_2
1	1	D_3

Q2 The boolean expression $f(a,b,c)$ in its canonical form for the decoder circuit shown below is

Ans

$\Rightarrow \Sigma_m(4,6)$

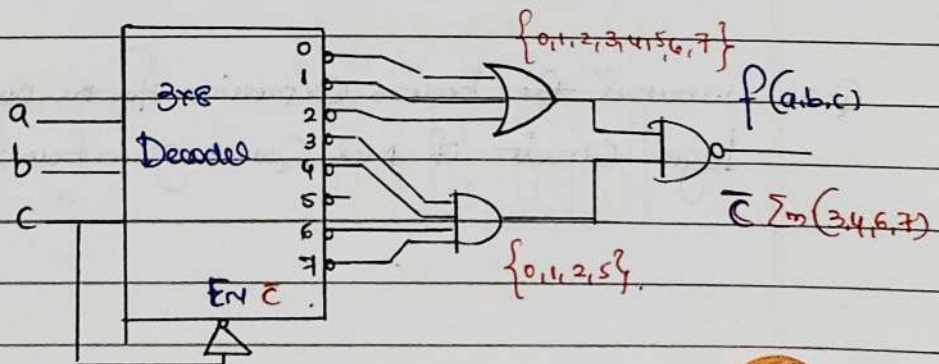

 

$$F = \sum m(3, 4, 6, 7)$$


$$= \bar{C} [ABC + \bar{A}BC + A\bar{B}C + A\bar{B}C]$$

$$= \bar{C} [ABC + \bar{A}BC + A\bar{B}C + A\bar{B}C]$$

$$= \bar{A}BC\bar{C} + A\bar{B}C\bar{C} + A\bar{B}C\bar{C} + A\bar{B}C\bar{C}$$

$$= \bar{A}BC + A\bar{B}C \Rightarrow \underline{\underline{\sum m(4, 6)}}$$

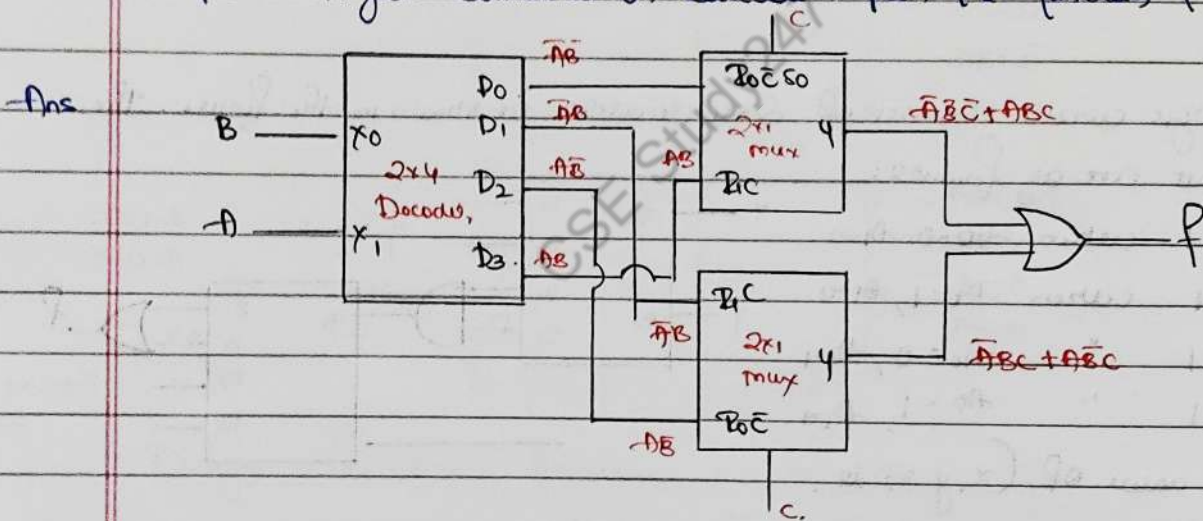Q3. A logic function 'f' is implemented by the circuit shown in the figure below. The circuit consists of one 2x4 decoder, two 2x1 multiplexers and a two input OR gate connected in cascade. Then the function f is equal to




$$f = \bar{A}BC + ABC + \bar{A}BC + ABC$$

$$= \sum m(0, 3, 4, 7)$$

$$\Rightarrow \underline{\underline{\bar{B}C + BC = B \odot C}}$$


A \ B	00	01	11	10
0	1		1	
1	1		1	

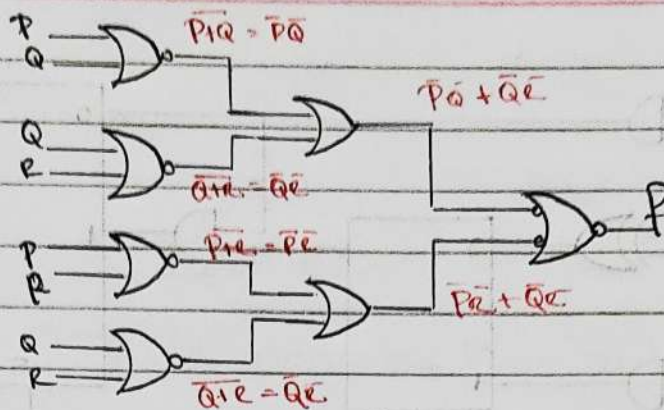Q2. What is the boolean expression for the output f of the combinational logic circuit of NOR gates given below.



$$\begin{aligned}
 f &= [\bar{P}\bar{Q}] \cdot [\bar{P}\bar{R}] \\
 &= \bar{P}\bar{Q}\bar{R} + \bar{P}\bar{Q}R + \bar{P}Q\bar{R} + \bar{P}QR \\
 &= \bar{P}\bar{Q}\bar{R} + \bar{Q}\bar{R} \\
 &= \bar{Q}\bar{R} [1 + \bar{P}] \\
 &= \bar{Q}\bar{R} \Rightarrow \underline{\underline{\bar{Q} + \bar{R}}}
 \end{aligned}$$

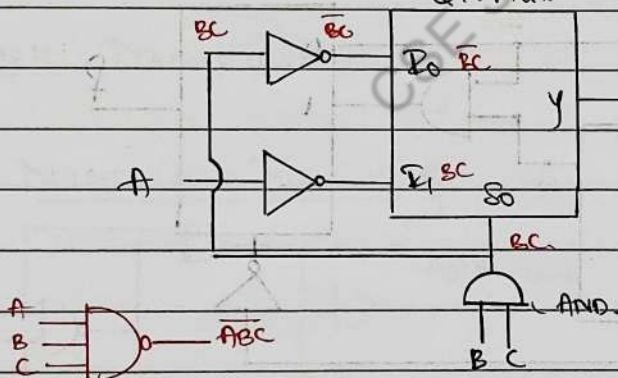Q4. The Combinational Circuit given below implements which of the following 2x1 Mux




$$\begin{aligned}
 &= \bar{B} \cdot \bar{C} + \bar{A}BC \\
 &= \bar{B}\bar{C} + \bar{A}BC \\
 &= \bar{A} + \bar{A}X \\
 &= (\bar{X} + \bar{A})(\bar{X} + X) \\
 &= \bar{B}\bar{C} + \bar{A} \\
 &= \underline{\underline{BCA}}
 \end{aligned}$$

} BC = X

∴ NAND Gate

 Q5. The combinational logic circuit shown in the given figure has an output Q which is




$$\begin{aligned}
 Q &= \bar{A}\bar{B}C + \bar{A}B + A\bar{B} + AB \\
 &= \sum m(1, 2, 3, 4, 5, 6, 7)
 \end{aligned}$$

A	B	00	01	11	10
0	0	0	1	1	1
1	0	1	1	1	1

⇒ A + B + C

Q6.

 Case 1: T=0

$$T = T_{AND} + T_{MUX}$$

$$T = 2 + 1 = \underline{\underline{3ns}}$$


Case 2: T=1

$$T = T_{AND} + T_{MUX} + T_{AND} + T_{MUX}$$

$$= 2 + 1 + 2 + 1 = \underline{\underline{6ns}}$$

$$\therefore \text{Max} = \underline{\underline{6ns}}$$

Q7.

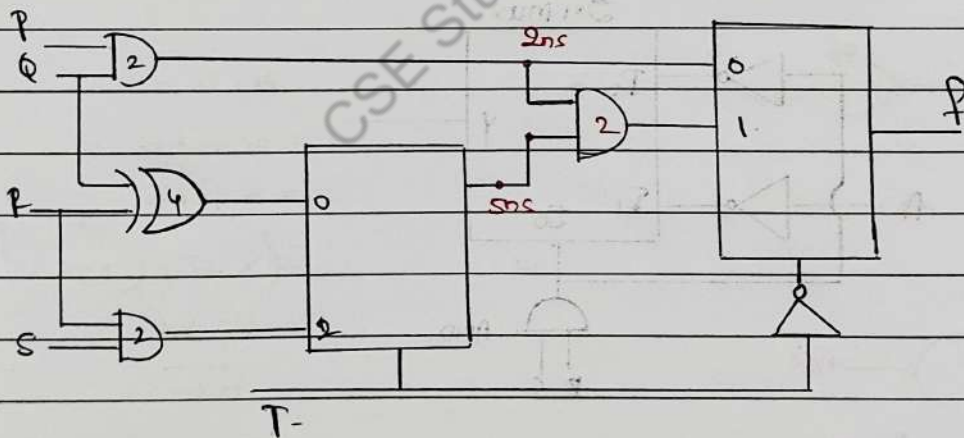Case (1): T=0

$$T = T_{xor} + T_{MUX} + T_{AND} + T_{MUX}$$


$$= 4 + 2 + 1 + 1 = \underline{\underline{8ns}}$$

Case (2): T=1

$$T = T_{AND} + T_{MUX}$$


$$T = 2 + 1 = \underline{\underline{3ns}}$$

Half Adder

 

* Two bit adder are known as half adder.

Step 1:

 

Step 2:



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Step 3: $Sum = \bar{A}B + A\bar{B} = A \oplus B$
 $Carry = AB$



Steps:

Step 4: Minimization.


NAND Gates Required = 5

  


By NOR Gate

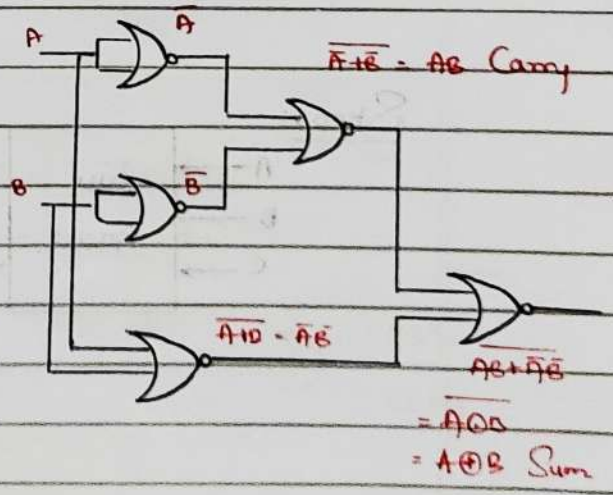 

Half Adder By Using Decoder.

 

Q1. What is the value of f_1 and f_2 ?

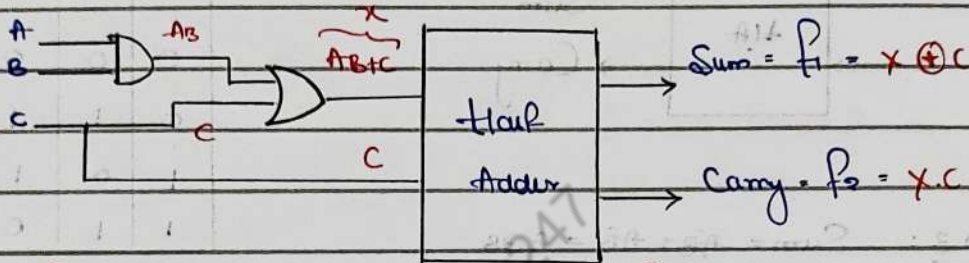

$$\begin{aligned} f_1 &= (AB + C) \oplus C \\ &= \overline{AB+C} \cdot C + (AB+C) \cdot \overline{C} \\ &= \overline{AB} \cdot \overline{C} \cdot C + AB\overline{C} + C \cdot \overline{C} \\ &= \underline{\underline{AB\overline{C}}} \end{aligned}$$


$$\begin{aligned} f_2 &= (AB + C) \cdot C \\ &= ABC + C \cdot C = ABC + C \\ &= C[AB + 1] \\ &= \underline{\underline{C \cdot AB}} \end{aligned}$$

Full Adder : Three bit adder are known as full adder.

0	0	0	0
0	0	1	1
<u>+ 0</u>	<u>+ 1</u>	<u>+ 1</u>	<u>+ 1</u>
00	01	10	11

Step 2:

Step 1:


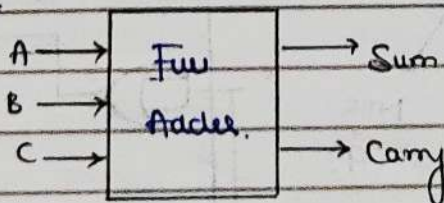


A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Steps: $\bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$
 (Sum) = $\sum m(1, 2, 4, 7)$
 = $A \oplus B \oplus C$


Step 4: Carry(A, B, C) = $\sum m(3, 5, 6, 7)$
 = $\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$
 = $AB + BC + AC$ - minimized exp.
 = $(A+B)C + AB(C+C)$
 = $(A+B)C + AB$ - 2 term minimized.

Steps:

  


$$\text{Sum} = (A \oplus B) \oplus C$$


$$\text{Carry} = (A \oplus B)C + AB$$

 

1 Full Adder = 2 H.A + 1 OR Gate

 


Full Adder by using NAND Gate.

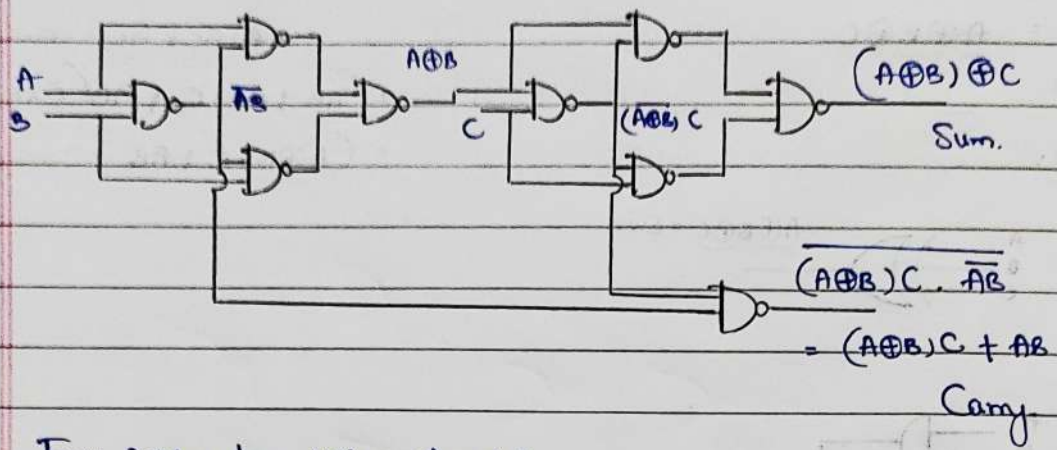


HW
Full Adder by using NOR GATE.


Full Adder by using decoder.

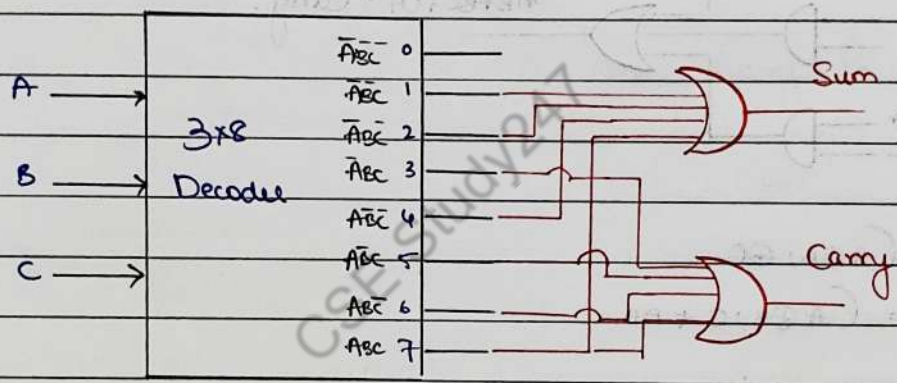

Half Adder	Full Adder
$\begin{cases} \text{Sum} = A \oplus B \\ \text{Carry} = AB \end{cases}$	$\begin{aligned} \text{Sum} &= \sum m(1, 2, 4, 7) = A \oplus B \oplus C \\ \text{Carry} &= \sum m(3, 5, 6, 7) \\ &= (A \oplus B)C + AB \\ &= AB + BC + AC \end{aligned}$
NAND/NOR = 5	NAND/NOR = 9
	1 Full = 2 HA + 1 OA

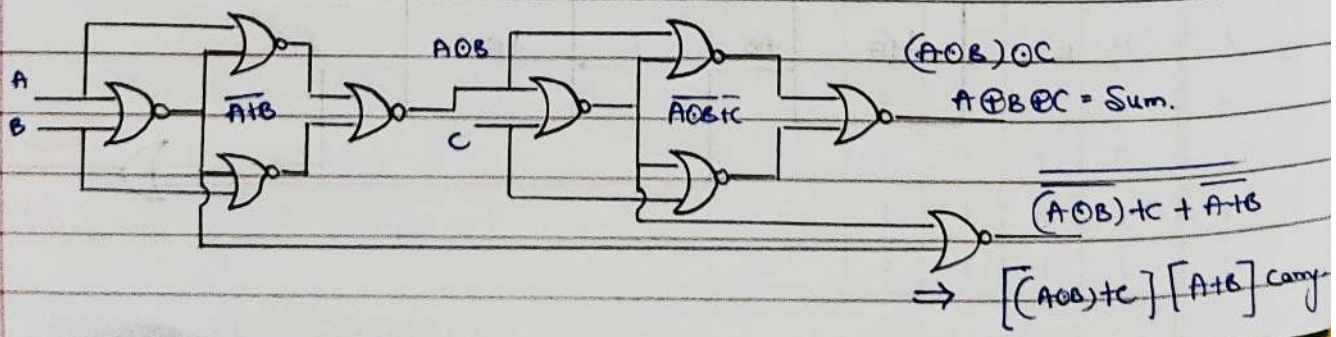

Full Subtractor

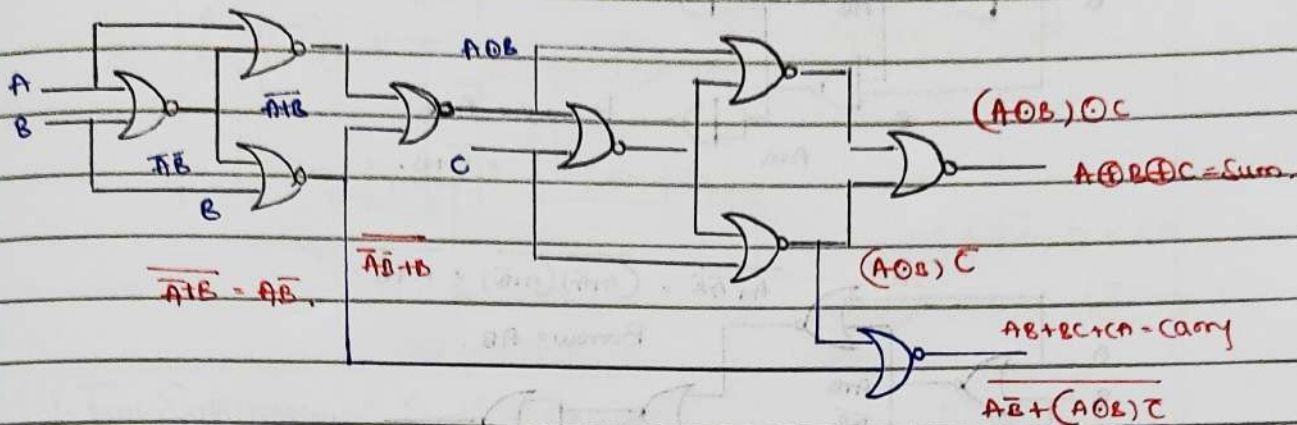


$$\begin{aligned}
 &= \overline{A\overline{B}} + (A \oplus B) \odot C \\
 &= \overline{A\overline{B}} \cdot (A \oplus B) \odot C \\
 &= (\overline{A} + B) [(A \oplus B) \odot C] \\
 &= (\overline{A} + B) [\overline{A}B + A\overline{B} + C] \\
 &= \overline{A}B + B\overline{A} + \overline{A}B + A\overline{B} + BC \\
 &\Rightarrow \overline{A}B + \overline{A}C + BC
 \end{aligned}$$

Borrow.

Half Subtractor : Two bit Subtractor are known as half subtractor.

Step 1:

 


Step 2:



A	B	Diff.	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Step 4:

Step 5:

 


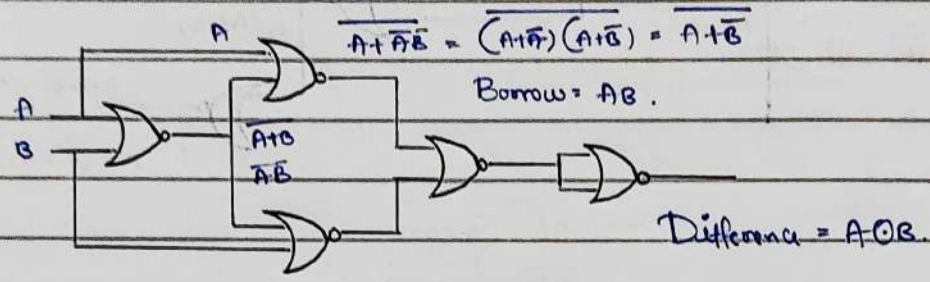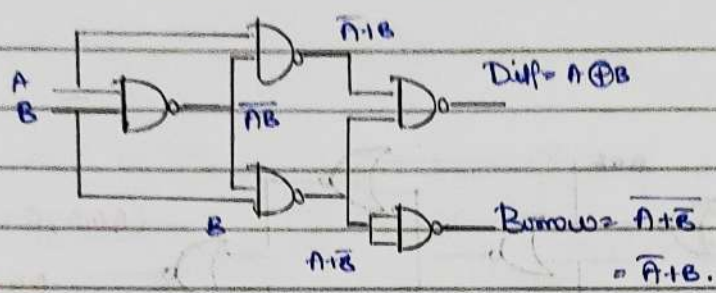Step 3: Diff = $A \oplus B$
Borrow = $A \odot B$



Full Subtractor

Step 1:

 

Step 2:


Input			Output	
A	B	C	Diff	Borr.
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Step 3: $Diff = \sum m(1, 2, 4, 7)$
 $= A \oplus B \oplus C$


$Borrow = \sum m(1, 2, 3, 7)$
 $= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + ABC$
 $= (\bar{A}\bar{B} + \bar{A}B)C + \bar{A}B(\bar{C} + C)$
 $= (\bar{A} \oplus B)C + \bar{A}B \rightarrow$ Semi minimized expression
 $\rightarrow \bar{A}B + \bar{A}C + BC$

Step 4:

Steps:

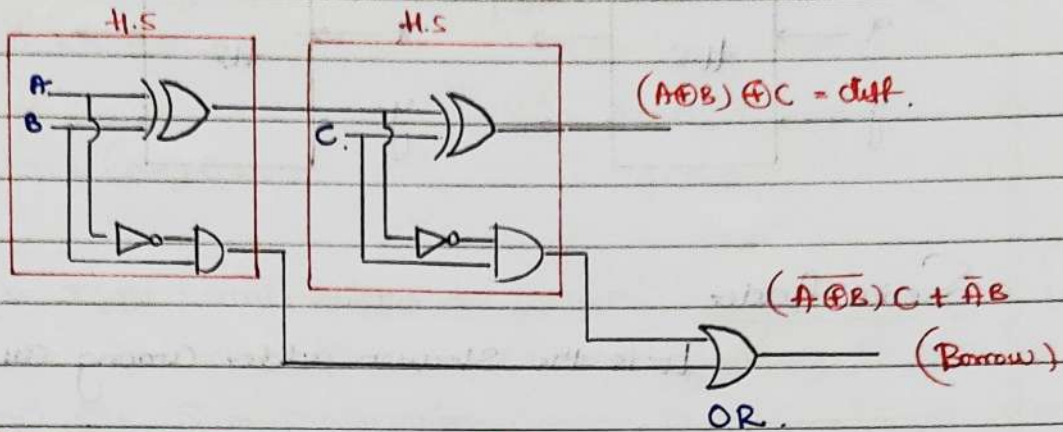


1 Full Subtractor = 2 H.S + Or Gate.

 

Half adder

Sum = $A \oplus B$

Carry = AB

 


NAND } 5.
NOR } 5.

Half Subtractor

Diff = $A \oplus B$

Borrow = \overline{AB}

 

NAND } 5
NOR } 5

Full Adder

Sum = $A \oplus B \oplus C$

Carry = $\sum m(3, 5, 6, 7)$
 $= (A \oplus B)C + AB$
 $= AB + AC + BC$


NAND/NOR = 9.

Full Subtractor

difference = $A \oplus B \oplus C$

borrow = $\sum m(1, 2, 3, 7)$
 $= (\overline{A \oplus B})C + \overline{AB}$
 $= \overline{AB} + \overline{A}C + BC$

NAND/NOR = 9.

 


Serial Adder "One by one addition"

It is the slowest adder among all the adders.

$$T = n \cdot T_{delay}$$

$n \rightarrow$ no. of bits



$T_{delay} \rightarrow$ delay of adder.

 

for synchronization.

Parallel Adder (Ripple Carry Adder)

Inputs are connected simultaneously

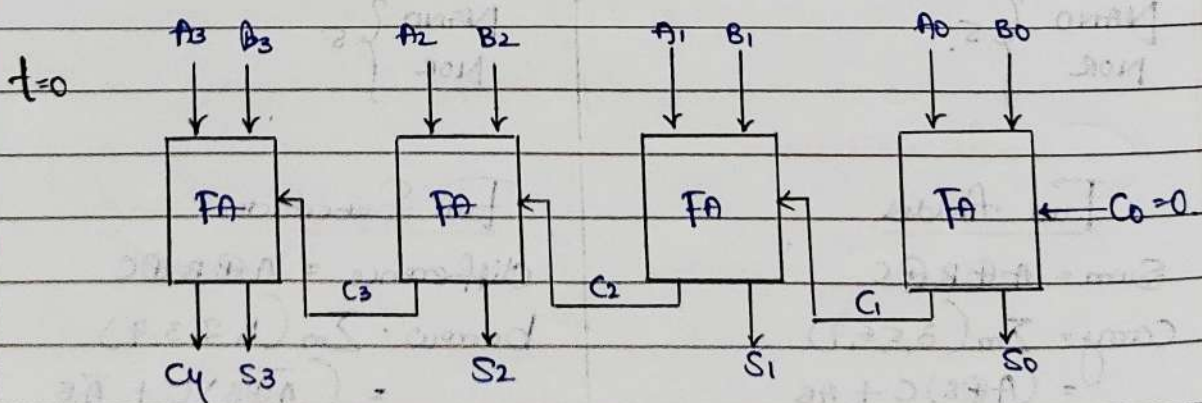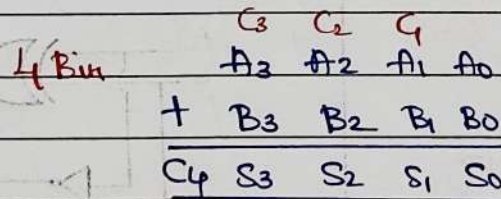


n bit Parallel adder

1. $(n-1)$ FA + 1 HA
2. n -FA
3. $(2n-1)$ HA + $(n-1)$ OR.



$$T = (n-1) T_{carry} + \max(T_{sum}, T_{carry})$$

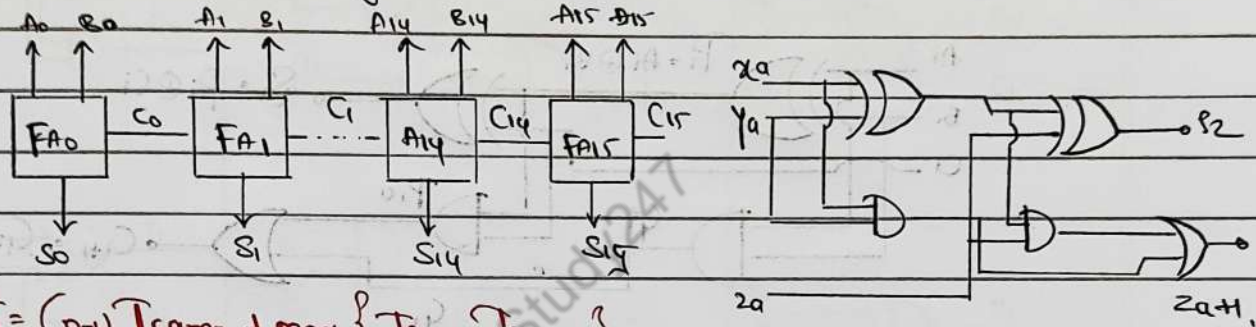Q1. A 16-bit ripple carry adder is realised using 16 identical full adders (FA) as shown. The carry propagation delay of each FA is 12 ns and the sum propagation delay of each FA is 15 ns. The worst case delay (in ns) of the 16-bit adder will be _____




$$\begin{aligned}
 T &= (n-1) T_{carry} + \max\{T_{sum}, T_{carry}\} \\
 &= (16-1) \times 12 \text{ ns} + \max\{15 \text{ ns}, 12 \text{ ns}\} \\
 &= 15 \times 12 + 15 \\
 &= \underline{\underline{195 \text{ ns}}}
 \end{aligned}$$

Parallel Adder (4 bit)

$T_{xor} = 2 \text{ second}$

$T_{and} = T_{or} = 1 \text{ second}$

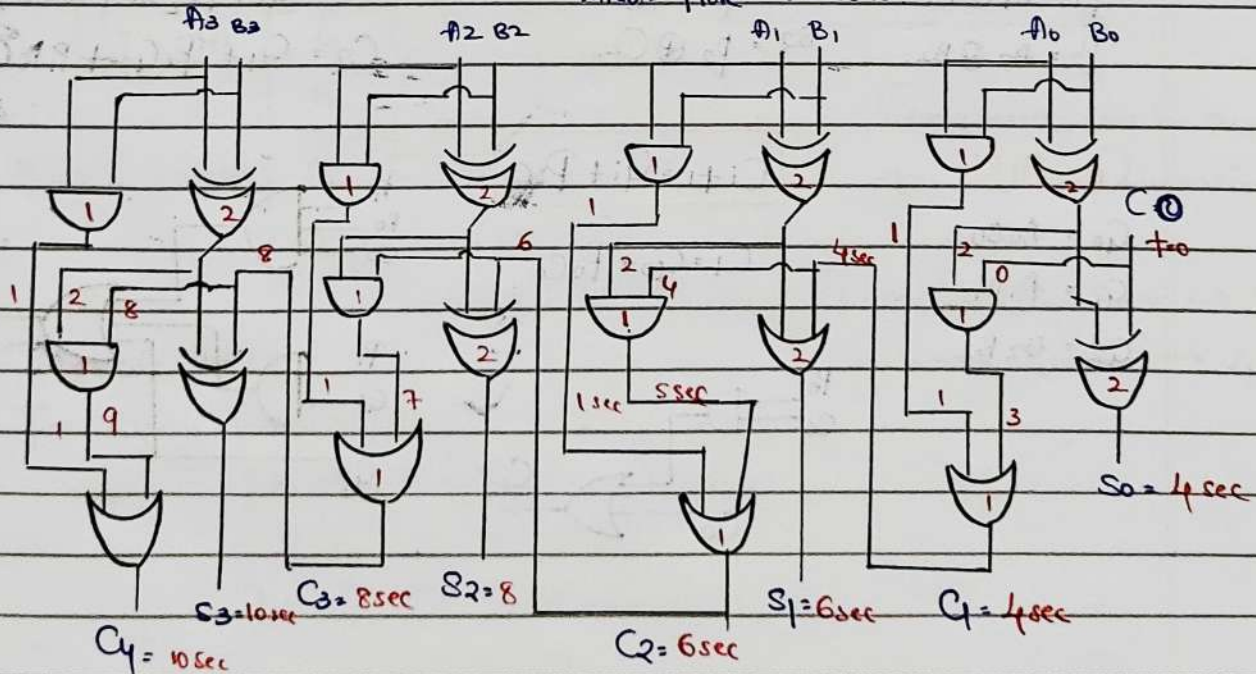


$$T = (n-1) \{ T_{AND} + T_{OR} \} + \max \{ T_{sum}, T_{carry} \}$$

$$\begin{aligned} T &= (4-1) \{ 1+1 \} + \max \{ 4, 4 \} \\ &= 3 \times 2 + 4 \\ &= \underline{10ns} \end{aligned}$$

Parallel Adder, LACA

[Look Ahead Carry Adder]

→ fastest adder among all the adders

 

$P_i \rightarrow$ Carry propagating term
 $C_i \rightarrow$ Carry generating term

$$P_i = A_i \oplus B_i$$

$$S_i = P_i \oplus C_i$$

$$P_0 = A_0 \oplus B_0$$

$$S_0 = P_0 \oplus C_0$$

$$C_2 = C_1 + P_1 C_1$$

$$P_1 = A_1 \oplus B_1$$

$$S_1 = P_1 \oplus C_1$$

$$C_2 = C_1 + P_1 [C_0 + P_0 C_0]$$

$$P_2 = A_2 \oplus B_2$$

$$S_2 = P_2 \oplus C_2$$

$$C_2 = C_1 + P_1 C_0 + P_1 P_0 C_0$$

$$C_i = A_i B_i$$



$$C_{i+1} = C_i + P_i C_i$$

$$C_0 = A_0 B_0$$

$$C_1 = C_0 + P_0 C_0$$

$$C_1 = A_1 B_1$$


$$C_2 = A_2 B_2$$

  


$$C_3 = G_2 + P_2 C_2$$

$$C_3 = G_2 + P_2 [G_1 + P_1 G_0 + P_1 P_0 G_0]$$
 
$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 G_0$$



CARRY BLOCK

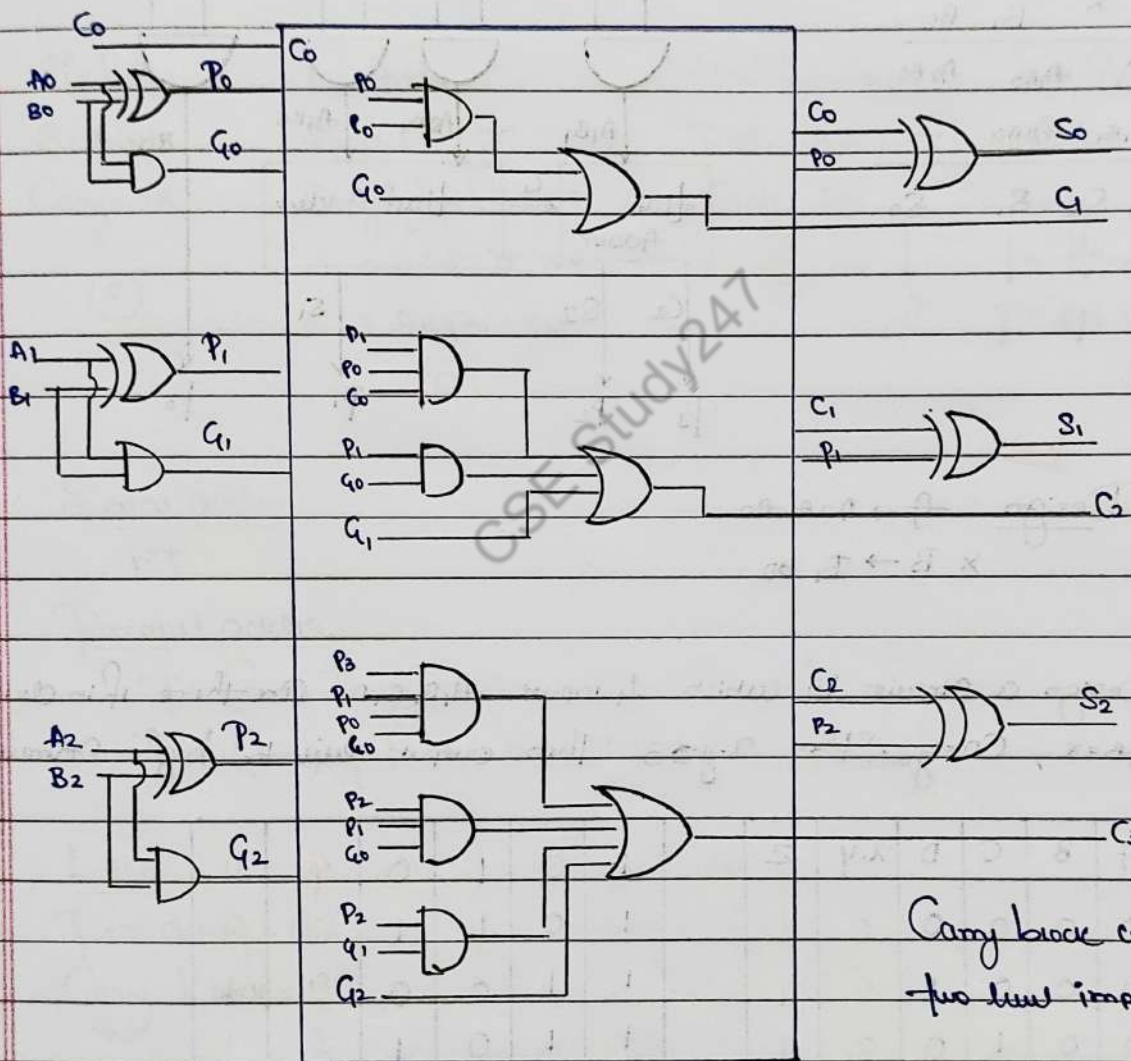

Carry block can be always two level implementation.

* Delay for Carry Block $\Rightarrow 2\tau$

* For entire circuit $\Rightarrow 4\tau$

'n' bit RACA




For carry block:

$$\text{No. of AND Gate} = \frac{n(n+1)}{2}$$

$$\text{No. of OR Gate} = n$$

Multiplication:

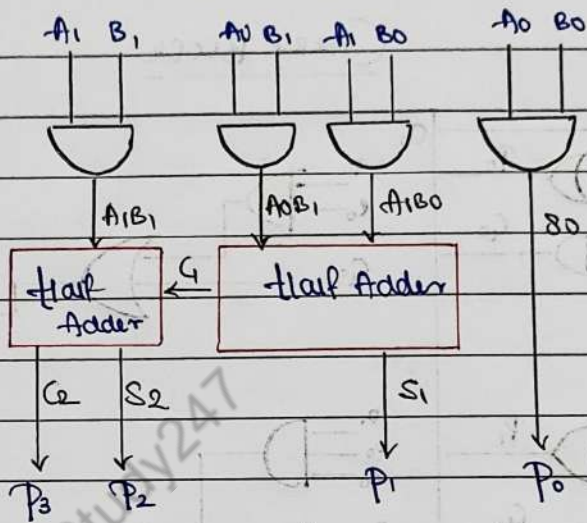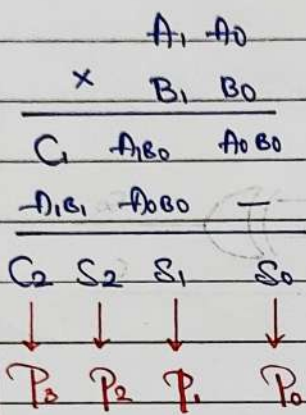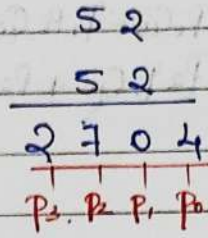2 bit. $A \rightarrow A_1 A_0$
 $B \rightarrow B_1 B_0$



hw

Design. $A \rightarrow A_2 A_1 A_0$
 $\times B \rightarrow B_1 B_0$

Q1. Design a circuit in which 4 inputs A, B, C, D. are there if in decimal $AB=x, CD=y$. Then $x \cdot y \leq 3$ Then output will be high otherwise low.

A	B	C	D	x.y	Z
1	0	1	0	4	0
0	0	0	0	0	1
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	2	1
0	1	1	1	3	1
1	0	0	0	0	1
1	0	0	1	2	1

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1		
10	1	1		

$$\overline{A+C} = \overline{AC}$$

Combinational Circuit - { static circuit }Quick Summary!Comparator

$$(A > B) \quad X \Rightarrow A\bar{B} + (A + \bar{B})A_0\bar{B}_0 \rightarrow \text{minimised}$$

$$A\bar{B} + (A + \bar{B})A_0\bar{B}_0 \rightarrow \text{Semi-minimised}$$

Mux, Demux

Encoder, Decoder.

Half Adder

$$S = A \oplus B$$

$$\text{Carry} = AB$$

(5)

Full Adder

$$\text{Sum} = A \oplus B \oplus C$$

$$\text{Carry} = \sum m(3, 5, 6, 7)$$

$$= (A \oplus B)C + AB$$

$$= AB + AC + BC$$

(9)

Half Subtractor

$$\text{Diff} = A \oplus B$$

$$\text{Carry} = \bar{A}B$$

(5)

Full Subtractor

$$\text{Diff} = A \oplus B \oplus C$$

$$\text{Carry} = \sum m(1, 2, 3, 7)$$

$$= \bar{A}B + (A \oplus B)C$$

$$= \bar{A}B + \bar{A}C + BC$$

(9)

Serial adder

n.T.

Parallel adder

$$T = (n-1) T_{\text{carry}} + \max \{ T_{\text{sum}}, T_{\text{carry}} \}$$

$$T = (n-1) \{ T_{\text{AND}} + T_{\text{OR}} \} + \max \{ T_{\text{sum}}, T_{\text{carry}} \}$$

LACA

$$\text{Total delay} = 4\tau$$

$$\text{Carry block} = 2\tau$$

Carry Block



$$\text{AND} = \frac{n(n+1)}{2}$$

$$\text{OR} = n$$


SEQUENTIAL CIRCUIT

Sequential Circuit:

 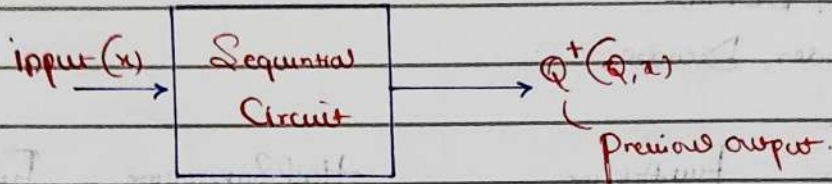- * A circuit with feedback and memory are called Sequential Circuit.
- * Output of the sequential circuit depends on previous output as well as present state of input.




Basic Memory Element
i = ii

 

Latches : Basic memory element

* Latches are level triggered

 * Latches have two output which is complement of each other




X	Y	Q	Q̄	
0	0	1	1	* Invalid
0	1	1	0	
1	0	0	1	
1	1	Q	Q̄	→ Hold

NAND


A	B	$y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Note: Whenever $x=y=1$ is applied and invalid condition occurs than a NAND having lower Propagation delay first change its output and other remain on its previous state are called racing problem or racing problem.


SR: Set-Reset Latch

 

S	R	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold
0	1	0	1	Reset
1	0	1	0	Set
1	1	X	X	(Invalid)

 


S-R Latch by using NOR Gate:

 

S	R	Q	\bar{Q}		NOR		
					A	B	$Y = \overline{A+B}$
0	0	Q	\bar{Q}	Hold	0	0	1
0	1	0	1	Reset	0	1	0
1	0	1	0	Set	1	0	0
1	1	X	X	Invalid.	1	1	0

Hw


①

 

x	y	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		


HW

2

 


X	Y	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

3

 


X	Y	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

4

 



X	Y	Q	\bar{Q}
0	0	1	0
0	1	1	0
1	0	0	1
1	1	1	0

5

 

X	Y	Q	\bar{Q}
0	0	Q	\bar{Q} → Invalid
0	1	Q	\bar{Q} → Hold
1	0	\bar{Q}	Q → Toggle
1	1	\bar{Q}	Q → Invalid

  → Latches with control phenomena are called "Flip Flop".




Flip Flop Steps

1. Circuit diagram
2. Truth table
3. Characteristic table
4. Characteristic equation
5. Excitation table
6. State diagram

SR Flip Flop (Ser-Reset Flip Flop)

Circuit diagram:

 

Truth Table:

S	R	Q _n	Q _{n+1}	
0	0	Q _n	Q _n	→ Hold/Pres.
0	1	0	1	→ Reset.
1	0	1	0	→ Set.
1	1	x	x	→ Invalid

Characteristic Table:

	S	R	Q _n	Q _{n+1}
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	x
7	1	1	1	x

$$Q_{n+1} = (S, R, Q_n) = \sum m(1, 4, 5) + \sum d(6, 7)$$

Characteristic Equation:

		$\overline{R}Q_n$	$\overline{R}Q_n$	RQ_n	RQ_n
		00	01	11	10
\overline{S}	0		1		
S	1	1	1	x	x


$$Q_{n+1} = \underline{S + \overline{R}Q_n}$$

Excitation Table:

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

State Diagram:

 

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

HW


Q Truth Table:

C	J	Q_{n+1}
0	0	$\overline{Q_n}$
0	1	Q_n
1	0	1
1	1	0

Write:

- * Characteristic Table
- * Characteristic equations
- * Excitation Table
- * State diagram

JK Flip Flop

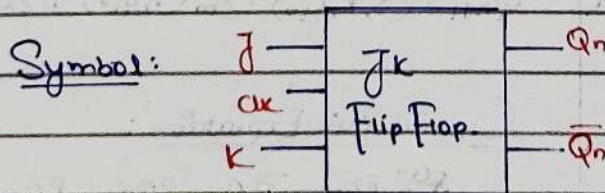

Truth Table:

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

Characteristic Table:

J	K	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$Q_{n+1}(J, K, Q_n) = \sum m(1, 4, 5, 6)$

Characteristic Equation:

	$\bar{J}\bar{K}$ 00	$\bar{J}K$ 01	$J\bar{K}$ 11	JK 10
\bar{J} 0		1		
J 1	1	1		1

$Q_{n+1} = \underline{\underline{J\bar{Q}_n + \bar{K}Q_n}}$


Excitation Table:

Table:


Q _n	Q _{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

J	K	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

State Diagram:


 


Q _n	Q _{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

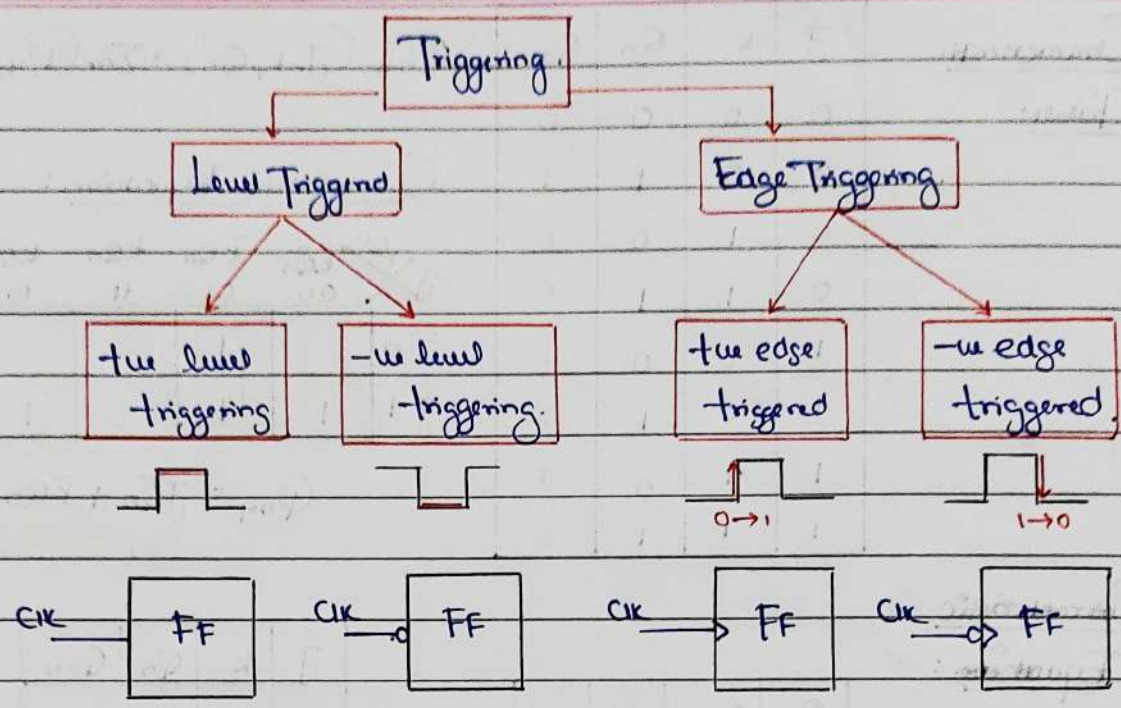

Note: level triggered JK flip flop suffers from the problem of "Race Around"

Race Around Problem:

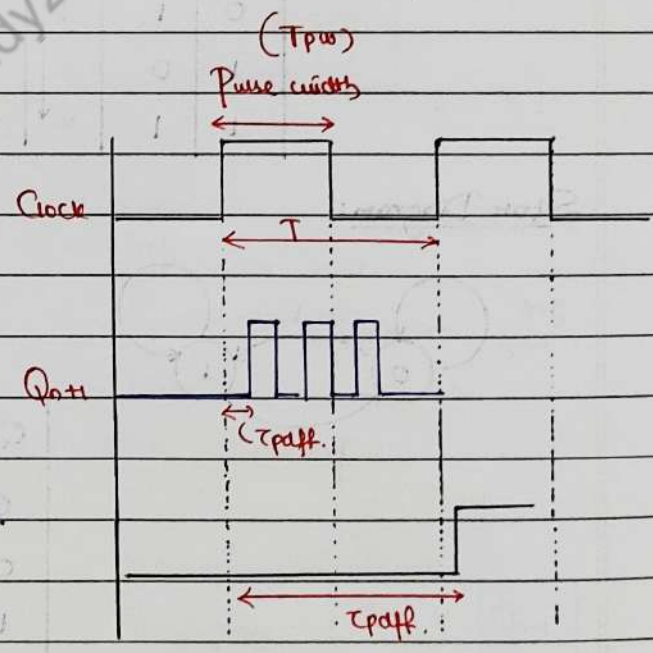 


To avoid the Race Around Problem:


1. $T_{pw} < T_{pdff} < T_{clk}$
2. By Master slave ff.

→ When $J=K=1$ is applied to the level sensitive of JK FF, then within the duration of pulse output of the FF toggle more than one times are called "Race Around Problem".

Master Slave FF

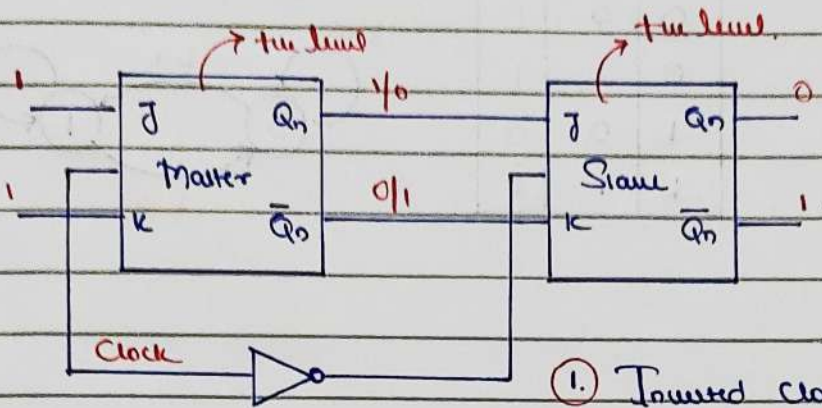

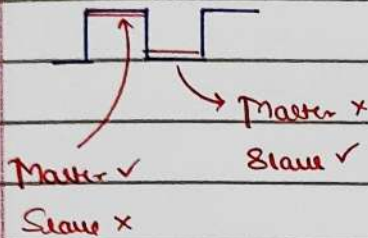(1) Inverted clock is applied to the slave as compared to master.




(2) Master-Slave flip flop is used to store single bit because output is taken only from slave.

(3) By the operation it seems that master is level triggered whereas slave is negative edge triggered.

D Flip Flop

- * It is known as Delay FF or Transparent FF
- * In the D FF whenever the input is applied it will directly come to the output along with the clock.

Symbol:

 

Characteristic Table:

D	Qn	Qn+1
0	0	0
0	1	0
1	0	1
1	1	1

Truth Table:

D	Qn+1
0	0
1	1


Characteristic Equation:

$$\underline{Q_{n+1} = D}$$



Excitation Table:

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1



State Diagram:

 

Q1.

  


Q2

  

T Flip Flop (Toggle Flip Flop)

Symbol:

 

Characteristic Table:

T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

Truth


Table:

Characteristic Equation: $Q_{n+1} = \bar{T}Q_n + T\bar{Q}_n$

$Q_{n+1} = T \oplus Q_n$

Excitation Table:

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

 State Diagram:

Note: J-K FF is also known as universal flip flop.

	J	K	Q_{n+1}
SR FF	0	0	Q_n
	0	1	0
	1	0	1
	1	1	\bar{Q}_n

T.F.F.

SR FF

$$Q_{n+1} = S + \bar{R}Q_n$$

Jk FF

$$Q_{n+1} = J\bar{Q}_n + \bar{K}Q_n$$

D FF

$$Q_{n+1} = D$$

T FF

$$Q_{n+1} = T \oplus Q_n$$

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	x

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

D	Q_{n+1}
0	0
1	1

T	Q_{n+1}
0	Q_n
1	\bar{Q}_n

Excitation Table

Q_n	Q_{n+1}	S	R	J	K	D	T
0	0	0	x	0	x	0	0
0	1	1	0	1	x	1	1
1	0	0	1	x	1	0	1
1	1	x	0	x	0	1	0

Designing of Flip Flop:

- Step 1: Write the characteristic table of desired FF
- Step 2: Write the excitation table of available FF
- Step 3: Write the logical expression
- Step 4: Minimize the logical expressions
- Step 5: Hardware implementation.

Q3. Design JK Flip Flop using SR Flip Flop.

Step 1	J	K	Q _n	Q _{n+1}	S	R
Step 2	0	0	0	0	0	x
	0	0	1	1	x	0
	0	1	0	0	0	x
	0	1	1	0	0	1
	1	0	0	1	1	0
	1	0	1	1	x	0
	1	1	0	1	1	0
	1	1	1	0	0	1

Step 3: $S(J, K, Q_n) = \sum m(4, 5) + \sum d(1, 5)$

$R(J, K, Q_n) = \sum m(3, 7) + \sum d(0, 2)$

Step 4:



	J \ K \ Q _n	00	01	11	10
S →	0		x		
	1	1	x		1

$S = J\bar{Q}_n$

	J \ K \ Q _n	00	01	11	10
R →	0	x		1	x
	1			1	

$R = KQ_n$

Step 5:

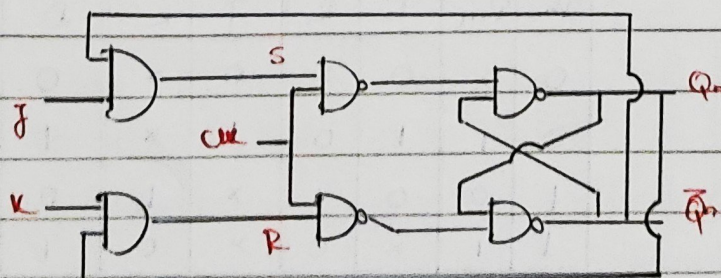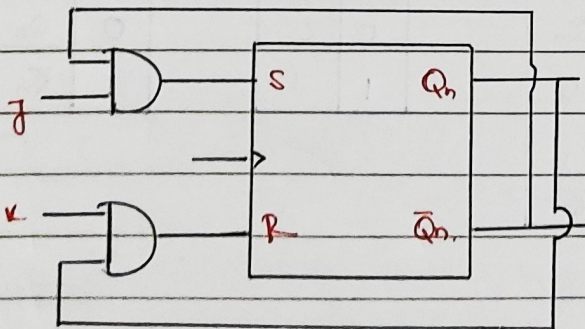

Q4. Design a D FF by using S-R FF.

Step 1:


D	Q_n	Q_{n+1}	S	R
0	0	0	0	x
0	1	0	0	1
1	0	1	1	0
1	1	1	x	0

Step 3 & Step 4:

D	Q_n	Q_{n+1}	S	R
0	0	0	0	1
0	1	0	0	1
1	0	1	1	0
1	1	1	0	0

$S = D$ $R = \bar{D}$

Steps:

 

Q5. Design a T-FF using S-R Flip Flop.

Step 1:


T	Q_n	Q_{n+1}	S	R
0	0	0	0	x
0	1	1	x	0
1	0	1	1	0
1	1	0	0	1

Step 3 & Step 4:

T	Q_n	Q_{n+1}	S	R
0	0	0	0	1
0	1	1	0	0
1	0	1	1	0
1	1	0	0	1

$S = T\bar{Q}_n$ $R = TQ_n$

Steps:

 


Q6. Design TFF using D-FF.

Step 1:

T	Q_n	Q_{n+1}	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

Step 3 & Step 4:
 $D = T \oplus Q_n$

Steps:

 

Q7. Design a CJ FF by using SR FF.

Truth Table:

C	J	Qn	Qn+1	S	R
0	0	0	1	1	0
0	0	1	0	0	1
0	1	0	0	0	x
0	1	1	1	x	0
1	0	0	1	1	0
1	0	1	1	x	0
1	1	0	0	0	x
1	1	1	0	0	1

C	J	Qn+1
0	0	\bar{Q}_n
0	1	Q_n
1	0	1
1	1	0

C/JK



C	00	01	11	10
0	1		x	
1	1	x		

$S = \bar{J}\bar{Q}_n$


C/JK

C	00	01	11	10
0		1		x
1		x	1	x

$R = \bar{Q}_n\bar{J}Q_n + CJ$

  


Shift Register

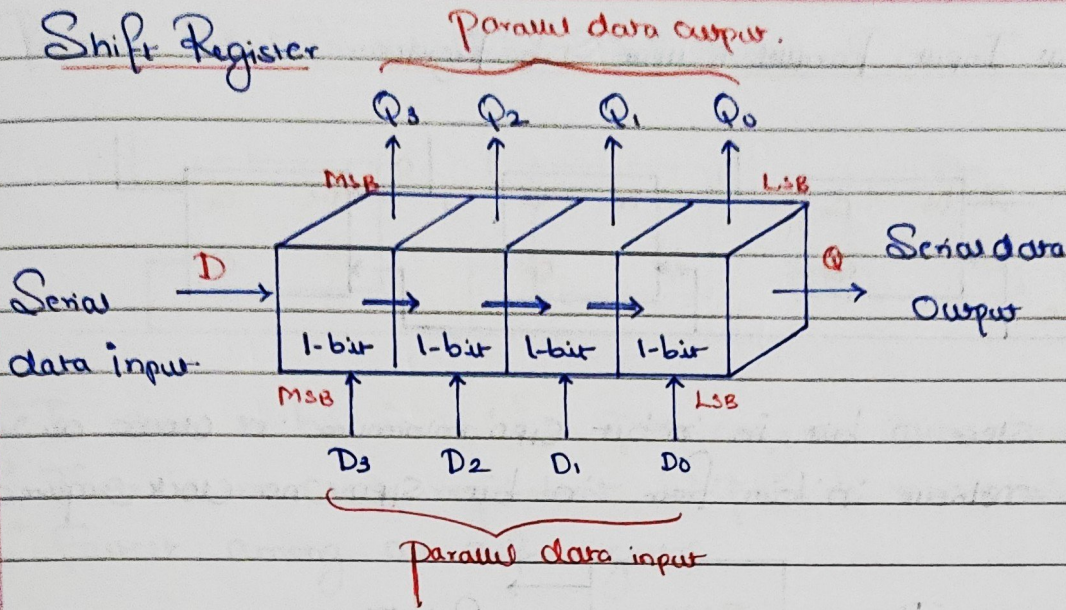

- * Registers are used to store group of bits
- * To store 'n' bits minimum 'n' flip flops are required.
- * Generally D Flip Flops are used to Design registers.

 1. Serial input Serial output shift register (SISO)
2. Serial input Parallel output shift register (SIPO)
3. Parallel input Serial output shift register (PISO)
4. Parallel input Parallel output shift register (PIPO)


Serial Input Serial Output Shift Register




Clock	Input	QA	QB	QC
0	101	0	0	0
1		1	0	0
2		0	1	0
3		1	0	1

- * To store 'n' bits in SISO minimum 'n' clocks are required
- * To retrieve 'n' bits from 'n' bit SISO minimum 'n' clocks are required
- * It is the slowest register among all the shift registers.

 Serial Input Parallel Output Shift Register



 
- * To store 'n' bit in 'n' bit SISO minimum 'n' clocks are required.
- * To retrieve 'n' bits from 'n' bit SISO no clock required.




Temporal code →

→ Spatial code.

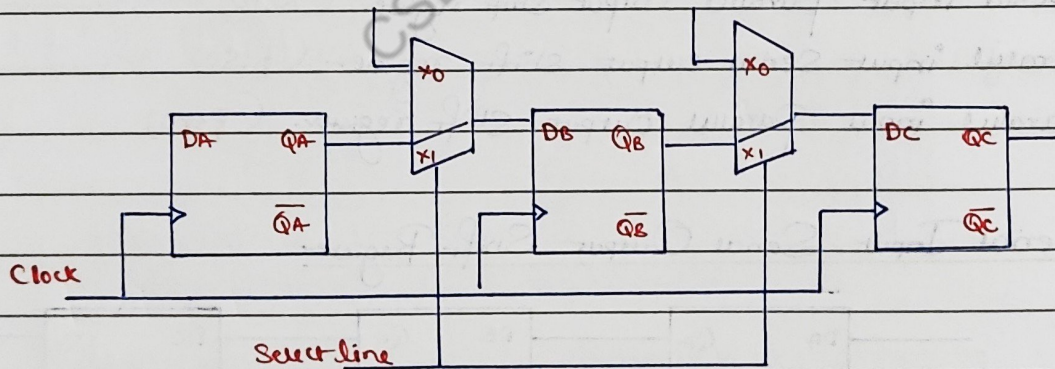
Parallel Input Serial Output Shift Register



 - * To store 'n' bits in PISO only one clock is required.
- * To retrieve 'n' bits from 'n' bit PISO minimum (n-1) clocks are required.



 
Parallel Input Parallel Output Shift Register.



- * To store 'n' bit in 'n' bit PISO only one clock is required.
- * There is no clock requirement in PISO to retrieve 'n' bits.
- * Fastest among all shift registers.

	Store	Retrieve	Total	
SISO	n	n-1	2n-1	→ Slowest
SIPO	n	0	n	
PISO	1	n-1	n	
PIPO	1	0	1	→ Fastest

 
Q1 Write the state of the register given below? Assume all flip flops are reset initially




Clock	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	1	0	0	0
6	0	1	0	0
7	0	0	1	0
8	0	0	0	1

HW

Q2 Output after 13th clock will be?

 

Q3. After 9th Clock the output will be?

 


Toggle Mode of flip flops.

1. T Flip Flop toggle mode.


$$Q_{n+1} = T \oplus Q_n$$

$$Q_{n+1} = 1 \oplus Q_n = \bar{Q}_n \Rightarrow Q_{n+1} = \bar{Q}_n$$

Toggle Mode

 


$$\left\{ \frac{f_{clk}}{2} \right\}$$

 

$$f_{clk} = \frac{1}{T_{clk}}$$

$$f_{Q_{n+1}} = \frac{1}{2T_{clk}} = \frac{f_{clk}}{2}$$


2. Jk Flip Flop toggle mode

 

$$J=1 \quad K=1$$

$$Q_{n+1} = J\bar{Q}_n + KQ_n = 1\bar{Q}_n + 1Q_n$$

$$Q_{n+1} = \bar{Q}_n$$

 


$$J = \bar{Q}_n \quad K = 1$$

$$Q_{n+1} = J\bar{Q}_n + KQ_n$$

$$Q_{n+1} = \bar{Q}_n \cdot \bar{Q}_n + 1 \cdot Q_n$$

$$Q_{n+1} = \bar{Q}_n$$

(iii)

 


$$J=1 \quad K=Q_n$$

$$Q_{n+1} = J\bar{Q}_n + KQ_n$$

$$= 1 \cdot \bar{Q}_n + \bar{Q}_n \cdot Q_n$$

$$Q_{n+1} = \bar{Q}_n$$

(iv)

 


$$J=\bar{Q}_n \quad K=1$$

$$Q_{n+1} = J\bar{Q}_n + KQ_n$$

$$= \bar{Q}_n \cdot \bar{Q}_n + 1 \cdot Q_n$$

$$Q_{n+1} = Q_n$$

3. Toggle Mode of SR Flip Flop

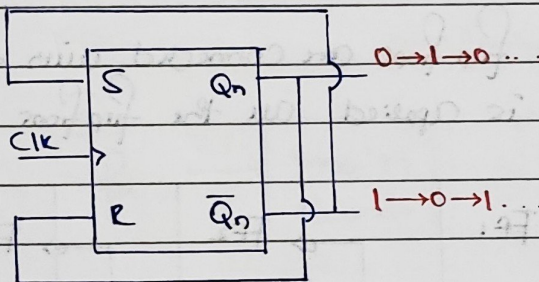


$$S=\bar{Q}_n \quad R=1$$

$$Q_{n+1} = S + \bar{R}Q_n$$

$$Q_{n+1} = \bar{Q}_n + \bar{1} \cdot Q_n$$

$$Q_{n+1} = \bar{Q}_n$$

4. D-Flip Flop Toggle Mode

 

$$D=\bar{Q}_n$$


$$Q_{n+1} = D$$

$$Q_{n+1} = \bar{Q}_n$$


Counters :

- * Counters are used to count number of clock
- * Counter are used as frequency divider circuit.
- * Counter are also used in ADC (Analog to Digital Converter)
- * Counters are also known as pulse stretcher circuit.

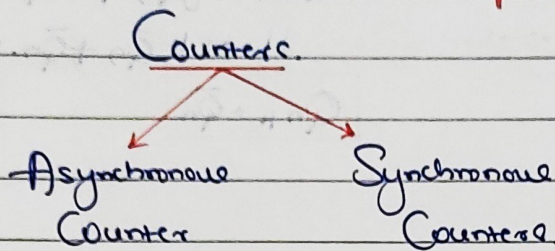
- * Counters also used in RADAR for detection of Range
↳ Radio detection & Ranging



 Asynchronous Counter: Only one flip flop having external clock and output of that flip flop will become clock for the next flip flop. So when clock applied only flip flop work at that time



 Synchronous Counter: All flip flops are connected with the same clock. Hence when the clock is applied all the flip flops work simultaneously.





	Asynchronous Counter	Synchronous Counter.
①	Only one FF having external clock and output of that FF will be clock for next FF.	All the FFs are connected with the same clock.
②	Slower.	Faster
③	Only increasing and decreasing counting possible.	All types of counting are possible.
④	There is transition error.	No transition error
⑤	Eg: Ripple counter	Eg: Ring counter, Johnson Counter.



Maximum no. of States = 2^n .

$\hookrightarrow n$: no. of FFs.

  Module of Counter: Total no. of States used by the counter are called mod of the counter.



Note: ① $\text{MOD}(m) \leq 2^n$.

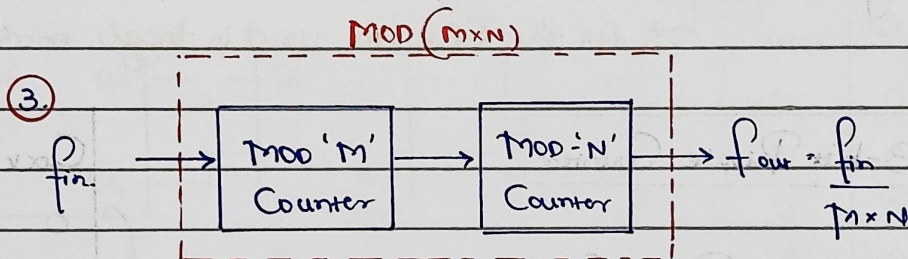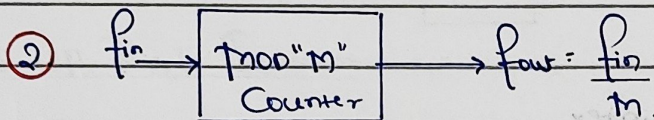

Bcd Counter:

0 \rightarrow 0000

1 \rightarrow 0001

2 \rightarrow 0010

3 \rightarrow 0011

4 \rightarrow 0100

5 \rightarrow 0101

6 \rightarrow 0110

7 \rightarrow 0111

8 \rightarrow 1000

9 \rightarrow 1001

MOD \rightarrow 10

$$M \leq 2^n$$

$$n \geq \log_2 M$$

$$n \geq \log_2 10$$


$$n \geq 3 \dots$$

$$n = 4$$

Q1. If mod-5 counter is cascaded with mod-2 counter, then it will become?

Ans. MOD-10 counter.

$MOD(5 \times 2) = MOD-10$

 


Q2. MOD-100, then no. of FF?

Ans $M \leq 2^n$
 $n \geq \log_2 M$
 $\geq \log_2 100$
 ≥ 6.64

$n \geq 7$


Asynchronous Counter

→ All the FFs are used in toggle mode.

 

3-bit Ripple Counter

MOD-8 UP Ripple Counter:

 



Clock	QC	QB	QA
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0
9	0	0	1
10	0	1	0

→ QA will toggle when the edge of the external clock appears.


→ QB will toggle when QA goes from 1 to 0

MOD-8 DOWN Ripple Counter:

 

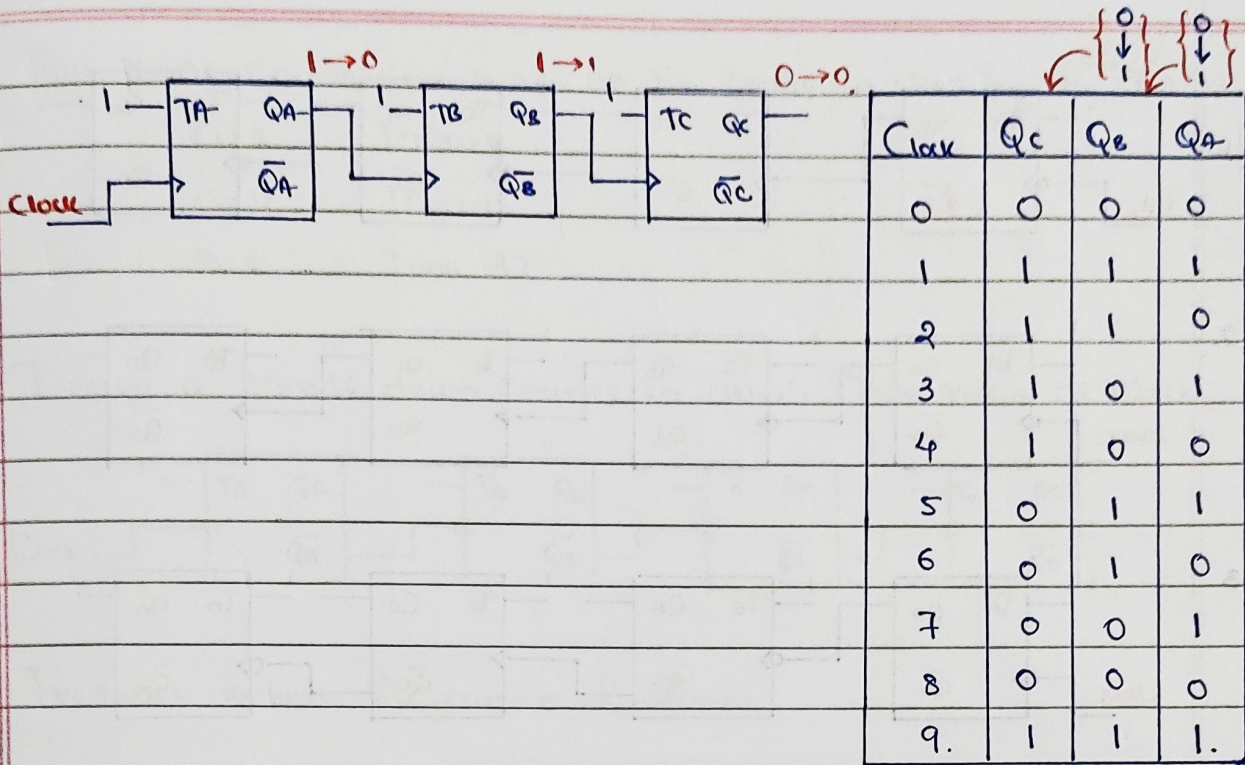


MOD-8 UP Ripple Counter





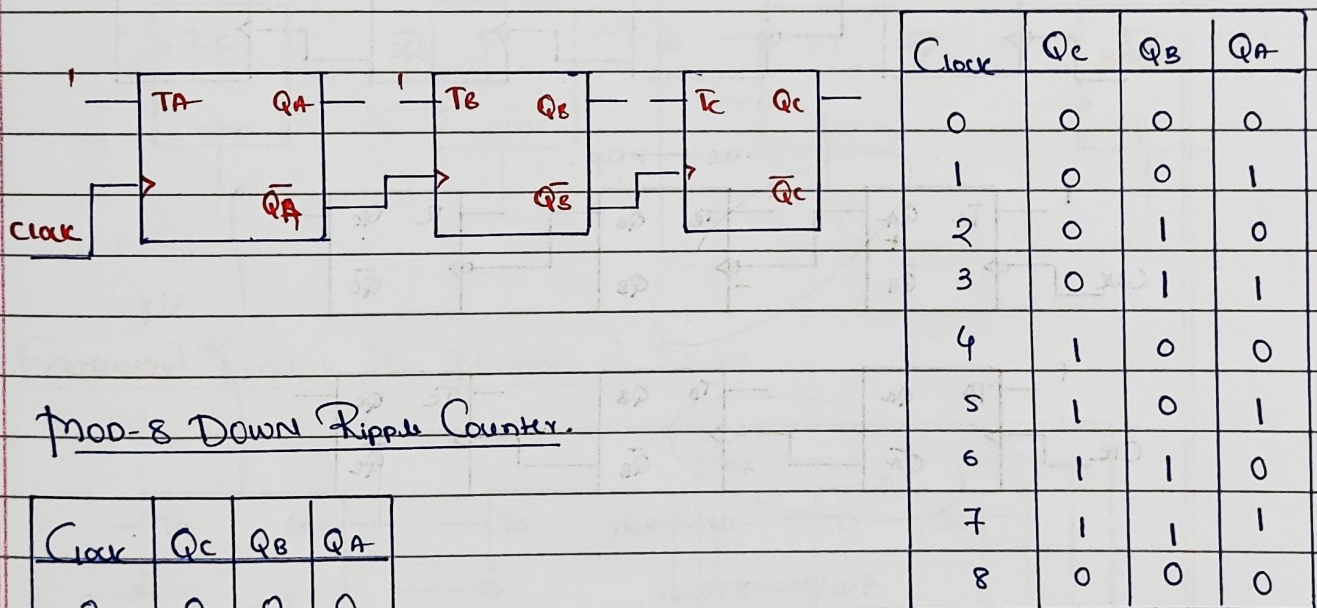


MOD-8 DOWN Ripple Counter



Clock	Qc	Qb	Qa
0	0	0	0
1	1	1	1
2	1	1	0
3	1	0	1
4	1	0	0
5	0	1	1
6	0	1	0
7	0	0	1
8	0	0	0

 


HW

     

UP Counter.

  

DOWN Counter.

 

(-x = +)


→ Full Mode Counter → when all the states are used by the counter.

$n=3$ $MOD=8$

$n=4$ $MOD=16$


$n=5$ $MOD=32$

 Q1. Design a MOD 16 down counter in which \bar{Q} is taken as clock.




→ Feedback reduces the number of states:


RESET - Clear

 

PRESET

 

Feedback Reduces the Number of States

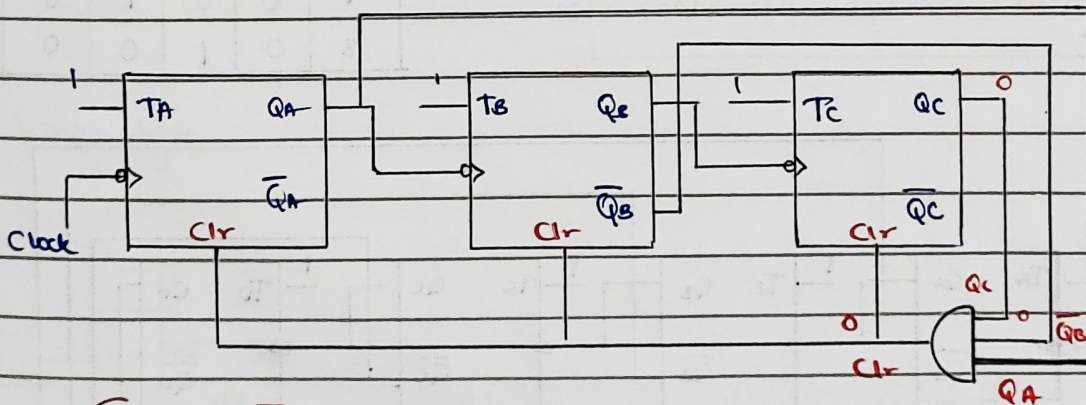


$Clr = QC \bar{Q}_B Q_A$

$= 101$


$= 5$

Clock	Qc	Qb	Qa	CLR = QcQbQA
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	↗ ⁰	↗ ⁰	↗ ⁰	↗ ⁰
6	0	0	1	0
7	0	1	0	0
8	0	1	1	0

 

MOD-6 UP Ripple Counter

$Clr = QcQbQA$

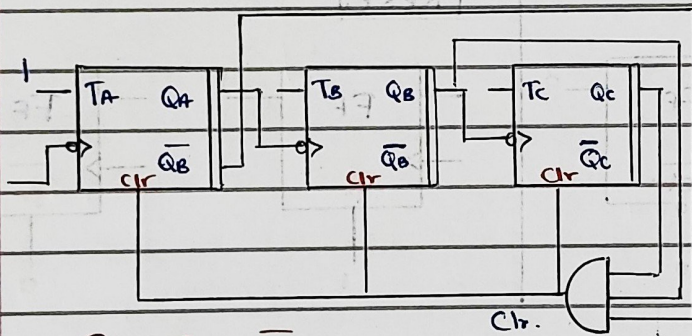

Clock	Qc	Qb	Qa	Clr
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	0
6	↗ ⁰	↗ ⁰	↗ ⁰	↗ ⁰
7	0	0	1	0
8	0	1	0	0

$Clr = QcQbQA$


$QcQbQA$

$110 \Rightarrow 6$

000 → 001 → 010 → 011 → 100 → 101



Q.2

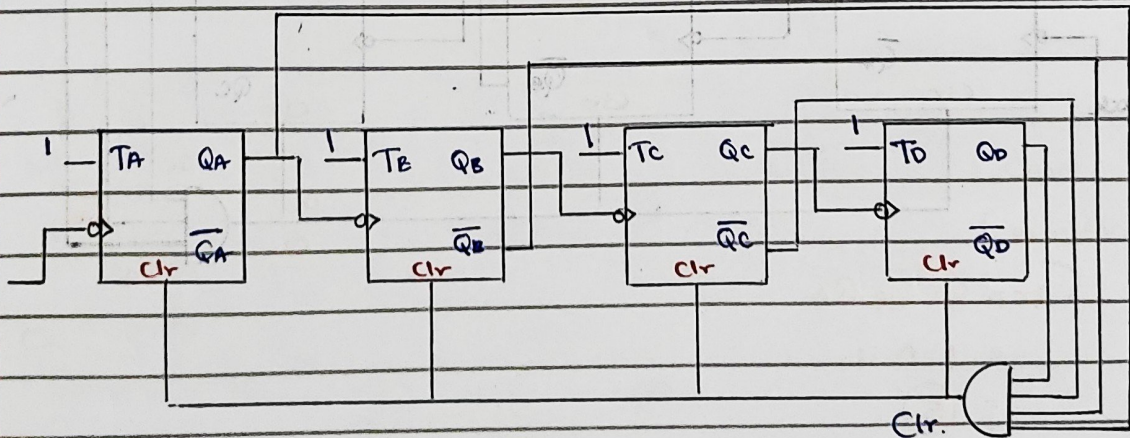

MOD-9 UP Ripple Counter.


$Clr = QdQcQbQA$

$1001 \rightarrow 9$

Clock	Q ₀	Q ₁	Q ₂	Q ₃	Clr
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1 ⁰	0 ⁰	0 ⁰	1 ⁰	1 ⁰
10	0	0	0	1	
11	0	0	1	0	


$Clr = Q_0 \bar{Q}_1 \bar{Q}_2 \bar{Q}_3 Q_4$
1 0 0 1 \Rightarrow (9)

Q3 Design a BCD Ripple Carry Counter.

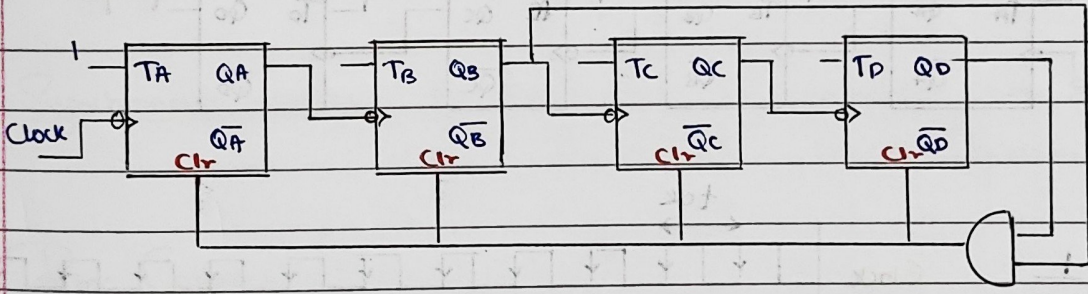

$Clr = Q_0 \bar{Q}_1 \bar{Q}_2 \bar{Q}_3 Q_4$
1 0 1 0
 \Rightarrow (10)


Q4 Which type of counter is shown below?

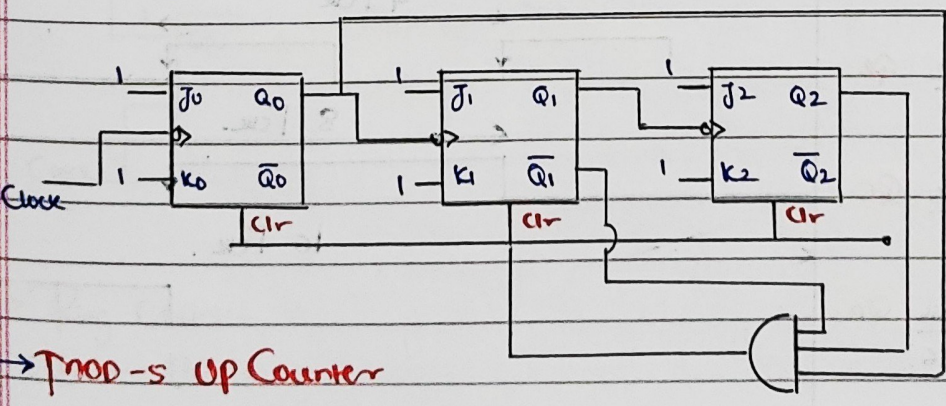

$Clr = Q_2 \bar{Q}_1 \bar{Q}_0$
1 0 1 \Rightarrow (5)



\rightarrow MOD-5 UP Counter

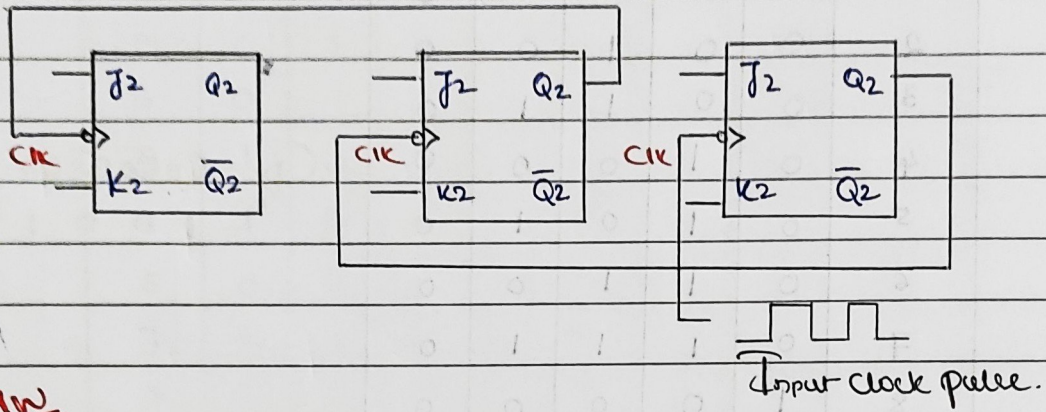HW
Q5. Consider the following clock. If Counter starts at 000, what will be count after 13 clock pulses?




HW
Q6. Design MOD-13, MOD-21, MOD-27, MOD-14 (Ailerp) Ripple Counter

Asynchronous [Ripple Counter]

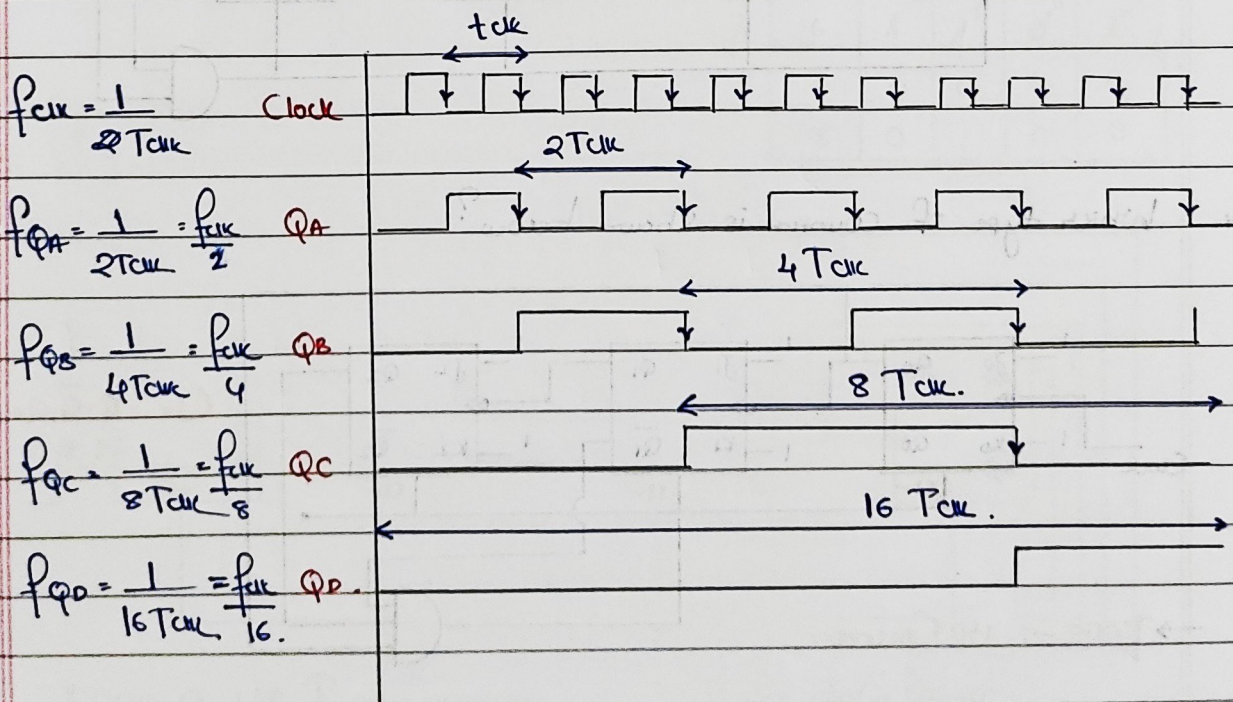 

Asynchronous Counter.

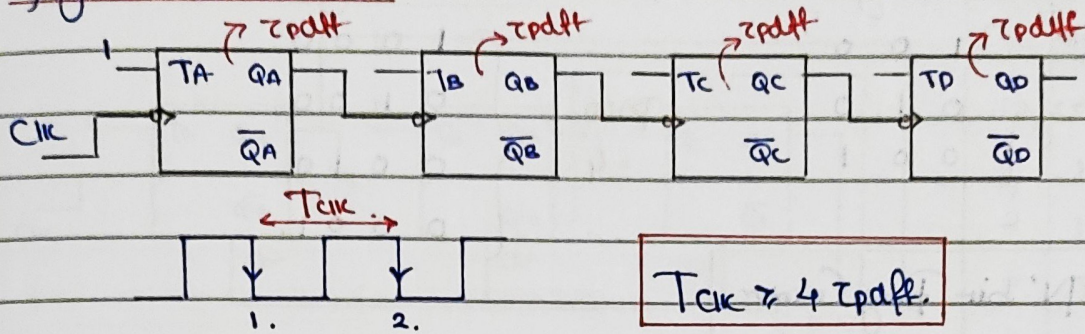

$$T_{clk} \geq 4 \tau_{pdff}$$

'N' bit asynchronous counter

$$T_{clk} \geq n \cdot \tau_{pdff}$$

$$f_{clk} \max = \frac{1}{n \cdot \tau_{pdff}}$$


$$\frac{1}{T_{clk}} \leq \frac{1}{n \cdot \tau_{pdff}}$$

$$f_{clk} \leq \frac{1}{n \cdot \tau_{pdff}}$$

Synchronous Counter : All the Flip Flops are Synchronized with same clock
eg: Ring Counter, Johnson Counter.


Ring Counter

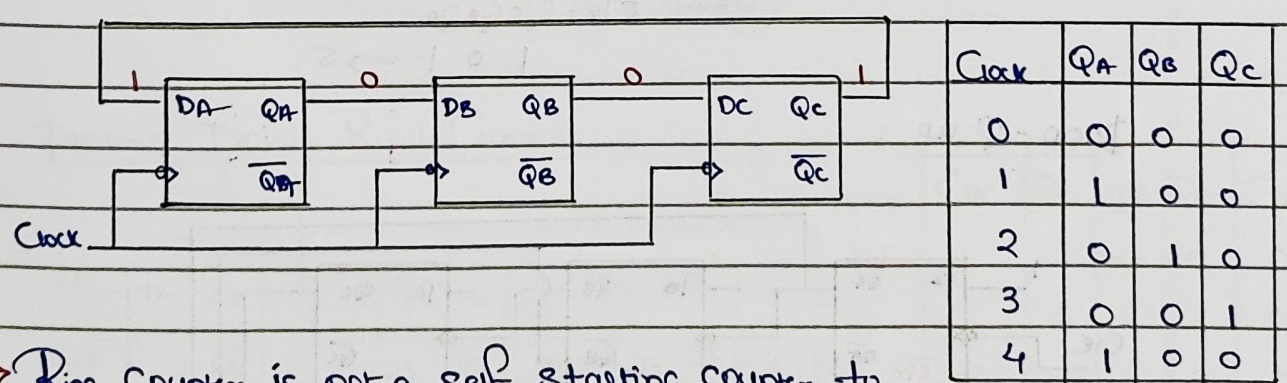→ It is also a SISO shift register in the form of Ring.




→ Ring Counter is not a self starting counter, to start the ring counter we have to place '1' at the MSB and that '1' will rotate among all the flip flops.

3 bit Ring Counter

 


4 bit Ring Counter

 

'N' bit Ring Counter
⇒ MOD=N

Self Starting Ring Counter

 


Clock	QA	QB	QC
0	0	0	0
1	1	0	0
2	0	1	0
3	0	0	1
4	1	0	0

MOD=3

H/W
Assure
of previous
class?


MOD-5 UP

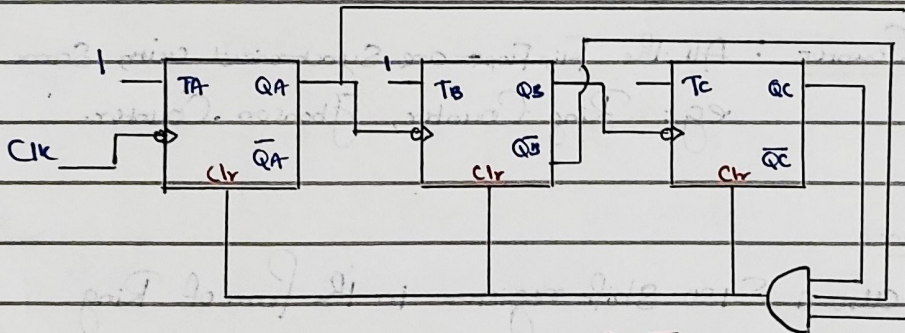


$$CLR = QC \bar{QB} QA$$

1 0 1 ⇒ 5

MOD-2 UP

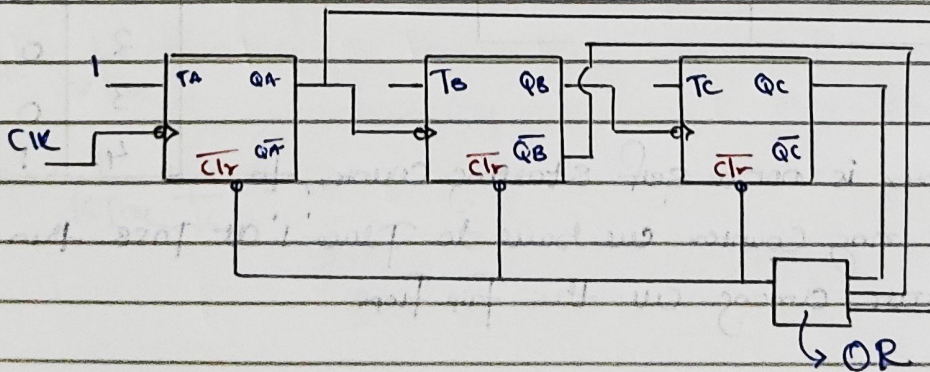

MOD-3 Down Ripple Counter

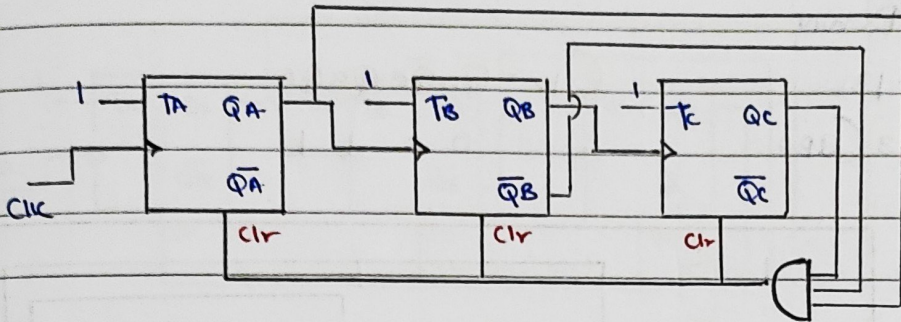

Clk	Qc	Qb	Qa	Clr
0	0	0	0	0
1	1	1	1	0
2	1	1	0	0
3	X ^o	X ^o	X ^o	X ^o
4	1	1	1	0
5	1	1	0	0
6	X ^o	X ^o	X ^o	X ^o

111 → 110 → 000


$Clr = QcQbQA$

Down = Full-up

$= 8 - 5$

$= 3$

MOD-4 Down Ripple Counter

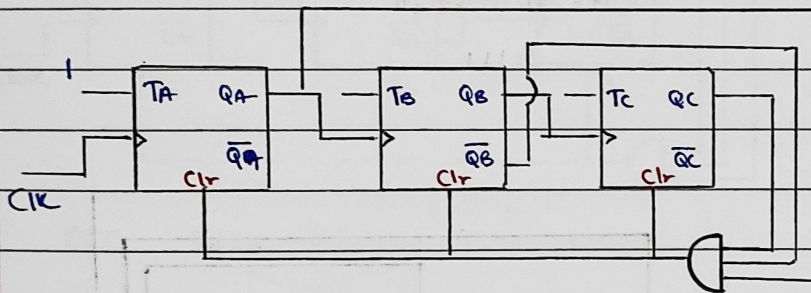

Clock	Qc	Qb	Qa	Clr
0	0	0	0	0
1	1	1	1	0
2	1	1	0	0
3	1	0	1	0
4	X ^o	X ^o	X ^o	X ^o

111 → 110 → 101 → 000


$Clr = QcQbQA$

100

Down = Full-up

$= 8 - 4 = 4$

MOD-5 Down Ripple Counter

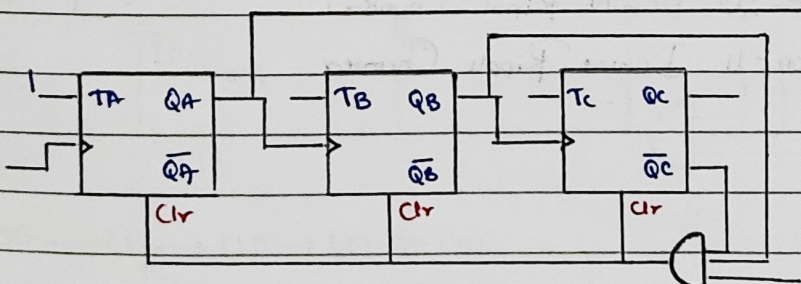

Clk	Qc	Qb	Qa	Clr
0	0	0	0	0
1	1	1	1	0
2	1	1	0	0
3	1	0	1	0
4	1	0	0	0
5	X ^o	X ^o	X ^o	1

111 → 110 → 101 → 100 → 000

Down = Full-up

$(5) = 8 - 3$

$\bar{Qc}QbQA$

$011 \rightarrow 3$

Q1. Design a mod-13 DOWN Ripple Counter.


Full-up = DOWN

$$16 - \text{UP} = 13$$

$$16 - 13 = 3 \text{ (UP)}$$

$$\text{Clr} = \overline{Q_D} \overline{Q_C} Q_B Q_A$$

$$0011$$

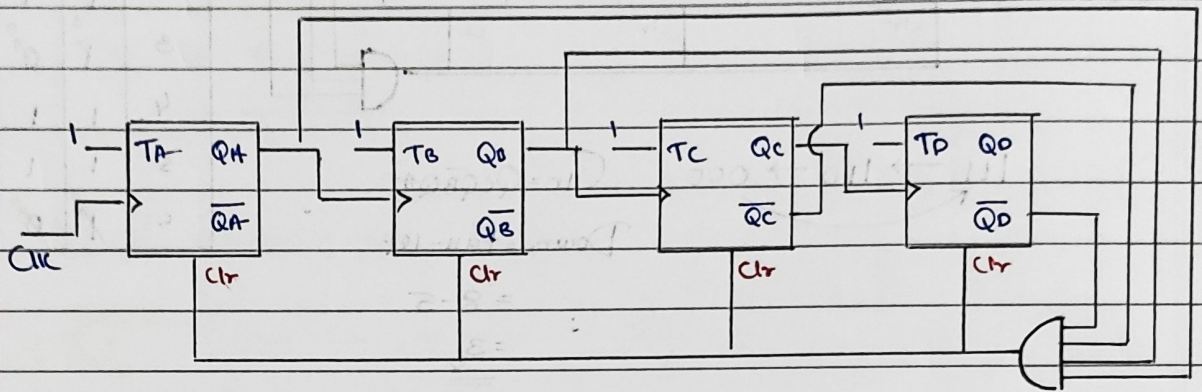

Q2. Design a mod-9 DOWN Ripple Counter.


Full-up = DOWN

$$16 - \text{UP} = 9$$

$$\text{UP} = 16 - 9 = 7$$

$$\text{Clr} = \overline{Q_D} Q_C Q_B Q_A$$

$$0111$$

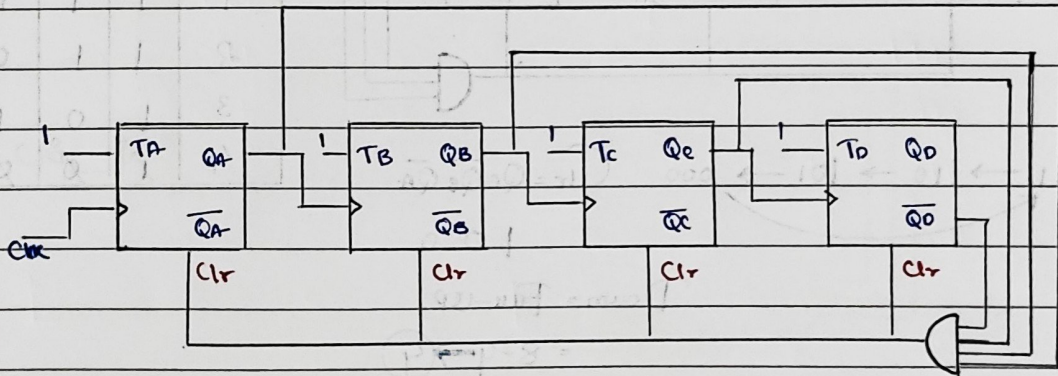


Q3. Design a mod-19 DOWN Ripple Counter.

Q4. Design a mod-23 DOWN Ripple Counter.

Q5. Design a mod-11 DOWN Ripple Counter.

MOD-6

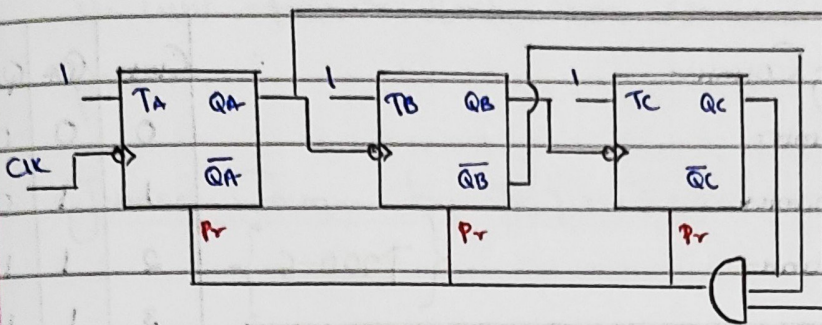


000 → 001 → 010 → 011 → 100 → 111

$Pr = Q_C Q_B Q_A$

Clock	Qc	Qb	Qa	Pr
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	X ¹	X ¹	X ¹	X ¹
6	0	0	0	0
7	0	0	1	0


MOD-2

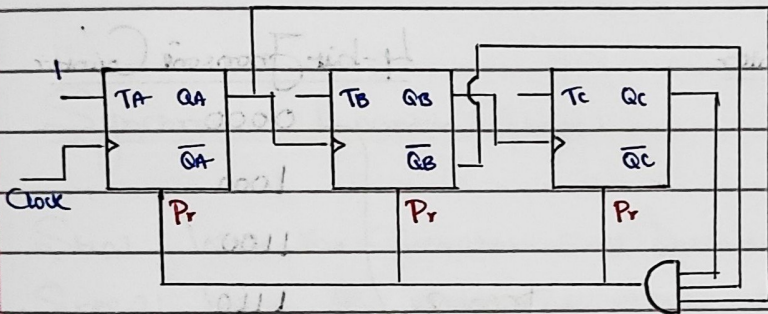

000 → 111 → 110

Clock	Qc	Qb	Qa	Pr
0	0	0	0	0
1	1	1	1	0
2	1	1	0	0
3	X ¹	X ¹	X ¹	X ⁰
4	1	1	0	0
5	X ¹	X ¹	X ¹	X ⁰
6	1	1	0	0
7	X ¹	X ¹	X ¹	1 ⁰

MOD-4

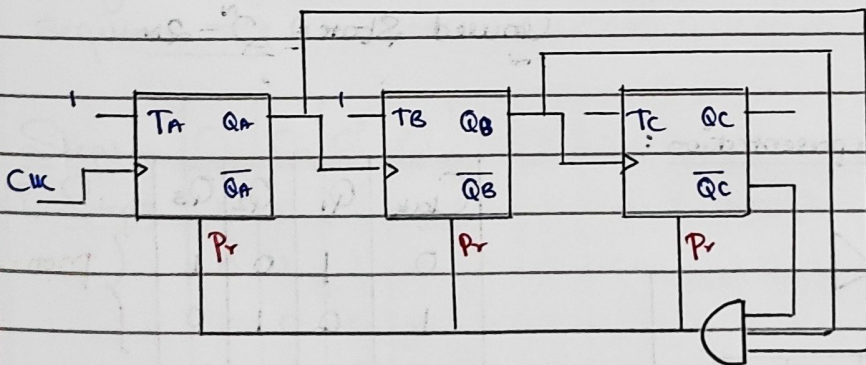

000 → 111 → 110 → 101 → 100

CLK	Qc	Qb	Qa	Pr
0	0	0	0	0
1	1	1	1	0
2	1	1	0	0
3	1	0	1	0
4	1	0	0	0
5	X ¹	X ¹	X ¹	X ⁰
6	1	1	0	0
7	1	0	1	0

Johnson Counter

Twisted Ring Counter

Creeping Counter

Mobius Counter

Walking Counter

Clock	QA	QB	QC
0	0	0	0
1	1	0	0
2	1	1	0
3	1	1	1
4	0	1	1
5	0	0	1
6	0	0	0
7	1	0	0

3 bit Johnson Counter

- Mod 6
- 000
 - 100
 - 110
 - 111
 - 011
 - 001


4-bit Johnson Counter

- Mod 8
- 0000
 - 1000
 - 1100
 - 1110
 - 1111
 - 0111
 - 0011
 - 0001

→ N bit Johnson Counter ⇒ mod (used state) = 2N

Unused state = 2^N - 2N

Symbolic Representation:

 


Clock	Q1	Q2	Q3
0	1	0	1
1	0	1	0
2	1	0	1
3	0	1	0
4	1	0	1

Mod-2

Lockout Problem!

Lockout Problem: Whenever Johnson Counter enters its unused state, it will trap or lock into unused state, are called Lockout Problem.

Johnson Counter by JK Flip Flop

 

Synchronous Counter Design:

- Step 1: Write the Previous and Present State
- Step 2: Write the excitation table of flip flop
- Step 3: Write the logical expression
- Step 4: Minimise the logical expression
- Step 5: Hardware implementation

Q1. Design a Synchronous Counter using "T" Flip Flop which count the sequence $\Rightarrow 0-3-1-2-0 \dots$ $\{ \infty - 11 - 01 - 10 \rightarrow \infty \dots \}$
 \hookrightarrow 2 FFs are required.

Step 1: & Step 2	Q_1	Q_0	Q_1^+	Q_0^+	T_1	T_0
	0	0	1	1	1	1
	0	1	1	0	1	ϕ
	1	0	0	0	1	0
	1	1	0	1	1	0

Step 3

& Step 4:


$$T_1 = 1$$

$$T_0 = \bar{Q}_1 \bar{Q}_0 + \bar{Q}_1 Q_0$$

$$T_0 = \bar{Q}_1 [\bar{Q}_0 + Q_0]$$

$$T_0 = \bar{Q}_1$$

Steps:

 

Justification:

Clock	Q ₁	Q ₀
0	0	0
1	1	1
2	0	1
3	1	0

Q2. Design a Synchronous Counter by using 'D' Flip Flops which count the Sequence 00 - 11 - 01 - 00

Method 1

Step 1 &

Step 2

Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺	D ₁	D ₀
0	0	1	1	1	1
1	1	0	1	0	1
0	1	0	0	0	0

Step 3 &


$$D_1 = \bar{Q}_1 \bar{Q}_0$$

Step 4

$$D_0 = \bar{Q}_1 \bar{Q}_0 + Q_1 Q_0$$

$$D_0 = Q_1 \odot Q_0$$


Step 5:

 


Clock	Q ₁	Q ₀
0	0	0
1	1	1
2	0	1
3	0	0

Method 2


Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺	D ₁	D ₀
0	0	1	1	1	1
0	1	0	0	0	0
1	0	x	x	x	x
1	1	0	1	0	1

 


$$D_1 = \bar{Q}_0$$

 

$$D_0 = Q_1 + \bar{Q}_0$$

 

Clock	Q ₁	Q ₀
0	0	0
1	1	1
2	0	1
3	0	0
4	1	1
5	0	1

 

No Lockout!

HW


Q3. Design a synchronous counter by using D-FF which count:
000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000 ...

Q4. Design a synchronous counter by using T-flip flop which count the sequence 0 → 2 → 3 → 0


00 → 10 → 11 → 00 2 bits → 2 flip flops are required

Method 1

Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺	T ₁	T ₀
0	0	1	0	1	0
1	0	1	1	0	1
1	1	0	0	1	1

 

 
$T_1 = \underline{Q_1 \oplus Q_0}$
 $T_0 = \underline{Q_1}$




Clock	Q ₁	Q ₀
0	0	0
1	1	0
2	1	1
3	0	0


Method 2

Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺	T ₁	T ₀
0	0	1	0	1	0
0	1	x	x	x	x
1	0	1	1	0	1
1	1	0	0	1	1

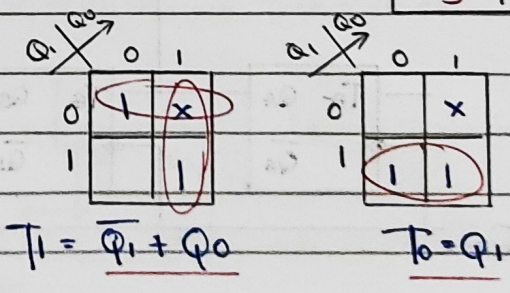

 


No Lockout Problem!

 

 Q1. Design a synchronous counter by using T Flip Flop which count the sequence $0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 4 \rightarrow 5 \rightarrow 6 \rightarrow 7 \rightarrow 0$.

Three bit \rightarrow Three Flip Flops Required

$\rightarrow T_A = 1, T_B = Q_A, T_C = Q_A Q_B$



$$T = T_{pdff} + T_{pdAND}$$


$$\frac{1}{T_{clk}} \leq \frac{1}{T_{pdff} + T_{pdAND}}$$

$$T_{clk} \geq T_{pdff} + T_{pdAND}$$

$$f_{clk} \leq \frac{1}{T_{pdff} + T_{pdAND}}$$

4 bit

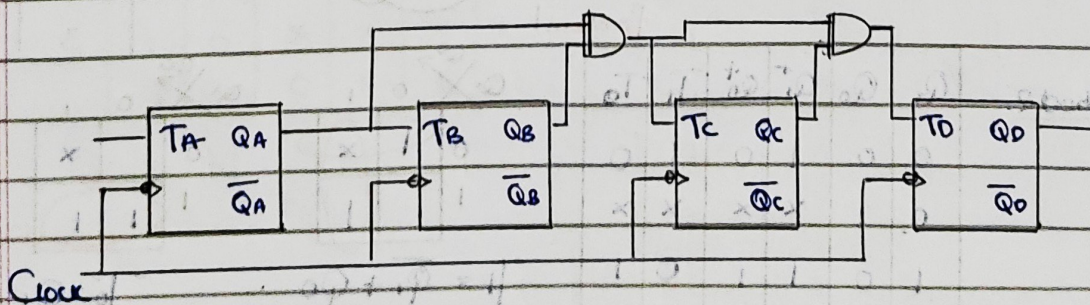$T_A = 1, T_B = Q_A, T_C = Q_A \cdot Q_B, T_D = Q_A \cdot Q_B \cdot Q_C$



$$T_{clk} \geq T_{pdff} + 2 \cdot T_{pdAND}$$


$$f_{clk} \leq \frac{1}{T_{pdff} + 2 T_{pdAND}}$$

Serial Carry Synchronous Counter:

$$T_{clk} \geq T_{pdff} + (N-2) T_{pdAND}$$

$$f_{clk} \leq \frac{1}{T_{pdff} + (N-2) T_{pdAND}}$$

Parallel Carry Synchronous Counter:

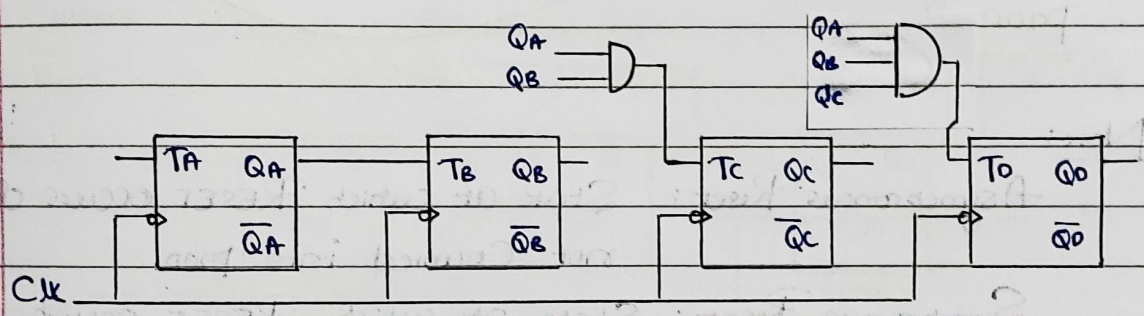


$$T_{clk} \geq T_{pdff} + T_{pdAND}$$

$$f_{clk} \leq \frac{1}{T_{pdff} + T_{pdAND}}$$


Q1. Minimum no. of flip flops required to construct BCD counter is
 Ans. 0000 } 4 bits → Four Flip Flops.
 1001 }

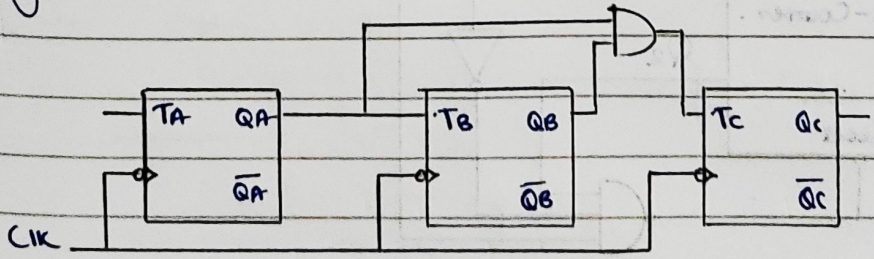Q2. Minimum no. of Flip Flops required to design counter state given below 0 → 0 → 1 → 1 → 2 → 2 → 3 → 3 → 0 → 0 ...



3 bit Synchronous up Counter
 ⇒ 3 Flip Flops Required

Q3. What is the mod of the counter?

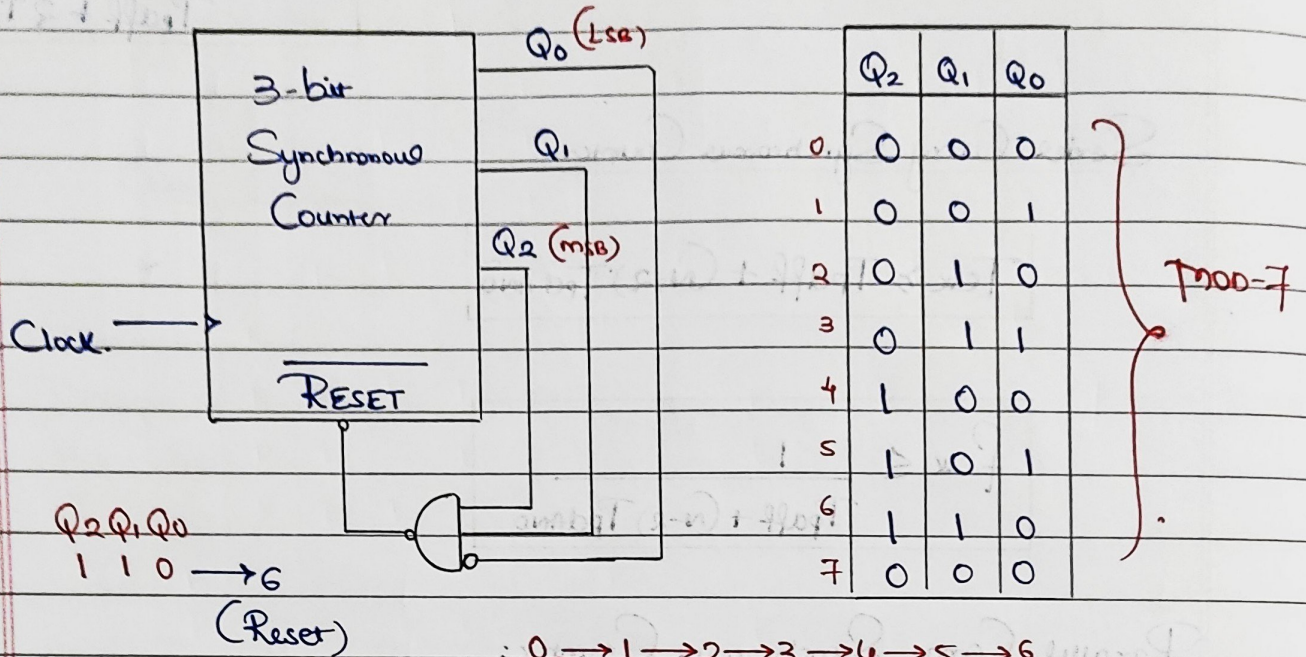

Q₂ Q₁ Q₀
1 1 0 → 6

(Reset)

0 → 1 → 2 → 3 → 4 → 5 → 6

MOD=7


Note:


Asynchronous Reset: State at which RESET occurs does not counted into mod.

Synchronous Reset: State at which RESET occurs is counted into mod.

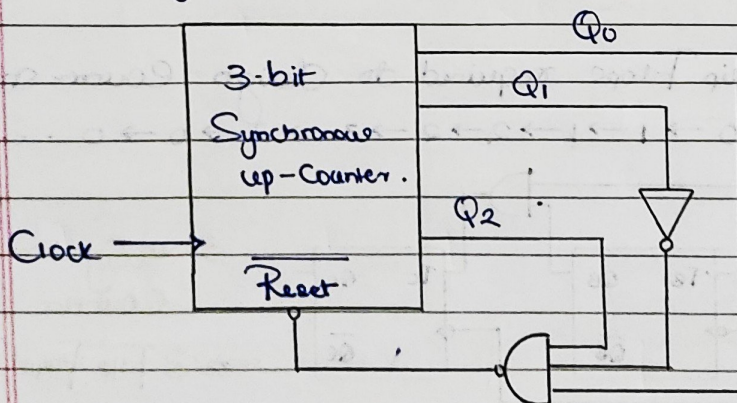Q4. Consider the below circuit:

The delay of NAND, NOR, gate is 3ns, 1ns respectively and that of the counter is assumed to be zero. If the clock frequency is 500 kHz, then the counter behaves as:



 

$Cir = Q_2 \bar{Q}_1 Q_0$


$f_{clk} = 500 \times 10^6 \text{ Hz}$

$T_{clk} = \frac{1}{500 \times 10^6} \text{ Sec} = \frac{1000 \times 10^{-9}}{500}$

$\therefore T_{mod} = 7$



$= 2nd$

 Q5. Consider the Circuit below with initial state $Q_0 = 1, Q_1 = Q_2 = 0$. The state of the circuit is given by the value of $4Q_2 + 2Q_1 + Q_0$. Which of the following is the correct state sequence of the circuit?



Sequence : 1 → 2 → 5 → 3 → 7 → 6 → 4

  Q6. Consider the circuit given below. The duty cycle of Y_2 is



Duty Cycle = $\frac{T_{on}}{T_{on} + T_{FF}} \times 100$

A	B	C	D	P	Q	Y ₀	Y ₁	Y ₂	Y ₃
0	0	0	0	0	1	0	1	0	0
0	0	0	1	1	1	0	0	0	1
0	0	1	0	1	1	0	0	0	1
0	0	1	1	0	1	0	1	0	0
0	1	0	0	0	0	1	0	0	0
0	1	0	1	1	0	0	0	1	0
0	1	1	0	1	0	0	0	1	0
0	1	1	1	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0	1	0


$10T = \text{Total time}$

$3T = T_{on}$

$D = \frac{3T}{10T} \times 100\%$

$= 30\%$

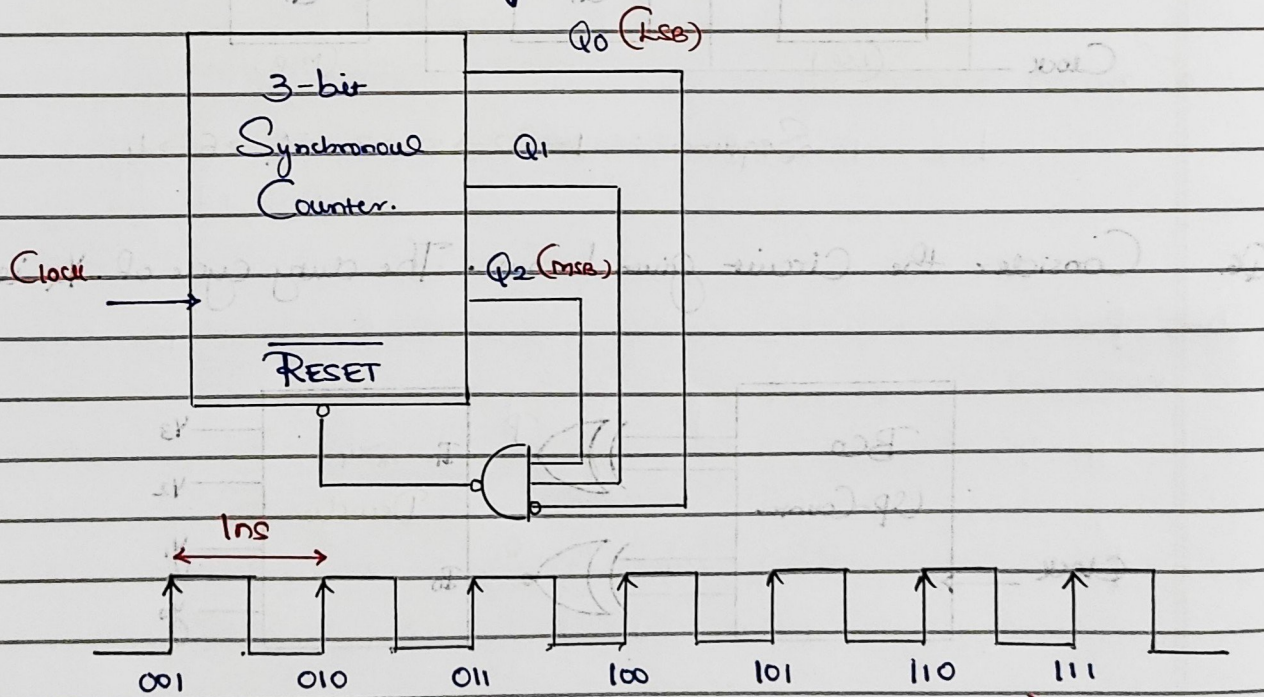Q7. For the circuit shown in the figure, the delay of the bubbled NAND gate is 2ns and that of the counter is assumed to be zero. If the clock frequency is 1GHz, then counter behaves as a:




$T_{clk} = \frac{1}{f_{clk}} = \frac{1}{1 \times 10^9} = 1 \text{ ns}$

⇒ MOD-8 Counter

NUMBER SYSTEM

Base (Radix)

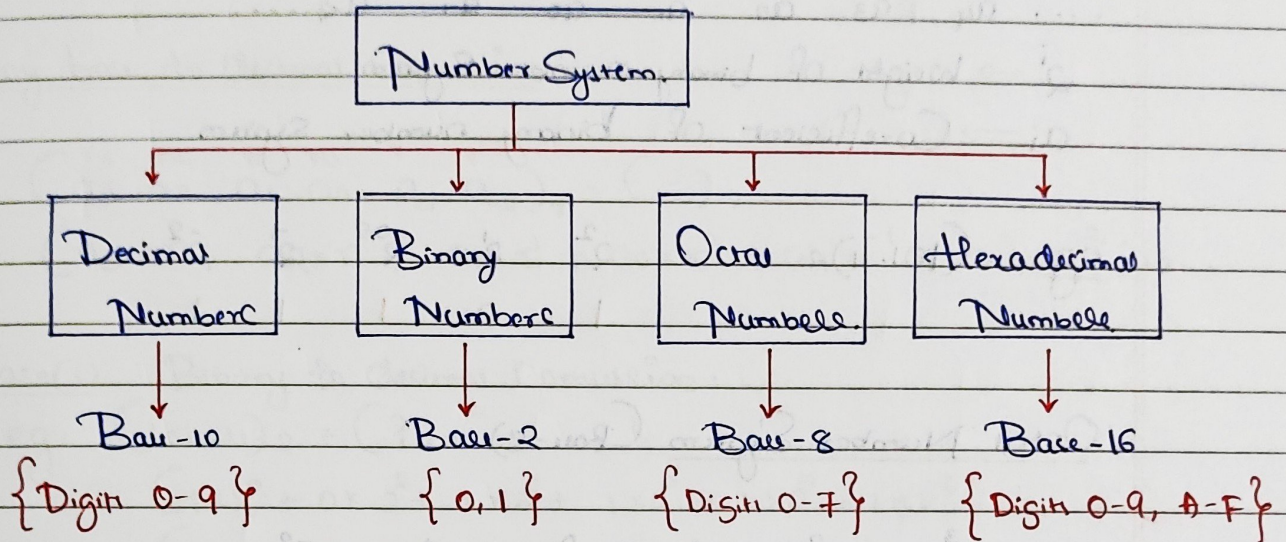Total number of digits used in the system.



Decimal Number System:

$$\dots \dots \dots 10^4 \quad 10^3 \quad 10^2 \quad 10^1 \quad 10^0 \quad 10^{-1} \quad 10^{-2} \quad 10^{-3} \dots \dots$$

$$\dots \dots \dots a_4 \quad a_3 \quad a_2 \quad a_1 \quad a_0 \quad a_{-1} \quad a_{-2} \quad a_{-3} \dots \dots$$

$a_i \rightarrow$ Co-efficient of decimal number system.

$10^i \rightarrow$ Weight of decimal number system.

eg: $(501.23)_{10}$

$$10^2 \quad 10^1 \quad 10^0 \quad 10^{-1} \quad 10^{-2}$$

$$5 \quad 0 \quad 1 \quad 2 \quad 3$$

Base	Digit
2	0 1
3	0 1 2
4	0 1 2 3
⋮	⋮ ⋮ ⋮
14	0 1 2 3 4 5 6 7 8 9 A B C D
15	0 1 2 3 4 5 6 7 8 9 A B C D E
16	0 1 2 3 4 5 6 7 8 9 A B C D E F

Binary Number System (Base=2)

$$\dots 2^4 \quad 2^3 \quad 2^2 \quad 2^1 \quad 2^0 \quad 2^{-1} \quad 2^{-2} \dots$$

$$\dots a_4 \quad a_3 \quad a_2 \quad a_1 \quad a_0 \quad a_{-1} \quad a_{-2} \dots$$

$2^i \rightarrow$ weight of binary number system

$a_i \rightarrow$ Co-efficient of binary number system

eg: $(101.11)_2$

2^2	2^1	2^0	2^{-1}	2^{-2}
1	0	1	1	1

Octal Number System (Base=8)

$$\dots 8^3 \quad 8^2 \quad 8^1 \quad 8^0 \quad 8^{-1} \quad 8^{-2} \dots$$

$$\dots a_3 \quad a_2 \quad a_1 \quad a_0 \quad a_{-1} \quad a_{-2} \dots$$

$8^i \rightarrow$ weight of Octal number system

$a_i \rightarrow$ Co-efficient of Octal number system $\{0-7\}$

eg: $(720.64)_8$

8^2	8^1	8^0	8^{-1}	8^{-2}
7	2	0	6	4

Hexadecimal Number System (Base=16)

$$\dots 16^3 \quad 16^2 \quad 16^1 \quad 16^0 \quad 16^{-1} \quad 16^{-2} \dots$$

$$\dots a_3 \quad a_2 \quad a_1 \quad a_0 \quad a_{-1} \quad a_{-2} \dots$$

$16^i \rightarrow$ weight of hexadecimal number system

$a_i \rightarrow$ Co-efficient of hexadecimal number system $\{0-9, A-F\}$

eg: $(A2C.F)_{16}$

16^2	16^1	16^0	16^{-1}
A	2	C	F

In base Conversion there are two key points:

- I. Any base to decimal conversion.
- II. Decimal to any other base conversion.

Any base to decimal conversion:

$$(a_3 a_2 a_1 a_0 . a_{-1} a_{-2})_r = ()_{10}$$

$$(a_3 \times r^3 + a_2 \times r^2 + a_1 \times r^1 + a_0 \times r^0 + a_{-1} \times r^{-1} + a_{-2} \times r^{-2})_{10}$$

Case (1) : Binary to decimal conversion.

$$\text{eg: } (1011.11)_2 = (?)_{10}$$

$$= (1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2})$$

$$= (8 + 0 + 2 + 1 + 0.5 + 0.25)$$

$$= (11.75)_{10}$$

Case (2) : Octal to decimal conversion

$$\text{eg: } (721.4)_8 = (?)_{10}$$

$$= (7 \times 8^2 + 2 \times 8^1 + 1 \times 8^0 + 4 \times 8^{-1})$$

$$= (448 + 16 + 1 + 0.5)$$

$$= (465.5)_{10}$$

Case (3) : Hexadecimal to decimal conversion

$$\text{eg: } (A2B.C)_{16} = (?)_{10}$$

$$= (A \times 16^2 + 2 \times 16^1 + B \times 16^0 + C \times 16^{-1})$$

$$= (10 \times 256 + 2 \times 16 + 11 \times 1 + 12 \times 16^{-1})$$

$$= (2663.75)_{10}$$

Case (4) : Base 5 to decimal conversion

$$\text{eg: } (432.22)_5 = (?)_{10}$$

$$= (4 \times 5^2 + 3 \times 5^1 + 2 \times 5^0 + 2 \times 5^{-1} + 2 \times 5^{-2})$$

$$= (100 + 15 + 2 + 0.4 + 0.08)$$

$$= (117.48)_{10}$$

Q1.

$$(62c) = (?)_{10}$$

By minimum base Convert into decimal:

$$(62c)$$

↳ 13, 14, 15, minimum = 13.

$$= (6 \times 13^2 + 2 \times 13^1 + c \times 13^0)$$

$$= (1052)_{10}$$

Decimal to any other base Conversion:

r	a_3	a_2	a_1	a_0	Remainder	$a_3 a_2 a_1 a_0$	$a_{-1} a_{-2}$
					b_0		
					b_1		
					b_2		
					b_3		

Before decimal
After decimal

$$\begin{aligned}
 0. a_1 a_2 a_3 \times r &= x_0 \cdot x_1 x_2 && x_0 \\
 0. x_1 x_2 \times r &= x_1 \cdot x_3 x_4 && x_1 \\
 0. x_3 x_4 \times r &= x_2 \cdot x_5 x_6 && x_2
 \end{aligned}$$

$$(a_3 a_2 a_1 a_0 . a_{-1} a_{-2} a_{-3})_{10} = (b_3 b_2 b_1 b_0 . x_0 x_1 x_2)_r$$

Case (1): Decimal to Binary Base Conversion:

eg: $(19.75)_{10} = (?)_2$

After decimal

2	19	1
2	9	1
2	4	0
2	2	0
		1

$$\begin{aligned}
 0.75 \times 2 &= 1.5 && 1 \\
 0.5 \times 2 &= 1.0 && 1
 \end{aligned}$$

$$(19.75)_{10} = (10011.11)_2$$

Case (2): Decimal to Octal base Conversion:

eg: $(210.23)_{10} = (?)_8$

8	210	2
8	26	2
	3	3

$$\begin{array}{l}
 0.23 \times 8 = 1.84 \quad \rightarrow 1 \\
 0.84 \times 8 = 6.72 \quad \rightarrow 6 \\
 0.72 \times 8 = 5.76 \quad \rightarrow 5
 \end{array}
 \quad \downarrow
 \quad (210.23)_{10} = (328.165)_8$$

Case (3) : Decimal to Hexadecimal base Conversion.

eg: $(1288.55)_{10} = (?)_{16}$

$$\begin{array}{r|l}
 16 & 1288 \\
 \hline
 16 & 76 \\
 & 4
 \end{array}
 \quad \begin{array}{l}
 12(C) \\
 12(C) \\
 4
 \end{array}
 \quad \uparrow$$

$$\begin{array}{l}
 0.55 \times 16 = 8.8 \quad \rightarrow 8 \\
 0.8 \times 16 = 12.8 \quad \rightarrow 12(C)
 \end{array}
 \quad \downarrow$$

$$(1288.55)_{10} = (4CC.8C)_{16}$$

Some Special Case

Case (1) : Binary to Octal base Conversion

eg: $(10110111)_2 = (?)_8$

Octal = base 8 $\Rightarrow 8 = 2^3$ (\therefore every 3 bits/digits of binary represent 1 octal).

$$\begin{array}{ccc}
 010 & 110 & 111 \\
 2 & 6 & 7
 \end{array}$$

hence: $(10110111)_2 = (267)_8$

Case (2) : Binary to Hexadecimal base conversion.

eg: $(1011011)_2 = (?)_{16}$

Hexadecimal = base 16 = 2^4 (\therefore every 4 digits of binary \rightarrow 1 digit of hexadecimal).

$$0101 \quad 1011$$

$$5 \quad 11(B)$$

hence $(1011011)_2 = (5B)_{16}$

Q2. $(330123)_4 = (?)_8$

Method 1: $(330123)_4 = (?)_{10} = (?)_8$

Method 2: $(330123)_4 = (?)_2 = (?)_8$

$$4 = 2^2$$

$$(\overline{111} \overline{100} \overline{011} \overline{011}) = (?)_8$$

$$(7433)_8$$

$$\leftarrow 2^3$$

BCD (Binary Coded Decimal) :

In this each digit is represented by its four-bit binary equivalent. It is also called as natural BCD or 8421-code and it is weighted code.

Excess-3 Code: This is a non weighted binary code used for decimal digits. Its code assignment is obtained from the corresponding value of BCD after the addition of 3.

BCO (Binary Coded Octal) : In this each digit of the octal number is represented by its three-bit binary equivalent.

BCH (Binary Coded Hexadecimal) : In this each digit of the hexadecimal number is represented by its four bit binary equivalent.

Decimal	BCD 8421	Excess-3	Octal	BCD	Hexadecimal	BCH
0	0000	0011	0	000	0	0000
1	0001	0100	1	001	1	0001
2	0010	0101	2	010	2	0010
3	0011	0110	3	011	3	0011
4	0100	0111	4	100	4	0100
5	0101	1000	5	101	5	0101
6	0110	1001	6	110	6	0110
7	0111	1010	7	111	7	0111
8	1000	1011			8	1000
9	1001	1100			9	1001
					A	1010
					B	1011
					C	1100
					D	1101
					E	1110
					F	1111

Q1. Find the base values which satisfy the equation $\left[\left(\frac{39}{3}\right)_x = 13\right]$

Ans $\frac{(39)_x}{(3)_x}$

$$\frac{3x+9}{3} = x+3$$

$3x+9 = 3x+9 \rightarrow$ This equation satisfies for all values of x
 \therefore Any base > 9 .

Q2. Find the base value which can satisfy the following two equations simultaneously.

(i) $2+3=5$

(i) $2_x + (3)_x = (5)_x$

(ii) $2 \times 4 = 10$

(ii) $2 \times 4 = 10$

$2 \times 2^0 + 3 \times 2^0 = (5 \times 2^0)$

$(2)_x \times (4)_x = (10)_x$

Ans

$2+3=5$

$(2 \times 2^0)_x \times (4 \times 2^0)_x = (1 \times 2^1 + 0 \times 2^0)$

$x > 5$

$2 \times 4 = x+0$

$x > 6$

$x = 8$

$\therefore x = 8$ will satisfy both.

Q3. Find the number of solutions of x and y to satisfy $(43)_8 = (20)_y$

Ans $y > x$
 $(43)_8 = (20)_y$
 $(4 \times 8^1 + 3 \times 8^0)_{10} = (x \cdot y + 0 \cdot xy^0)_{10}$
 $35 = x \cdot y$

\therefore No. of solutions = 9

x	y
35	1
1	35 ✓
5	7 ✓
7	5

Q4. Find the number of solutions of x & y to satisfy $(123)_5 = (x8)_y$

Ans $y > 8$
 $(123)_5 = (x8)_y$
 $(1 \times 5^2 + 2 \times 5^1 + 3 \times 5^0) = xy^1 + 8xy^0$
 $25 + 10 + 3 = xy + 8x$
 $xy = 30$

\therefore No. of solutions = 3

x	y
1	30 ✓
2	15 ✓
3	10 ✓
5	6

Q5. Result of addition of $34+43$ performed on minimum base is stored in an 8-bit register. The content will be

Ans $(34)_5 + (43)_5$

$$(3 \times 5^1 + 4 \times 5^0) + (4 \times 5^1 + 3 \times 5^0)$$

$$= (42)_{10} \Rightarrow \underline{00101010}$$

Q6 $7 \times 512 + 3 \times 256 + 6 \times 128 + 5 \times 64 + 3 \times 16 + 3$

If the number given be written in binary then number 1's present will be?

Ans

$$2^0 = 1 \quad (4+2+1)2^9 + (2+1)2^8 + (4+2)2^7 + (4+1)2^5 + (3+1)2^4 + 2+1$$

$$2^1 = 10 \quad 2^9 + 2^8 + 2^7 + 2^6 + 2^5 + 2^4 + 2^3 + 2^2 + 2^1 + 2^0$$

$$2^2 = 100 \quad 2^9 + 2^8 + 2^7 + 2^6 + 2^5 + 2^4 + 2^3 + 2^2$$

$$2^3 = 1000 \quad 2^9 + 2^8 + 2^7 + 2^6 + 2^5 + 2^4 + 2^3$$

$$\Rightarrow \underline{7}$$

Magnitude Representation

	Unsigned	Signed	Compliment	
			1's Compliment	2's Compliment
+5	101	0101	0101	0101
-5	x	1101	1010	1011

$$\begin{array}{c} r=10 \\ \swarrow \quad \searrow \\ r-1 \quad r \text{ (10's Compliment)} \\ \text{(9's Compliment)} \end{array}$$

eg. Find 9's Compliment

$$\begin{array}{r} 999 \\ - 732 \\ \hline 267 \end{array}$$

Unsigned Representation

3 bit Number
Range: 0 to 7.
0 to $2^3 - 1$
(n=3)

Binary	Decimal		
000	0	100	4
001	1	101	5
010	2	110	6
011	3	111	7

Signed Representation:

n bit number: $\{2^{n-1}-1\}$ to $\{2^{n-1}\}$.

Signed Number	Equivalent decimal	Signed Number	Equivalent decimal
0000	+0	1000	-0
0001	+1	1001	-1
0010	+2	1010	-2
0011	+3	1011	-3
0100	+4	1100	-4
0101	+5	1101	-5
0110	+6	1110	-6
0111	+7	1111	-7

1's Complement Representation:

n bit number: -7 to +7.

n bit
 $-\{2^{n-1}-1\}$ to $+\{2^{n-1}-1\}$

1's Complement	Equivalent Decimal	1's Complement	Equivalent decimal.
0000	+0	1000	-7
0001	+1	1001	-6
0010	+2	1010	-5
0011	+3	1011	-4
0100	+4	1100	-3
0101	+5	1101	-2
0110	+6	1110	-1
0111	+7	1111	-0

Q1. 001101 \rightarrow +13

Q2. 110010 \rightarrow -13

001101 \rightarrow +13

2's Complement Representation.

4 Bit Number: -8 to +7.

'n' bit
Range: $-\{2^{n-1}\}$ to $+\{2^{n-1}-1\}$

2's Compl.	Equivalent dec.	2's Compl.	Equivalent dec.
0000	+0	1000	-8
0001	+1	1001	-7
0010	+2	1010	-6
0011	+3	1011	-5
0100	+4	1100	-4
0101	+5	1101	-3
0110	+6	1110	-2
0111	+7	1111	-1

Q1. Convert the number given in 1's Complement into Equivalent Decimal.

1. 01101 \rightarrow 13

5. 11110010 \rightarrow -13

2. 001101 \rightarrow 13

6. 11101010 \rightarrow -21

3. 00001101 \rightarrow 13

7. 0000 \rightarrow +0

4. 110010 \rightarrow -13

8. 1111 \rightarrow -0

Q2. Convert the number given in 2's Complement into Equivalent Decimal?

1. 01101 \rightarrow +13

5. 11110010 \rightarrow -14

2. 001101 \rightarrow +13

6. 11101010 \rightarrow -22

3. 00001101 \rightarrow +13

7. 0000 \rightarrow 0

4. 110010 \rightarrow -14

8. 1111 \rightarrow -1

Q3. 1's Complement of $(2BFD)_{hex}$ is D402

FFFF

2BFD

D402

Q4. A number is expressed in binary two's Complement as 10011. Its decimal equivalent value is -13

Q5. The greatest negative number, which can be stored in a computer that has 8-bit word length and uses 2's Complement arithmetic is.

Ans $-\{2^{n-1}\} = -2^{8-1} = \underline{\underline{-128}}$

Q6. What is the resultant of $(C4)_{16} - (7B)_{16}$?

Ans

Q7. The number of bytes required to represent the decimal number 1856357 in packed BCD (Binary Coded Decimal Form) is _____

Q8. 11001, 1001, and 111001 correspond to the 2's Complement representations of which of the following sets of numbers?

Ans $-7, -7$ and -7 respectively.

Q9. P, Q, and R are the decimal integers corresponding to the 4-bit binary number 1100 considered in signed magnitude, 1's complement and 2's complement representations respectively. The 6-bit 2's complement representation of $(P+Q+R)$ is 110101

Ans $P = -4$

$Q = -3, R = -4$

$P+Q+R = -11$

$\xleftarrow{2's} 001011 \xrightarrow{2's} 110101$

Q10. What is the possible base of the given number system. $\sqrt{41} = 5$.

Ans $(\sqrt{41})_x (5)_x \quad x > 5$

$\sqrt{4x+1} = 5$

$4x+1 = 25$

$4x = 24 \quad \therefore \underline{\underline{x = 6}}$

Q11. -13 in 2's complement can be -?

$+13 = 01101$

$-13 = 10011$

To 2's complement: 110011

Q12. Let us consider the following equation in a 6-bit binary number system $X = A + BA$ is given. A point is $(001010)_2$ in 1's Complement binary number system, B is given as $(111010)_2$ in signed number system. What would be X in 2's Complement number system?

Ans

$$\begin{aligned} A &= 10 & X &= A + BA \\ B &= -26 & &= 10 + (-26) \times 10 \\ & & &= -250 \end{aligned}$$

$$01111010 : 250$$

$$\underline{10000110 : -250}$$

Q13. -24 in 2's Complement form is 11101000

$$00011000 \rightarrow +24$$

$$\underline{11101000} \rightarrow -24$$